25c [30c]

AUGUST, 1934

\$3.00 PER YEAR BY SUBSCRIPTION

ESTABLISHED 1917

SHORT-WAVE AND EXPERIMENTAL


-IN THIS ISSUE-

Low Cost RK-20 Radio Telephone Improving the Performance of the FBXA Better Results From Receiving Antennas Complete Data on Velocity Microphones Engineering the Class A Prime Amplifier 3-Tube R. F. Receiver Design Data The Siamese Oscillator and Its Applications



An inexpensive and efficient Oscilloscope

> Full Details in This Issue

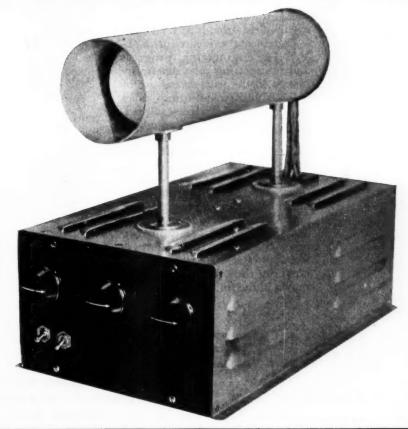

FEATURE ARTICLES By . . .

Clayton F. Bane - - D. B. McGown - E. M. Sargent - Norris Hawkins
Col. Clair Foster - - I. A. Mitchell - - W. W. Smith - - C. C. Anderson
McMurdo Silver

liable s who of our earest e is atus ANY scounts NG /6AVV ind, itors. itors. ply Store ts" d parts. g Tubes. ators,

d and socker

UBES CARPONEL CONTRACTOR OF THE CONTRACTOR OF TH

SOCKET 59

JLY PARTER NO NO 2

Individuality... Progress!

GRAPHITE ANODE TRANSMITTING TUBES

Sylvania




Every single type of SYLVANIA GRAPHITE ANODE transmitting tube represents a complete and exclusive SYLVANIA achievement -not a mere copy of an old conventional design. The eye immediately notes the rugged, clean cut, and original design of these ultra-modern SYLVANIA tubes.

A distinctly improved line of standard transmitting tubes-leading the field-that is SYLVANIA.

Convincing evidence of SYL-VANIA engineering progress and transmitting tube superiority is seen in the wide-spread use of SYLVANIA transmitting tubes among broadcast stations. Broadcast engineers, of necessity extremely critical and exacting, now generally concede that SYLVANIA tubes are superior. They are rapidly replacing the old, conventional tubes in broadcast transmitters. Today more than 35% of our American broadcast stations use SYLVANIA transmitting tubes. Stations small and largefrom 50 watts to 50 kilowatts-are now using these tubes to the extent shown in the following table:



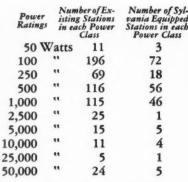


Amateurs, the world over, are enthusiastic and were among the first to "discover" these tubes. The whole field is talking about SYL-VANIA GRAPHITE ANODE tubes-they are saying good things about them.

You, too will be a SYLVANIA enthusiast once you have used these dynamic SYLVANIA GRAPHITE ANODES. Install them in your station now and enjoy the low cost per hour performance that only SYLVANIA GRAPHITE ANODE transmitting tubes can

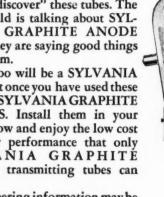Engineering information may be obtained by writing to the Amateur Radio Division, Electronics Department, Clifton, N. J.







BRANC New 253 \

3618 No

1455 G

Vol.

Amate

Wholesa time a s

ard prov

and who

had been

selling to

favor of

misunde

exceptio

fore the

which i

as Allie Walter

burgh),

pointed

well re

commit

consens

A unan

distribu

commit

rate and

and th

code to

tinue t

der th ditions

enjoy o

is almi

tutes 1

every low p

RA

prices.

though yet unde

HYGRADE SYLVANIA CORPORATION

HYGRADE LAMPS

FACTORIES: SALEM, MASS. **ELECTRONICS DEPARTMENT**

CLIFTON, N. J.

EMPORIUM, PA.



ST. MARYS, PA.

SYLVANIA TUBES

CLIFTON, N. J.

RADIO FOR AUGUST

BRANCH OFFICES: New York City, 253 W. 128th St. Tel. MOnument 2-2812 Boston, J. H. Condon, 6 Marlboro St. Chicago, C. W. Nelson, 3618 North Bernard St. Los Angeles, Calif. 1455 Glenville Drive Tel. CRestview 4017

NATIONAL MAGAZINE - PUBLISHED MONTHLY

Publication Offices-Pacific Building, San Francisco, California

Clayton F. Bane, Editor

H. W. Dickow, Business Manager.

Norris Hawkins, Associate Editor.

D. B. McGown, Technical Editor. Frank C. Jones, Ultra-Short-Wave-Engineering Editor.

Clair Foster, Amateur Activity Editor.

George B. Hart, Contributing Editor.

25c per copy, \$3.00 per year by subscription in the U.S. \$4.00 elsewhere. Send subscriptions to the San Francisco office. Entered as second class matter at the Post Office at San Francisco, California, under the Act of March 3rd, 1879.

Vol. 16

AUGUST, 1934

No. 8

RADIOTORIAL COMMENT

Amateur Price Legislation

URING the 8th annual convention of the Radio Wholesalers Association at Chicago, June 11-13, the Code of Radio Wholesaling was discussed. At the same time a meeting of radio parts jobbers was called to decide whether or not they should join the radio wholesalers. The tube group met first and were about to put through standard provisions for sale to the trade, dealers, wholesalers or distributors. Not a word had been mentioned about amateurs, and although they are getting dealer's discounts, yet under the definition of a dealer as one selling to the ultimate consumer, the amateur would have to pay list prices. Rex Munger, W9LIP of Lew Bonn Co., St. Paul, first found this defect and very strenuously argued in favor of amateurs continuing to enjoy present prices. Against considerable opposition and misunderstanding, he succeeded in making this exception of amateurs.

Later he brought up the same subject before the entire group of radio parts jobbers, which included such commonly heard names is Allied Radio (Chicago), Wholesale Radio (New York), Burstein-Applebee (K. C.), Walter Ashe (St. Louis), Cameradio (Pittsburgh), Seattle Radio Supply, etc. Of the 50 members present, a committee was appointed to investigate the advisability of joining the RWA, its existing code, and drawing up suggested changes. The amateurs were well represented by Mr. Walter Ashe on this committee, and after discussion it was the consensus of opinion that the committee should give special consideration to amateurs. A unanimous decision was made by the parts distributors to recommend to the RWA code committee that the parts business is a separate and distinct problem, not at all similar to that of the large receiving set wholesalers, and that provision should be made in the code to enable the parts distributors to continue their business the same as in the past. Theoretically, the parts jobbers operate under the blanket RWA-NRA code but they were quite united in permitting present conditions to continue, rather than to place re-

It is well to point out that radio amateurs enjoy discount privileges unusual to any other

strictions on their own business.

type of "hobbyist", including golf, photography or motoring.

Paying list prices for amateur equipment is almost an unknown "art" and approximatey 40% discount from old list prices constitutes the amateur selling price, or "effective list", as it might be called. Millions of dollars are spent by amateurs

every year and the continuation of present ow prices is of timely importance.

"N" Prefix Progress

OR about two years certain Naval Reserve amateurs and Fred Schnell, W9UZ, in particular have been working to get the letter N instead of W as a call prefix for amateurs interested in Naval Reserve work so that they quickly recognize each other over the air in emergencies, ordinary routine communication and drills. Progress was slow and Schnell finally was astounded to find that the Executive Committee of the amateur's league was the stumbling block. Knowing where to direct his efforts, he gave this matter wide publicity. The result is now well known . . . the league directors at their annual meeting reversed the decision of the Executive Committee and recommended to the Federal Radio Commission that the plan pro-

On June 29th the following order was is-

sued by the Commission:
USE OF THE CALL LETTER PREFIX "N"
BY AMATEUR LICENSEES WHO ARE COMMISSIONED OR ENLISTED MEMBERS OF THE U. S. NAVAL RESERVE. Upon the recommendation of the Navy Department the Commission adopted the follow-

In the case of an amateur licensee 384A. whose station is licensed to a regularly commissioned or enlisted member of the United States Naval Reserve, the Commandant of the naval district in which such reservist resides may authorize in his discretion the use of the call letter prefix "N" in lieu of the prefix "W" or "K", assigned in the license issued by the Commission, provided that such "N" prefix shall be used only when operating in the frequency bands 1715-2000 KC and 3500-4000 KC in accordance with instructions to be issued by the Navy Department.

Plans in the 9th Naval District are well under way for the issuing of suitable certi-ficates by the Commandant.

Here Is a Copy of the Navy Department Instructions Covering Use of Prefix Letter "N"

1. Commandants of naval districts may, in their discretion, authorize members of the naval reserve holding valid amateur radio station licenses, to substitute the prefix letter "N" for the prefix letter "W" or "K" assigned by the Federal Radio Commission subject to provisions of F.R.C. Rule 384a.

2. Use of prefix "N" shall be effective only during the life of the station license issued by the Federal Radio Commission and further only at the discretion of the commandant of the naval district in which the reservist resides or maintains an amateur radio station.

3. Amateur frequency bands in which the prefix "N" may be used will be limited to the frequency bands 1715-2000 kc., and 3500-4000

4. Amateur stations authorized to use the prefix "N" will be subject to all rules and regulations of the Federal Radio Commission prescribed for amateur radio stations.

5. The prefix letter "N" when authorized by commandants may be used for general communication between U. S. amateurs, but not with foreign amateurs, and need not be conned to naval reserve drills or naval reserve

6. The authority to use the prefix letter "N" by any amateur station, may be revoked at any time by the commandant of the naval district for any violation of the regulations, improper or injudicious use, needless inter-ference or other objectionable use, or as a disciplinary action in connection with the administration, training or drilling of the naval reserve.

all persons authorized to use the prefix letter 7. Commandants will maintain a record of and of all cancellations of authority for its use. Cancellation by a commandant of authority for use of the prefix letter "N" will not affect the validity of the Federal Radio Commission license nor the right of an individual to use prefix "W" or "K."

8. The monitoring stations of the Federal Radio Commission will make no reports on the use of the prefix "N." If any member of the navy or naval reserve observes use of the prefix "N" by an amateur not authorized to do so, he shall report this fact to the commandant of his district with all details as to time, type of operation, etc. The navy de-partment will bring such operation to the at-tention of the Federal Radio Commission. Any other violations of the regulations observed by Federal Radio Commission will be taken up directly by that commission with the amateur regardless of whether an "N," "K," or "W" prefix is used.

COL. FOSTES COMMENT

READ IT AND WEEP

HAVE you read the official reports of the annual meeting of the ARRL directors?

You get your account of the meeting in two doses, a narrative by K. B. Warner and the "Official Minutes". Both accounts are replete with self-praise, self-righteousness and self-justification.

The narrative says this meeting of 1934 was one of the most important the directors ever held. It was, and for the reason that the directors were called upon to meet three charges of vital importance to all amateurs: (1) That the Secretary-Manager had concealed in his reports to both directors and members the true wording of the new amateur regulations of Madrid. (2) That the Board of Directors had not determined the ARRL's policy of not opposing ratification of those regulations. (3) That the ARRL membership is made up more of commercial radio people and other non-amateurs than of licensed amateurs.

For months prior to the meeting these charges had been hurled at the ARRL head-quarters from all parts of the country and directors had been bombarded with them. Now just look through all parts of the published reports of the meeting and see if you can find that even ONE of these charges was met. All you will find is Warner's declaration that the Board spent five hours in examining and discussing the various criticisms and that "It found no justification for any of the charges that have been disturbing members and voted hearty commendation of the Secretary and other officers for their conduct of League affairs."

Just note how the directors did their investigating. When the subject came up the New England director immediately moved a resolution of confidence in Warner and hearty commendation of his conduct of League affairs; AFTER which they spent five hours "investigating". Render the verdict first and "investigate" afterwards!

But the verdict was all foreordained. President Maxim had previously devoted most of his annual report to plastering all those who had dared to question Warner's actions, and to enveloping himself, Warner and the ARRL in general in an aura of righteousness. He had called our criticisms falsehoods, slanderous, lies, and used various other forms of invective. He had used many of the psychological devices for formulating the thoughts of men who are unacquainted with the technic and how to keep from being influenced by it. The devices of shame, fear, command, exhortation, threat, and what not. His report abounds with varying forms of mental influence. I'll give you, direct from Mr. Maxim's report to the directors—which you can get from your director if you care to read the whole of it—some examples:

SHAME—"Decent men and women cannot be expected to remain in an organization composed of persons who stoop to such practices as the leaders of the present agitation".

FEAR—"ARRL must positively be purged of this sort of thing or our end is in sight."

COMMAND—"Your president requests

that this Board announce its position as regards its officers in clean-cut and unequivocal language and then take positive steps to prevent a repetition of the present agitation. If there is the slightest doubt on the part of the Board as to the integrity and ability of the officers an unbiased investigation will quickly disclose the truth."

EXHORTATION—"If there be one duty to which the present Board should address itself it is to decide upon the policy and the means of doing this unmasking of those persons who are guilty of falsehood concerning

THREAT—"To challenge the honesty, sincerity and loyalty of the officers and head-quarters staff is to challenge the honesty, sincerity and loyalty of your president. Your president is not the kind of person to have his integrity challenged when he knows he does not deserve it."

ND so the directors, honest and sincere though they be, came to the meeting with their minds all made up for them. And so that they should not forget how they were expected to vote the New England director makes his motion aforesaid to bring to vivid recollection the pronouncements of Mr. Maxim's annual report. Neat work—of its kind.

Mr. Maxim is a tradition with the ARRL. The League is his child; he brought it into being. For several years after it was born it gave promise of great usefulness. Then it came under an evil influence and fell far from grace. It began life as an association wholly of licensed amateurs. It continued so until a year after Warner took it in charge. Then suddenly it became a league of any old thing that happened to subscribe for QST. It continued to parade as a league of amateurs and does so to this day. But it is not. How the change came about and who profited by it enormously in cold cash we reserve for another story. But the fond parent still cherishes the child as his own and anyone who dares to criticize its failings just isn't fit to associate with "decent" people.

To make the directors feel that their white-

washing of Warner had substantial outside approval, communications endorsing Warner were read to them from two men whose opinions... if they were not now in the employ of commercial concerns which pay money to QST for advertising their goods to amateurs—would certainly carry weight.

It is certain that many directors, too, had in their possession communications bearing testimony directly adverse to the two that were read to the Board. For example, the St. Louis Club of Kerr's division had wired him just before the meeting a message demanding the removal of Warner and telling Kerr they wanted that message read to the directors. Kerr had the message right before him at the meeting and yet never mentioned it. So it is a cinch that around that directors' table there was much testimony adverse to Warner and his conduct of League affairs that never emerged from concealment.

Perhaps Kerr was relying upon the letter Warner wrote to certain directors some two years ago in which he gave a new slant to his oft-published assertion that the League has "truly representative government—nothing could be more so—just like the United States Government—the majority rules." If you want the exact wording of the letter get it from your director—if he received one. Not all directors did. I seem to recall that I was a director at the time, and I know I never received it—from headquarters. In this letter Warner indicated that directors should stick by their own individual views rather than those of their constituents because there was no bi-chamber organization in the ARRL corresponding to the House and Senate in the United States government, and so a League director while he should act as a "representative of the people" should at the same time act as a "statesman"; that a League director's higher duty was to look at amateur radio as a whole and then do what was best for the majority; that his higher duty might often demand that the director disregard the mandate of his own division, duly expressed.

THE Pro me and righ

pletely ence, eit able of

their lo

men so

growing

and right short, a can spe-

furtheri

going f

sibly se

teurs of

in the a

ing the

into ac United

It Is N

the of

has no

no regidues. Toolly a

amateu

ciation

of men

It is a

and vi

quate 1

ment t

rights e

fortuite

sumed

take th

Congre

resigne

cial con

to exer

our rig

of the

the lic

mined

I le

but 12

dicken

of poy

antenn

as the

you

hear, c

utmost

We co

20 mi

frigera

frenzy

someth

RA

In th

In ot

A mo

of his own division, duly expressed.

And that's just the kind of "representation" most of us ham have been getting—assurance that we are getting real representation while our directors are tipped off from headquaters to give us the run-around. How do you like it? And compare this with Warner's opening statement in his description of the Board meeting: "As every radio amateur knows, this annual meeting of the Board is the high point in amateur affairs of the year, for at this time the policies of the League are gone over in minute examination, responsive to the wishes of the majority of the members, and new plans made for a coming year. With every director present, fully conversand with the wishes of the amateurs in his region, it was possible to make a thoroughly intelligent survey of all the affairs of amateur radio."

What About the Commercial Members?

OW, all this refers to representation of amateur members of the ARRL. What about the representation of the commercial and non-amateur members? They are the majority owners of the ARRL's property and assets. They assuredly HAVE representation, for no business man has a money interest in ANYTHING unless that interest can be made useful to his business. These commercial members cannot well get their rep resentation directly through the directors, for the directors have very little direct contact with them. You will notice that Warner says each director is "fully conversant with the wishes of the AMATEURS in his region." League officers have frequent contacts with commercial members but directors do not. But it is by action of the directors that the interests of the commercial members are looked after; so there must be liaison between them and the directors. Just who are the intermediaries who carry their wishes to the directors? Obviously it must be the officers of the League. So the advice that directors get from the officers must regard the interests of these majority owners of the ARRL's business and assets; either that of their interests are being ignored. And if you (Continued on page 34)

6

A. R. P. A.

HE PURPOSE of the Amateur Radio Protective Association is to provide a medium devoted wholly to the interests and rights of the transmitting amateurs, com-pletely divorced from all commercial influence, either within or from without, and cap-able of recovering for the amateurs some of their lost rights and frequencies. A body of men so strong that it can secure for the growing ranks of the amateurs frequencies and rights commensurate with expansion. In short, a group of leaders that legitimately can speak vigorously and act aggressively in furthering the interests of all amateurs.

A movement that does not meet the foregoing fundamental requirements cannot pos-sibly serve the needs of the licensed ama-teurs of America today. There are many men in the amateur ranks who are already grouping themselves under the aims of the ARPA into active units in different parts of the United States and Canada.

nt to his

gue has

nothing

d States

If you

r get it ie.

at I was

I never

ld stick

er than ere was

in the

League

resenta-

me time

irector's

radio as

for the

ften de-

mandate

ntation' ssurance

n while

eadquar-

do you

Varner's

of the

amateur

Board is

he year.

League

respon

ne mem-

ng year.

nversant

region

radio."

mbers?

ation of

They are roperty resenta y inter-

rest can se comeir rep ors, for

contact

ner says

ith the

region.

ts with

hat the

ers are

etween are the to the

that di-

ard the

of the

that or

JST

Not

It Is Not an Organization . . . It is a Movement

THE ARPA IS NOT an organization in the usual sense. It is loaded with none of the mechanism the usual sense. It is loaded with none of the machinery of organization. It has no constitution, no by-laws, no rules and no regulations, no directors no officers, no dues. There is nothing to "join." There is only a set of principles and aims for each amateur to work for. The ARPA is an association of ideas replaced to the control of ideas and association of ideas are benefit to the control of ideas are the control of the control of ideas and association of ideas are the control of the control of ideas are the control of the control of ideas are the control of the con dation of ideas rather than an association of men.

In other words, ARPA is a MOVEMENT. It is a movement to get method and courage and vigor into the process of securing adequate rights for all amateurs. It is a move-ment to take the safeguarding of amateur rights out of the realm of the haphazard and fortuitous and place it in the position as-sumed by other large bodies of citizens who take their wishes severally and en masse to Congress. It is a movement to stop accepting resignedly such "privileges" as the commer-cial corporations permit us from time to time our right to our share of the air as citizens of the United States. It is a movement of the licensed amateurs to stop having our tights as citizens of the United States determined to the total states are the united States determined to the total states are the united States determined to the total states are the united States determined to the total states are the united States mined by a few commercial corporations and

a horde of quarreling Europeans. It is a movement to cease permitting any one man to be the sole official mouthpiece for all the licensed amateurs of America and, in-stead, to have many articulate spokesmen whose interests are wholly amateur—to per-mit all amateurs to speak directly with the instruments of government instead of de-pending upon a small but highly centralized "control" to voice their wishes.

It is a movement for the exercise of the

right of every citizen of a representative government to carry his wishes directly to his representatives. It is a movement to make known that the 40,000 non-commercial radio stations in the United States are potentially a great asset of the public and the nation, and that the rights of these non-commercial stations shall not be left at the mercy of a few commercials. It is a movement to show that non-commercial radio men are a class of citizens so self-respecting that they may demand and exact the respect of all other users of the air. It is a movement to ensure the voice of amateur radio in the halls of

Congress Recognizes the Amateur

PRIME ESSENTIAL of the movement is that the various groups and interested individual amateurs throughout the country shall make it their continuing job to inform their senators and representa-tives in Congress of the amateur position in any given situation and at all times. All that Congressmen need is that in any specific case they be informed fully and truthfully. The Congress will listen with an open mind to the requests of the licensed amateurs. One of the keenest observers of all movements in the communications field writes us from Washington, "The few protests you amateurs made against the Madrid treaty created a lively impression on senators who have been most concerned with radio legislation, and Congress is now disposed to give the amateurs everything they ask within reason.

Why Wait Until 1937?

ND THE TIME to begin speaking is NOW. The day is past for the futile practice of the whole amateur body to sit quietly and inertly awaiting the pleasure of the commercials and foreigners at Cairo in 1937. It is Congress that can decide that great areas of the air now held by commercial corporations but not of use to them shall be devoted to stations-amateur or otherwisethat are disgracefully cramped. And when Cairo finally does come along it is the Congress of the United States that will determine what the non-commercial stations of the United States require to permit them to serve the interest of the public and the nation. One of the chief concerns of the ARPA groups is the recently enacted Communications Bill that sets up a new alignment and control of all communications. The most important item in the Bill is the provision for a special report to be submitted to Congress by February 1, 1935, recommending the new detailed legislation necessary for the proper control of all communications. If the amateurs do not now see that their rights and interests are properly protected in this report then they will have no one to blame but themselves for the amateur restrictions the commercials will surely insert in the new radio law of the United States. It is easy to keep such restrictions out now; it is exceedingly difficult to get them out once they are incorporated in the law. This is infinitely more important and immediately necessary work for the amateurs than hazy speculation on what may or may not "happen" at Cairo in 1937. The various groups of the ARPA will get on their toes now, and not only keep in touch with the progress of this report that will recommend the provisions of the new law, but they will formulate recommendations of their own to be incorporated in it.

That is what the ARPA is, and if you are a live amateur you will enter heartily and energetically into the movement of the intelligent and forthright men who are resolved that the rights and interests of all amateurs shall be properly guarded and promoted.

The ARPA will function independently of existing amateur associations, fraternities and leagues. It will protect the interests of all amateurs, regardless of their present affiliations. It holds malice toward none.

Antennas for City Dwellers

HE recent craze of antennas 260 feet long (and longer) gives us poor city dwellers the jitters. Our own lot is but 120 feet long and inflexible as the very dickens!


In these days of many stations using plenty of power, the problem of the transmitting antenna does not worry us nearly as much as the receiving antenna. The old adage, you cannot work that which you cannot hear, etc." still holds good. One factor of utmost concern to ye city dweller is NOISE. We counted 70 autos passing the house in 20 minutes. Power leaks, oil burners, re-frigerators and other infernal gadgets exact their awful toll of DX. Driven to a near frenzy by power noises, we decided to see if something couldn't be done to remedy the situation. Doublet antennas long since prov-

By CLAYTON F. BANE

ed to be fine noise collectors in this location. so here's what we did.

The receiving antenna for 14 MC was a full wave affair and was about 40 feet off the ground at both ends. This antenna was let down and fitted into a convenient stretch of the yard. The height above ground was carefully measured until both ends of the carefully measured until both ends of the antenna were an exact quarter wave above ground. It happens that a quarter wave is a mere 15 feet, thus you can readily realize that, theory to the contrary, many misgivings were felt as to the probable effectiveness of this low antenna. This may have been somewhat exaggerated in our case because we belong to the old school, "The higher, the better." Anyway, to waive all preliminaries,

the effect on the noise was remarkable. Signals that could only be read with difficulty on a higher antenna were now QSA5. Weaker, true-but none-the-less much more readable. Of course, this type of antenna with the ground acting as a reflector is naturally a high-angle affair, and apparently discrimi-nates strongly against the ground wave and other low-angle components. Attesting the soundness of this theory, a great many European signals (DX to us) which had a perfectly solid body on the higher antenna, had that peculiar "shaky" characteristic of signals from the same station coming in from different directions and slightly out of phase, and also of extreme high angle radiation. It should be stated that this hollow effect in no way deterred from the readability of the signals, since the lack of noise more than offset this trouble. (Continued on page 23)

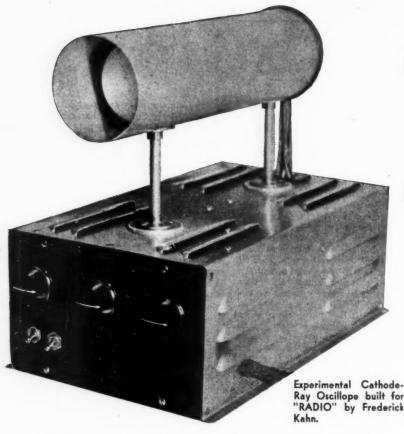

Cathode Ray Tube Theory and Application electron cause the

of the ribeam is

ing the the bea face of changin

up and coils, v

the pla

vantage an infin they man nate an netic C ance to

would

Havi

eration

ample

operati

ture ha

fact the

tive in

one up

One

age an

case, it

former

correct

intensi spot o

be car

this sy good brillia

ing of

an inc

indeed If, ho

even e

ably b

in the

erable

ple an

flectin

ing n

capab

point

acteri

906 t

spot,

makes

is lar

In a

By CLAYTON F. BANE

A LTHOUGH long known by scientific workers and laboratorians, the cathode ray tube has, until recently, remained a mystery to the average amateur. Progress in any line is never possible until the industry, as a whole, has the product available, and at a reasonable price. With many of these tubes now in use, valuable data on refinements and improvements can be gathered collectively, instead of from a small, select group.

group.

The reasonably-priced cathode ray tube gave the needed impetus to place this valuable device in the hands of the technical amateur. There can be no doubt that a cathode ray tube, in conjunction with associated apparatus, will soon become a standard piece of apparatus in all good amateur stations.

Left—The RCA 906 Cathode-Ray Tube. Right—Close-up of Deflector Plates.

When television emerges from the laboratory, those who now acquaint themselves with cathode ray tubes will be among the first to profit.

Much has been written about cathode ray oscilloscopes for determining character of modulation and allied measurements. A rather careful perusal of the various articles has failed to disclose any that gave a careful, elementary explanation of the basic principle of the cathode ray tube. With this fact in mind it is felt a proper understanding of the principles will serve a definite purpose for those who may eventually be called upon to handle similar tubes for television purposes. It goes without saying that the proper understanding is also invaluable to those who will merely use the tubes for their own experiments.

A cathode ray, instead of being something mysterious and technical, is in reality nothing more than a high velocity stream of electrons, traveling from the cathode (or filament) to plate.

In physical characteristics, the average tube has the general shape of a funnel. That por-tion which would be the neck, in this case, is made considerably larger in diameter, and that portion which would correspond to the mouth is a closed end, slightly convex. It is on this end that the cathode ray comes to focus. A cathode or filament is sealed into the narrow end, this cathode serving as the electron emitter. The grid is between this cathode and the plate. This is the simple, basic type of tube. Many of the present models have an additional grid. The plate has a small aperture through which the electrons from the cathode pass. When the cathode is heated, electrons are given off and if a positive potential is applied to the plate these negative particles will be attracted toward the plate in a continuous stream. As has been mentioned, this plate has a small opening in its center through which some of the electrons may pass through and into the outer portion of the envelope. It can be readily understood that if a varying potential is applied to the grid, the number of electrons passing through the plate can be controlled in much the same manner in which the grid of an ordinary vacuum tube controls the plate current. The application of the grid in the cathode ray tube will be discussed later in this article.

Let us now return to the stream of electrons coming from the opening in the plate. As these electrons travel out into the open portion of the tube, they no longer hold to a narrow stream, but gradually spread out as they get farther away from the plate. Un-less the initial velocity is very great, the negatively charged particles begin to exert a repelling force on one another and spread apart. The resulting "cloud" is useless for all practical purposes, so it becomes necessary to resort to some means of obtaining a narrow stream, keeping the beam in focus. There are several ways in which this can be achieved, although admittedly some are much better than others. The first and most practical is to use an extremely high positive potential on the plate, so as to give the electrons such a treemelous initial velocity that the beam does not lose its character. Many of the earlier types of tubes were filled with gas, Argon being generally used. As the gas, Argon being generally used. As the negative electrons pass through the gas they cause ionization, with the result that the positive ions collected around the negative electrons (unlike-forces attracting), and tended to "squeeze" or keep them in line, i.e., in focus. Gas filled tubes have the disaders are the disaders are the statement of t vantage in that the impedance across the deflecting plates is not infinite and, consequently, would render certain types of measurement impossible, due to loading of the circuit under measurement. Varying the temperature of the cathode will also cause the beam to focus sharply. A solenoid around the narrow arm of the tube has also been used as a focusing medium. All in all, the high vacuum type of tube using very high plate potentials is considered much more satisfactory than any of the other systems.

Certain chemical substances have the unique property of being fluorescent, i.e., when they are struck by an electrical charge they give off light from the areas exposed to the charge. As an example, Calcium Tungstate will give off a blue light under these conditions, while Zinc Silicate will give off a yellowish-green light. If the large face of a cathode ray tube is coated with such a fluorescent substance, a spot of light will appear on the face of the tube when the cathode ray beam strikes its surface. If we can cause this spot to move in some regulated manner it can be seen that we can reproduce its movement in the form of light on the face of the tube.

face of the tube.

If a magnet is placed in proximity to the electrons' beam it will be seen that we can cause the spot to shift into any position on the face of the tube by changing the position of the magnet. This proves that the cathode beam is very sensitive to magnetic effects and suggests a means of controlling the beam. A number of tubes use magnetic deflection by using large coils placed in horizontal and vertical relation to the beam so that by varying the current through the horizontal coils the beam will be made to move across the face of the tube horizontally. Inversely, by changing the current through the vertical coils the spot may, at the same time, move up and down. If, instead of using magnetic coils, we place flat plates within the tube and in the same relative positions with respect to the beam, we can achieve exactly the same result by varying the potentials on the plates. This latter system has the advantage in that the plates offer practically an infinite impedance to any load to which they may be connected and in this way eliminate any loading effect. Obviously, the magnetic coils would offer a very finite impedance to the same load and, consequently, would be unsuited to many types of work entirely feasible with electrostatic deflection. Having discussed basic principles of operation, we will now take up a specific example of an oscilloscope that has been in operation in our laboratories. Most literature has failed to place enough stress on the fact that such a device is an extremely sensitive instrument. Of course, anyone can hook one up and obtain operation of some sort, but we certainly cannot stress too strongly the fact that correct design is absolutely necessary if the full capabilities of the tube are to be realized.

ntrolled

the grid

rols the the grid sed later

lectrons

ate. As

en por-

out as

e. Un-

eat, the

exert a

spread

s for all ecessary

g a nar-

focus.

can be

e much

st pracpositive

he elecity that Many

ed with

As the

hat the

egative

in line,

disad-

the de-

equent-

he cir-

temp-

and the

n used

e high

n plate satis-

e the

charge osed to

Tung-

ive off

face of

such a

en the

If we

ulated

on the

ST

One prolific source of trouble in the average amateur oscilloscope is AC pick-up, or AC ripple. This may be caused by wrong placement of the transformers and, in this case, it is easily cured by mounting the trans-formers in such a manner that they have no effect on the beam. Put some flexible leads the transformer and move it around until the minimum effect is noted. The test for a correct spot is very simple. It should be pos-sible, by manipulation of the focusing and sole, by manipulation of the focusing and intensity controls, to obtain a perfectly round spot on the screen. For purposes of testing, be careful to avoid having the intensity of this spot any greater than is necessary for good definition. A prolonged holding of a brilliant spot on one place on the screen may destroy the fluorescent material on the streen, and in extreme cases may cause heating of the glass with attendant possibility of puncture. If the spot, when brought up to a size of approximately three-eighths of an inch is perfectly round, or at least has outside edges that are sharply defined, you are indeed lucky and need have no further worry. If, however, the spot, instead of being an even one, has a tendency to show a ragged edge, you have AC. This may also conceivably be due to an incorrect bleeder and filter condenser combination, which would result in the output of the rectifier having considtrable ripple; this cannot be tolerated. Ripple and pick-up must be cleared-up before an attempt is made to put voltage on the deflecting plates.

In addition to being very regular and having no ragged edges, the spot must also be capable of being drawn down to a mere point of light without changing its characteristics. It should be mentioned that the 906 tube is capable of producing a round spot, although this may not be true of other makes of tubes, since the shape of the spot is largely dictated by the shape of the emitting surface of the cathode, the spot in some tubes being square!


If the spot when drawn very small shows a halo, this phenomenon may be due to: (a) insufficient bias to focusing electrode. (b) Too-high filament current.


If, when the spot is drawn down in size, it has a tendency to elongate or take a curling shape, it is possible that the beam is being pulled out of shape by some stray field. This field can well be caused by some large mass of metal in the immediate vicinity. If this statement sounds improbable, just take a piece of metal that has possibilities of being magnetic, and hold it close to the tube. Another thing that sounds almost ridiculous, but is nonetheless true, is that the spot will probably be in a different position on the

will probably be in a different position on the face of the tube, depending upon the time of day! This is simply another way of saying that the beam is affected by the earth's magnetism. An iron or steel shielding tube should cover the cathode ray tube so as to act as a magnetic shield. The shield tube should first be de-magnetized.

If it is impossible to make the spot go down to a fine point, it is well to look to the voltage on the cathode as the source of trouble, since low voltage on this element will play havoc with the focus. Practically the same effect will be noted if too-high bias is applied to the focusing electrode. The cure in both cases is obvious.

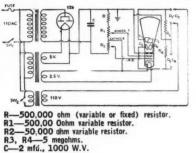
When the spot has been cleared-up to conform to the extent that we have insisted upon,



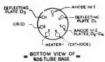

Circuit diagram used in "RADIO's" Oscilloscope

it is then time to apply some type of sweep circuit to the horizontal deflecting plates so that the spot may be drawn out into a line. For simple applications, a one-to-one ratio transformer can be utilized as a source of sweep voltage. The input of this transformer, of course, is connected to the 110 and the output to one deflecting plate and ground. By varying the control on Anode No. 1 the spot can be drawn-out into a line, and the intensity of the line varied by the grid bias control. The line gives the appearance of standing still, but actually the line effect is caused by the spot moving back and forth across the face of the tube at the frequency of the sweep voltage. The familiar "persistence of vision" takes care of the movement to give the effect of a solid line. If hum, halo, distortion and other troubles have been previously removed, it is possible that the line can be drawn into a sharp, clear affair by manipulation of the focusing controls. Since this line is to be the index line, and since it will remain in the same relative position regardless of the type of sweep used, it is generally considered to make it parallel to the table on which the instrument rests.

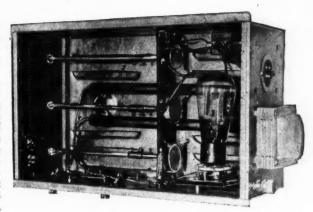

Under chassis view of the Oscilloscope. The rectifier tube is a 5Z3. The variable resistors are fitted with long coupling shafts.

Moving the socket that holds the tube is a very easy way of achieving this result. Thus it is wise not to permanently mount the tube socket until one sees the angle of the trace line.

The circuit diagram shown is similar to the one which we are using in our oscilloscope. This circuit is an exact duplicate of the one recommended by RCA in various application bulletins. The output from the high voltage transformer should be approximately 1000 volts, and since the current drawn is extremely small, one of the small transformers used for the better type broadcast sets should prove very suitable. Since the current taken from the condenser is so small, and since the charging of this condenser takes place during a small fraction of the AC cycle, the output from the rectifier is assumed to be equal to the peak voltage of the transformer. Use a small transformer with the entire winding, instead of the center-tap methods, as is usual in the conventional full-wave rectifier. Careful consideration must be given to the selection of the size of bleeder resistor and filter condenser if the value of ripple is to be kept as low as it should be for proper operation. Using common values of bleeder resistance, a 2 microfarad condenser is a very safe value. According to the excellent graph in RCA "Application Notes No. 39" the value of this condenser in conjunction with a one-megohm bleeder would give a value of ripple voltage approximately 0.2 per cent, which is very low. From the same source we find that a 1 mfd. condenser with the same value of bleeder would give about 0.5 per cent ripple.

Again referring to the circuit-the value of R3 and R4 can be anything from 1 to 10 megohms, although we have found that 5 megs apparently makes no difference. One thing that will be seen to differ from usual practice is that the positive high voltage is at ground, and that the cathode (filament) floats. The insulation of the filament transformer must be capable of withstanding the plate voltage if breakdown is to be a ided. At this point, one very serious caution is necessary. Most of us have developed a carelessness when working with low voltages. Remember—don't be deceived by the small size of the transformer used in these -a thousand volts, aside from oscilloscopesinflicting a jolt that will long be remembered, is also capable of inflicting fatal damage under certain conditions! (Confidentially, I have three nice scars on my hand, attesting to the viciousness of "a mere thousand volts").

It is hardly within the scope of this paper to go into greater detail as to the various applications of the "Scope". We intend to take up this phase in detail in a subsequent

(Continued on page 17)

RADIO FOR AUGUST

The New W9USA at the Chicago Fair

THE Science Theatre at A Century of Progress presents an adventure in the popular branch of present-day Science—Radio. This feature is sponsored through the cooperation of The World's Fair Radio Amateur Council, and you see in the photographs the equipment of a radio station which has been assigned by the Federal Communications Commission the call letters W9USA.

All of this apparatus has been constructed by Mr. Royal Higgins, W9AIO, who will personally be in charge of the demonstration. He will be assisted by Mr. Jack Stanton, W9PSP, who will operate the receiving end of the equipment located on Northerly Island.

attempt to find some location sufficiently quiet for 14 MC reception. A spot was found on Northerly Island which seemed to fill the bill. It is appropriate at this point to comment on the 100% cooperation given this feature by A Century of Progress. Mr. Farrier, an official in charge of Events, whole-heartedly granted every desire. A small shack was set up on the island and to it were run power and fone lines. Four forty-foot concrete embedded poles were installed, antennae hoisted and then things began to move. The RCA exhibit donated a World Wide antenna which, incidentally, has proved well worth while. At this time the only way a favorable signal to noise ratio can be maintained is to use antennae with directional reflectors. Three receivers are housed in the shack, the output of any one, or all three being fed into the 500 ohm PSC line back to the stage. The shack on the island and the stage are separated by


to p.p. 56's, to p.p. 2A3's all Class "A". Notmal input to the Class "C" stage, which feeds a 132-ft. single wire fed Hertz, is 400 watts, Under actual measurement, an output of 212 watts of RF is obtained.

watts of Kr is obtained.

In the first five weeks of operation, the station has worked 44 states, and has been heard in all 48. Confirmation of reception has been received from fifteen foreign countries, and contact has been made with four. It might be of interest to mention that W9. USA at the Hall of Science acknowledges all cards. Two different cards are used, one for acknowledging those received from SWL's, the other goes to amateurs in confirmation either of a QSO or a heard report. All cards must have Hall of Science on them to be properly delivered.

W9USA at the Hall of Science—in Chicago,

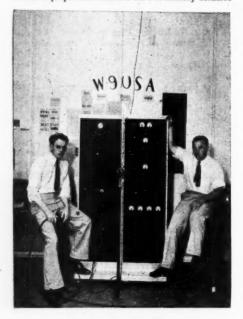W9USA at the Hall of Science—in Chicago, would like to voice genuine appreciation to all amateurs who have made the presentation




Left—W9AIO and W9PSP at the W9USA transmitter panels

Right—Northerly receiving antenna of W9USA.




Below: Left — W9USA Radio Room.

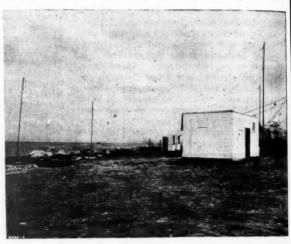Right—Hall of Science Theatre Where the Presentation Is Made.





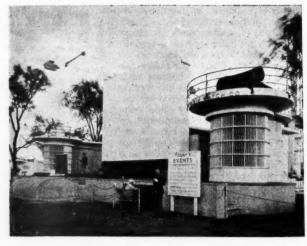

Such signals as he receives will be sent to

this point over telephone lines.

This equipment has been in contact with forty foreign countries in five continents.

Unfortunately, not all of W9USA is presented to the audience. Should all of the headaches which went into the installation of W9USA at the Hall of Science be known by the audience the presentation would be more appreciated.

The old adage that you can't work what you can't hear was all too apparent when a receiver was set up on the stage. Imagine the QRM from 1,200 electrical gadgets demonstrating electrical phenomenae only 350 feet removed from the receiver. Receivers were lugged all over the Fair grounds in an

about three-quarters of a mile. This line is split so that input is afforded to the PA system of the Court of the Hall of Science as well as for a pair of headfones for the operator on the stage. Ordinarily no higher level than a minus 6 db. is fed over the fone lines.

The various units comprising the transmitter, after a little preliminary friction with the electrical union, were mounted in the two W.E. racks and testing at the Fair grounds began May 24. The RF section consists of a 59 oscillator with a 7080 KC crystal, a 59 doubler, a '10 buffer, a 211 buffer, followed by the final p.p. 211 Class "C" stage. This stage is modulated Class "B" by two 203A's. The input amplifier working from a double-button carbon microphone is a 56,

of Amateur Radio to the public a possibility. What the amateurs are doing in working this station, especially from 5 to 5:30 C.S.T. every day when the transmitter is on the stage for the feature, is a concrete example of the spirit of amateur radio. Exemplary of this spirit, and a fitting example to be followed is the wonderful cooperation given by K4SA.

wonderful cooperation given by K4SA.

Other than the 5 to 5:30 C.S.T. period ham phraseology is preferred. But, when W9USA is presented to the public, the conversation should be in English and as non-technical as possible. "Please—leave out such tomfoolery as diddle de bump de bump . . . (at all times for that matter)" . . . reads a request from the Fair. This is a "show" given to the public

(Continued on page 32)

two year larity of simple, tion to much in Fund crystal the mos when it one fre several beyond

pocked are con themgood self in freque quence a min

fying

crysta
coil.
The
ming
very
persu
tiona
ously
oscill
run a
cryst
grav:
cryst
sible
high
outp

rysi quad Fig. trite prop crys Sian siste met

W

con erat obta acro tap' met

RADIO FOR AUGUST

The Siamese Exciter

By W. W. SMITH, W6BCX

VITH the influx of amateurs into the 14 megacycle band which began to assume appreciable proportions some two years ago ,and with the growing popularity of the 28 and 56 megacycle bands, some simple, economical means of obtaining excitation to the high-frequency output stage was much in demand.

Fundamental control with a tourmaline crystal although the most simple, is far from the most economical. This is especially true when it is desired to operate on more than one frequency within a band, necessitating several tourmalines—one of which is usually beyond the reach of the average amateur's or eight watts of precious "ten meter RF" can be obtained. By substituting a graphite anode 841 (high mu 210) for the 46, the input to the doubler stage can be raised to twice the output obtainable from a 46. Some efficiency will be lost, to be sure, but it can be tolerated for the sake of output.

The Siamese will also fully excite another 53, used this time as a "push-push" doubler. The tube is connected as though it were two separate 46's—the same values of circuit constants being correct for the single 53, except that the plate voltage should not run much over 300. To effectively couple from the output of the Siamese into the "push-push" grid

time to restore oscillation. If the capacity of C3 is raised beyond a certain value, oscillation will be unstable or may even cease, regardless of the spacing adjustment. The capacity should then be backed-off a bit from that value, or until steady, stable oscillation is had with correct spacing of turns on L2. By heavily loading the oscillator in this manner, the crystal current is kept down to a low value and the drift is negligible. The tank L1-C1 is low-C and resonates at

wice the crystal frequency. The condenser C1 should be just large enough to tune the

When the exciter is completely tuned and



'A". Nor. hich feeds 400 watts

ut of 212

ation, the

has been

reception

ign coun.

vith four.

that W9.

ledges all

l, one for n SWL's

firmation

All cards

m to be

Chicago, iation to sentation

sibility.

ing this

every

age for

e spirit

od ham

V9USA

rsation nical as


foolery

1 times


om the public

ST

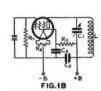
CRYSTAL OSCILLATOR, indamental circuit using triode



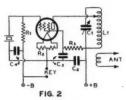
PENTODE EXCITER TYPE OSCIL-LATOR, fundamental circuit R1—20,000 ohms. R3—50,000 ohms C3-C4—.004 mfd.



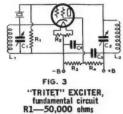POWER PENTODE TRANSMITTER Type Oscillator R1—20,000 ohms R3—50,000 ohms C2-C3-C4—.004 mfd.





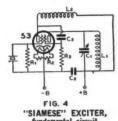

'SIAMESE' EXCITER, fundamental circuit C2—.004 mfd.

pocketbook. Low frequency quartz crystals are comparatively cheap, a whole flock of them being obtainable for the price of one good tourmaline. The problem resolved itself into the development of high-efficiency frequency multipliers so that the lower-frequency quartz plates could be utilized with a minimum outlay of equipment.

Then someone got the bright idea of modifying the Dow oscillator, whose output circuit is rich in harmonics, so that a quartz crystal could be used in place of the grid toil. Thus evolved the "Tritet" of today. The fundamental circuit, without any trimmings, is shown in Fig. 3. It is usually a very ready oscillator—crystals that can't be persuaded to oscillate at all in the conventional pentode oscillator will oscillate vigorously in the Tritet. In fact, the crystal usually oscillates so hard that unless the exciter is run at very low voltages, there is considerable crystal heating—the harmonic operation ag-gravating the frequency drift. To keep the ctystal current down to as low a value as pos-sible, the cathode coil, L1, should be fairly high-C. For maximum harmonic output, the output coil, L2, should be as low-C as it is possible to make it.

While not performing multiplication of the crystal frequency as well as the tritet when quadrupling, the "Siamese" exciter shown in Fig. 4 will give just as much output as the titet at twice the crystal frequency, and, when properly adjusted, with less heating of the crystal. There are also fewer parts in the Siamese, one less condenser and one less resistor being required. When used with a 40-title are also fewer parts in the siamese, one less condenser and one less resistor being required. When used with a 40-title are also fewer parts and for the second condenser. sistor being required. When used with a 40-meter crystal, it will fully excite a 46 (triode connected) or 59 (tetrode connected) regenerative doubler. The regeneration may be obtained either by using a skimpy by-pass across a cathode resistor, or by a "neutralizing tap" and feedback condenser. The former method works well at frequencies above 14 megacycles, while the latter system is to be preferred at the lower frequencies. Thus, with her translations the 53 used with a 40-meters. preferred at the lower frequencies. Thus, with but two tubes, the 53 used with a 40meter crystal in a Siamese, and a 46 regenerative doubler working on 28 megacycles, seven

tank of the 53, link coupling should be used. The output of the Siamese may be used to excite a pair of 46's in push-push instead of the single 53, though the output of the Siamese is not really sufficient to drive the grids of the 46 push-pushers to full output at maximum obtainable efficiency. As the two 46's cost almost twice as much as a single 53, it is very doubtful as to whether or not their use is justified when the push-push stage is driven by a Siamese exciter.

STUDY of Fig. 4 will reveal that the Siamese is basically a high-mu triode high-mu triode doubler. The oscillator grid resistor should be either carbon or metallized. and should have a resistance of about 30,000 ohms. If one of the small, sectional wound ohms. If one of the small, sectional wound grid-leak mounting type chokes is used in series with the grid resistor, the resistor may be dropped to around 5,000 ohms with a very slight increase in output. The grid resistor of the doubler section of the Siamese, designated as R3 in Fig. 4, should have a value of between 50,000 and 100,000 ohms, and it also be metallized. There is no advantage in putting an RF choke in series with this resistor. ting an RF choke in series with this resistor. The coupling condenser, C3, may be either a length of twisted hook-up wire, or, better still, a small mica "padding" condenser of the compression type. It is shown as a fixed condenser in the diagram, because when once adjusted it is perser touched again adjusted it is never touched again.

The coils, L1 and L2, are both wound with No. 22 DCC on one-inch forms. L2 is close wound with what is guessed to be more than the required number of turns, and turns are then removed, one at a time, until the circuit goes into oscillation. C3 at this stage of the tuning-up process should be adjusted to a very low value of capacity, and not over 175 volts should be applied to the circuit until all preliminary tuning-up is first accomplished. After the circuit is oscillating, all further tuning of L2 is done by merely spacing the turns on the form. The capacity of the coupling condenser, C3, is gradually increased, and the spacing of the turns adjusted each working properly, the plate voltage may be raised to 275 or 300 volts. There is no object in using higher voltages, because 250 volts on the oscillator is sufficient to fully excite the doubler and also because fairly low voltages are desirable on doubler stages for optimum operation. A doubler stage works best with high bias, lots of excitation, and a fairly low value of load resistance (rather heavily loaded) to favor harmonic generation. And because the efficiency of a doubler is none too high, even at its best, it is impossible to run a doubler at high plate voltages (such as would be desirable for a high-efficiency, neutralized class C stage) and under the afore-mentioned conditions of operation (heavily loaded and excited) without exceeding the dissipation rating of the tube.

The oscillator plate-resonating coil is not critical in adjustment, and if the circuit is tuned-up with a 7250 KC crystal, either a 7000 KC or 7500 KC crystal may be used without adjusting the spacing of the turns of the oscillator coil. Slight readjustment of C1 is the only retuning required.

If the crystal is removed and if the value of R1 is raised to 50,000 or 100,000 ohms, an excellent "cascade doubler", or quadrupler is the result. The 53 then takes the place of two high-mu triode doublers. A midget condenser similar to C1 is advisable across L2 when using it as a "double doubler" to facilitate the tuning process, as it would be necessary to readjust the spacing of the turns on L2. if no condenser is across it, every time a crystal is changed.

Thus the 53 can be used as an oscillatordoubler, a push-push doubler, or a quad-rupler. A larger edition of this tube, pos-sibly with a thoriated filament, would be a SWEET addition to the already overgrown family of tubes on the market. Manufactur-ers gave us the "50 watt" pentode—now let's hope they come out with an overgrown version of the 53!

And, by the way, the 53 makes a fine push-pull final amplifier for a low-power 10-meter rig . . . IF you have a yen for push-pull.

Getting More Out of the FBXA

By C. C. ANDERSON, W6FFP

Some practical suggestions for improving the performance of the receiver and a new wrinkle on an antenna system which has given exceptionally good results.

ANY users of the FBXA have been bothered with Old-Bugaboo Image from high-power commercial stattions. Some of us cannot afford a preselector. The suggestion that a regenerative detector be used to reduce image interference, as well as to increase the sensitivity of the receiver, did not appeal to me. Various other methods were given consideration. The electron-coupled circuit of Lieut. J. B. Dow was finally chosen as the best solution of the problem. It is so simple and so easy to improve the overall performance of the FBXA with a few slight modifications that it behooves all users of this receiver to give thought to the changes which I have made. You will be well rewarded for the time and effort spent in making these improvements in your own FBXA.

Fig. 1 shows the complete FBXA circuit, and the portion surrounded by the dotted lines is where the improvements are to be

made.

The cathode was put above ground potential with respect to RF by the use of a radio frequency choke between the cathode and suppressor grid of the 57, with a variable cathode resistor hooked to the suppressor grid. A variable resistor was added to vary the screen potential. It was beginning to sound like a lot of knobs to twist again, for the ole regeneration control has been a missing motion; in fact it seemed absurd to just sit and copy without having both hands on the receiver, even on a nice crystal signal. But a preselector knob would have been just as bad to my way of thinking. However, that is slightly ahead of the story.

The next thing to do is to mount the resistors. The two switches on the front were very seldom used, in fact the one cutting the plate voltage (SW-2), seemed more than useless, but in this case it was nice to have the hole there. The BFO switch was moved to the rear, it being necessary to drill a hole there for it. This left two nice holes in the front for mounting the two 50,000 ohm variable resistors. The battery switch (SW-2) was taken out of the circuit and a drop of solder substituted for it, thus gaining about seven inches of wire to continue the job. Moving the BFO switch (SW-1) also helped considerably. Now to supply the electron coupling.

erably. Now to supply the electron coupling. It was observed that there was an extra prong on the coils to bring out the tap, but this looked like work to me. Being a normal ham, an easier method was discovered. The band spread tap on the 7 and 14 MC coils was

just the right place to put the cathode tap for electron coupling, and since this tap eventually arrived at the tuning condenser it was placed on the stator of the rear gang. To get it there was slightly puzzling, but National must have foreseen something like this coming up and conveniently provided two holes in the subpanel at the rear of the two gang condenser (Fig. 3) and these holes are within one inch of the cathode lug on the first detector tube socket. By using a stiff wire, insulated with spaghetti, the coupling condenser, .002, was mounted. It was necessary to remove the first detector and first IF tubes from their sockets to put a soldering lug on the stator of the rear condenser. The total amount of work was done in less than an hour, and the results were more than gratify-

properly "terminated" by the impedance of the small indoor antenna. Still being too lazy to put the 20-meter coils in the doublet of the renowned Huber, a brilliant idea occurred . . . to use an RF choke between the antenna and ground posts on the set. This worked like a million. The regeneration was again under control, and the signals jumped-up about ten db. The rig even worked slightly on 7 MC with this indoor antenna, and at this point occurred the peak of my "brilliance." It seems and sounds insane, but it solved my receiving antenna problem. The doublet was lowered, spliced together ... making a 66-foot flat top. A vertical 33-foot section was added with an RF choke hooking the two together (Fig. 4) and the transmission line hooked across the RF choke. This set-

EDITO

tation

teur T

introd

have l

Georg

menta he wi

will b

produ

about ties o

its de

ing th

were ed sli

Tung

cient

ing g

much

rectifi

vanta can b

charg

usual

what

trons

very ode a

is the

the si

the a

be ob

electr

the ti

main neigh


spot fore

can

curre pool,


an el

Th

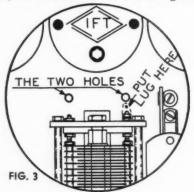


ing. Signal strength doubled, so did the sensitivity, although the ear was the only means of telling this. Signals were heard that were never heard before, and on contact with these signals it was learned that they had always been there, and had called me several times with no result.

But the story does not end here. The revamped receiver was tried out on the 7 MC band. In one of my weaker moments I had built Louis X Hubers' weird tuned doublet receiving system, and had a 7 MC tuned coil up in the air. Being somewhat lazy (I am still a normal ham) I hated to take the antenna down every time I wanted to listen on other bands. An inside antenna was tried, and it seemed impossible to stop the regeneration and squawking of the first detector. Having had considerable experience with "21 circuit balance tests", it seemed only natural to believe that the antenna circuit was not

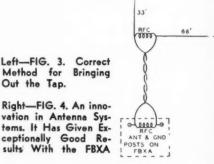

up did wonders, and still does, on all bands; at least it proved to be the best that had ever been tried.

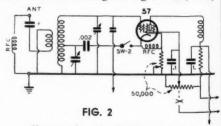The next thing was to try the receiver on 3.5 MC. The regeneration could not be controlled there, nor on 1.7, for the reason that the band spread tap used for the cathode feedback was too far up the coil. It was a case of either making the rig normal, or try



Showing the Actual Changes Made

something else. The easiest way out was to put a switch in series with the electron coupling and cut it off on these two bands. SW-2 was recalled, another hole drilled on the right hand side of the cabinet, and it was so placed. The only precaution necessary is to keep the wires to the switch well separated and in the clear, to cut down the series capacity with the condenser. The variable resistors were enough to cause regeneration on 3.5 and 1.7 MC bands. Aussies and Zedders came in better than they did (Continued on page 32)

12



ince of

ng too doublet

dea ocen the

of my insane. oblem. her .. 33-foot

ooking nission

nis set-

bands; ad ever

ver on

be conon that

athode

was a or try

easiest

switch

lectron off on

-2 was

drilled

of the placed.

neces-

ires to ted and wn the ne con-

resist-

use re-1.7 MC Ledders

ney did

32)

JST

This eration signals work. ntenna.

The Multi-Arc Rectifier

A Self-Starting, 15,000 Volt, 10 Ampere Rectifier, Developed by a Radio Amateur. Air Cooled ... 10 Inches High ... Silent in Operation. It Solves Many of the Problems of High-Voltage Rectification.

By GEORGE A. BECKER*

EDITOR'S NOTE—The Multi-Arc is a new adaptation of an old principle. It is another of amateur radio's contributions to the art, and its introduction will be welcomed by many who have long sought the solution to high power rectification at low cost. The inventor, Mr. George A. Becker, here presents the fundamental principles of the Arc. In the next issue he will tell you how to use this new tube in amateur transmitter power supplies. The Arc will be ready for the market within 30 days; production is already under way.

HE Mercury Arc Rectifier is a natural outgrowth of the invention of the Mer-Vapor Lamp by Peter Cooper-Hewitt about 35 years ago. The rectifying properties of the Vapor Lamp, discovered early in its development, were expanded rapidly during the next few years and by 1905 Rectifiers were produced which have only been improved slightly in all the intervening years.

The Mercury Arc takes its place between Tungar Bulbs and Kenotrons, being less effi-

cient than Tungars at low voltages, but offering good efficiency from about 100 volts to 5000 or 6000 volts output. Kenotrons follow, up to 200 KV or better, although as much as 40,000 volts has been successfully rectified by Mercury Arcs. Their chief advantage lies in the amount of current that can be rectified, even in small size Rectifiers. Due to the neutralization of the space charge effect of the electrons by the positive mercury ions of the mercury vapor, the voltage drop through the tube is very low, usually around 15 or 20 volts. It varies somewhat with the design of the tubes. The eleccient than Tungars at low voltages, but offer-

what with the design of the tubes. trons in the first place, are produced in a very unique manner from the mercury cathode and originate in the Cathode Spot, which is the bright spot that "skitters around" over the surface of the mercury pool.

This spot is maintained by the passage of the arc current itself and there seems to be

no limit to the number of electrons that can be obtained. Since this spot is the source of electrons that can be obtained. Since this spot is the source of electrons there can be no current through the tube until the spot is established. Once established, however, the current flow will maintain it, provided the current is in the neighborhood of 3 or 4 amps. If the current is interrupted, even for a split second, the spot goes out and must be re-established before the tube will again operate. The spot fore the tube will again operate. The spot can be established by breaking a separate current circuit at the surface of the mercury pool, either by rocking the tube or moving an electrode in the tube so as to break conthe Cathode Spot. We see, therefore, that there must always

tact with the mercury surface, thus creating


a small arc which immediately develops into

be a current flowing through the tube in or-der to maintain the spot. This means that there must be more than one Anode, so that one is always carrying current while the others are idle.

This explains the fundamental difference between Mercury Arc Rectifiers and Tungars

filament consumption of Hot Cathode Type Rectifiers.

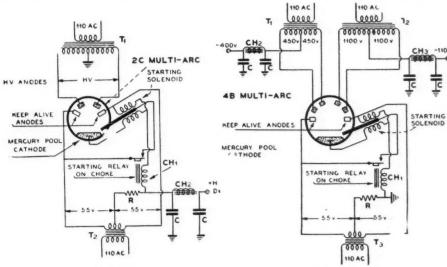Since we can have any number of Anodes, and since they will not interfere with each other, it follows that we can use one tube for rectifying several different sources of AC simultaneously. Of course, the Mercury Cathode is the COMMON POSITIVE connection of all the supplies, but the NEGA-TIVES are distinct and separate terminals. In addition we can secure multi-phase recti-



2C MULTI-ARC

4B MULTI-ARC

or Kenotrons. First, there is no filament or heated cathode to supply the electrons, since they are obtained from the Cathode Spot on the Mercury Pool and, second, more than one Anode is necessary; third, there is no limit to the number of Anodes that can be used inside the same bulb.

They do not interfere with each other in any way. A space-charge of positive ions builds up around a negative electrode and effectively shields it.

Since a current of about 3 or 4 amps must

always flow through a Mercury Arc to maintain the Cathode Spot, a natural addition to lightly loaded or intermittently operated tubes is a pair of small Anodes operating at low voltage and carrying enough current to maintain the spot. This current flows in an impedance circuit and is wasted. Its sole pur-pose is to maintain the spot when the other Anodes are idle or when they are carrying less than 3 or 4 amps.

This represents a loss of efficiency, but the wasted power can be held down to about 150 watts, which is not much greater than the fication by the same process. This will be described more fully in a later article.

Summing up the advantages of the Mercury Arc Rectifier for amateurs we have:

First-No filament to burn out or lose its emission, therefore extremely long life at top efficiency.
Second—Good rectification right in the

range desired by amateurs, without cumbersome or expensive equipment.

Third—Large current capacity; no such thing as overloading in amateur circuits.

Fourth—Several separate power supplies can be rectified in ONE TUBE, simultaneous-

ly.
Fifth—Multi-phase Rectification in ONE
TUBE, resulting in better DC with less ripple to filter.

Sixth-Simple circuits with common garden variety equipment.

In the next issue the details of this new adaptation of an old system will be fully described—with the information on the new Multi-Arc Tube that opened this field to the

* EX-6BIP, 2445 Telegraph Ave., Oakland, Calif.

RADIO FOR AUGUST

The Velocity Microphone

By D. B. McGOWN, Technical Editor

THE ribbon or velocity microphone is one of the most desirable types of audio pick-up devices available at the present Ordinary diaphragm microphones such time. as the condenser type are almost non-directional, and as a result they are sensitive to sounds coming from all directions; thus all extraneous noises and sounds will be heard as well as the sound it is desired to pick up. The ribbon microphone has a marked directional effect, and while this is a disadvantage for some types of work, if this property is used to advantage it will result in very desirable operating features under proper conditions. The directional characteristic of a ribbon microphone permits its use in rooms or enclosures with poor acoustics, because the ribbon may be placed so that the reverberation coming from the side walls may be reduced by proper microphone placement. The ribbon microphone has very good frequency characteristics and is capable of high-quality speech reproduction. It is a low impedance device which permits it to be located at almost any convenient distance from the pre-amplifier. It is simple and easy to build and is relatively inexpensive; there are no close tolerances in its construction and it lends itself well to the amateur builder. There are no difficult parts to obtain, and when damaged it can be quite easily repaired. It is rugged and sturdy, is not easily damaged by shock or jar; in fact, it is probably less damaged by rough handling than any type of microphone. On the other hand, it is a more difficult microphone to handle when used outdoors, especially if the wind pressure is strong. A heavy "wind gag" or a thin cloth "ball-shaped" wind shield will prevent such trouble. Its output level is very low and it requires considerable pre-amplification in order to bring it up to a satisfactory operating level. It sometimes exaggerates the low frequencies. The low impedance of the ribbon makes it difficult to obtain a proper impedance match between the ribbon and the pre-amplifier, or coupling transformer. coupling transformer requires exceptional shielding to prevent troublesome pick-up due to stray magnetic fields, such as nearby AC lines, etc., which would introduce considerable objectionable noise.

Principles of Operation

THE principle of the ribbon microphone is very old, and is also very simple; the operation depends on the electrical law that a conductor moving in a magnetic field has an electromotive force induced in it by its action in cutting the magnetic lines of force in the field. The magnitude of the electromotive force thus produced is equal to the rate of change of the flux through the circuit. This is exactly the same action that makes possible the operation of electrical generators and other similar devices. Obviously, the higher the flux the greater the current generated, and therefore it is desirable that a high flux be available in the ribbon microphone, through which the ribbon may move. Furthermore, because the actual movement of the ribbon is small, the higher the flux the more current will be supplied to the output.

Construction

RIBBON microphone can be made by taking a thin aluminum alloy ribbon (duralumin) about a half mil. in thickness, .00035 to .0005 inch, and about Ar-in. wide. The ribbon is then corrugated by run-

ning it through a pair of gears, about 10 to 16 teeth per inch, the entire ribbon strip being about 21/2-in. long. The ribbon is suspended between the pole pieces of a powerful magnet. This may be in the form of an electro-magnet or a permanent magnet. Fig. 1 shows the general construction. The permanent magnet from an old magneto may be picked up in almost any automobile wrecker's place for a small sum. If the magnet is weak it can be re-magnetized at a magneto service station. These magnets usually have holes drilled in their sides, and this makes the rest of the unit easy to mount. The soft iron pole pieces should be made of soft Norway iron, but it is sometimes hard to obtain

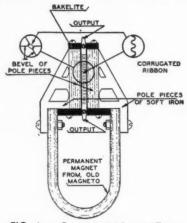


FIG. I—Permanent Magnet Type

and difficult to handle. Quite satisfactory results can be obtained if soft cast iron is used instead. It is easy to make a small wooden pattern for this work, which can be cast at any foundry, and if the pattern is carefully



FIG. 2—Showing Palor Response of Microphone

made the finishing can be done with a file and emery cloth, thus avoiding machine work. An electro magnet may also be used (see Fig. 2), where the general arrangement is the same. Field excitation must be pure, unvarying direct current; otherwise every change in the supply will be heard in the speech output. Battery supply is best, although well-filtered rectified AC is sometimes satisfactory. Commercial direct current is entirely satisfactory, provided a good filter is used, as shown in Fig. 4. The commercial supply is not always free from commutator ripples, etc. A very good supply would be well filtered DC obtained from a 25Z5 or similar tube, for which no transformer would be necessary, and which would give plenty of current for the purpose.

The Ribbon

THE aluminum ribbon must be floated between the poles at very low tension, so that the frequency of the ribbon is below audible range. Generally the ribbon will hang slightly "limp", but care should be taken that it does not hang too freely. It should hang in such a position that it will

vibrate easily when breathed upon very gently, with the mouth well opened, the speaker's lips being about a foot from the ribbon. The ends of the ribbon should be screwed to bakelite or rubber insulating blocks, and small metal plates should be provided between the screw and the bakelite to hold the ribbon in place. The screws pass through the plate, ribbon and bakelite. These screws also serve as the output terminals for the speech currents to the output transformer.

In some types of ribbon microphones it will be found that holes are pierced in the poles pieces, as shown in Fig. 2. The reason for this is that these pole pieces act as a baffle, similar to the baffle on a dynamic cone loudspeaker, and the shorter the path between the front and the back, the higher the frequency response. This distance should be about 1/2, the wavelength of the highest frequency. If the frequency is 15,000 cycles, it will be desirable to have this distance about .44 inches, which is a half wavelength at 15,000 cycles. In ordinary work, this extreme high frequency response is hardly necessary, and it is usually not necessary to pierce the poles.

not necessary to pierce the poles.

Since the impedance of the ribbon is very low, usually from 0.2 to 0.5 ohms, it is very easy to insulate the ribbon, and stray moisture or temperature changes will have no effect on the ribbon. It makes it quite difficult, however, to match this impedance with a proper transformer. Transformers can be obtained commercially which will give a proper im-

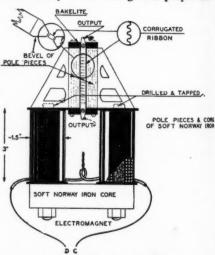


FIG. 3-Electro-Magnetic Type

The cores are 11/2 by 3 inches, with following windings: 6 v. DC, No. 19 enameled wire. 12 v. DC, No. 22 enameled wire. 110 v. DC, No. 35 enameled wire. 220 v. DC, No. 38 enameled wire

pedance match and it is usually better practice to use transformers with output impedances of 200 or 500 ohms, which can then be fed into a line, or, if desired, into another transformer which serves as the input of the preamplifier. Transformers are available which will match directly from the ribbon to the grid of the tube, and either type, in several popular makes, can be obtained from any supply house.

Response

THE response of the ribbon microphone will cover the entire audio frequency range, up to about 15,000 cycles. Usually there is a slight loss at the high frequencies, starting at about 1500 to 2000 cycles, and

average
This cordirectly
a reason
enough
practical
bon. V
close to

istics ch

distance

conside

distance

graduall

not be
a perso
public a
For a
objectic
can be
filter w
in comm
too-flat
pre-amj
about t
for rep
for this

Pre-Ar

quired.
about
of 6 m
about
then g
pad, or
ously,
put tra
ance of
Heat
a preated,
former
simple

power filter,

perime

substit


FIG. 5

or iro
tance
will b
An
phone
the in
pedan
throug
of the
first t
possib

first to possible the methat to from and eva fert prope

RA

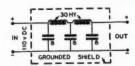gradually dropping until at 15,000 cycles the average microphone is down about 6 d.b. This condition is with the sound coming from directly in front of the microphone, and from a reasonable distance, the distance being great enough so that the sound waves present a practically uniform or "flat" field to the ribbon. When the microphone is moved up close to the source, the frequency character-



-Filter for DC Field Supply

istics change considerably. See Fig. 5. At 1-foot distance the low frequency response increases considerably, and decreases rapidly as the distance is increased. The microphone should not be placed closer than about three feet to a person who is singing or speaking, as in public address work.

public address work.

For amateur use this is not a very serious objection, and the low frequency response can be eliminated by using a "high pass" filter with about 100 cycle cut-off, as is done in commercial microphones, or by using not-too-flat audio frequency transformers for the pre-amplifier. The cheaper types cut off at about this frequency. The common types sold for replacement in broadcast sets are suitable for this purpose. for this purpose.

Pre-Amplifier

gently, beaker's

n. The o bake-l small

een the

bon in

plate,

o serve urrents

s it will

e poles for this

similar peaker, e front ncy reout ½

inches, cycles.

quency

usually

is very Oisture

ffect on

proper brained

er im-

PPED

llowing o. 12 v. No. 35

ed wire

ractice dances

be fed trans-

ne prewhich he grid opular house.

phone quency

s, and

ST

PRE-AMPLIFIER is absolutely necessary with the ribbon microphone, and essary with the ribbon microphone, and usually about two stages will be required. The output of the microphone is about 70 to 100 d.b. below a reference level of 6 milliwatts, and the output should be about minus 30 to 40 d.b. The output can then go to either a mixer, a volume control pad, or directly into the final amplifier. Obviously, the pre-amplifier should have an output transformer which matches the impedance of the final amplifier, 200 or 500 ohms. Heater type tubes are best to use for such a pre-amplifier. They can be battery oper-

Heater type tubes are best to use for such a pre-amplifier. They can be battery operated, or operated from a step-down transformer. Battery operation is easier and simpler, and is by all means advised in experimental set-ups. AC operation can be substituted later. The plate supply for such an amplifier should be well filtered and shielded. It is good practice to mount the power supply, including the rectifier and filter, and filament heater supply in a steel


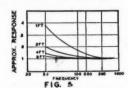



FIG. 5—Response at Various Distances from in Front (or back) of Microphone

or iron shielded box, and place it some dis-tance from the pre-amplifier, so that there will be no stray fields to set up hum. An amplifier suitable for a ribbon micro-

An amplifier suitable for a ribbon microphone is shown in the diagram, Fig. 6. Here the input is led from the ribbon to an impedance matching transformer, and thence through a 200 or 500 ohm line to the input of the pre-amplifier. It is best to mount the first transformer as close to the ribbon as possible, even mounting it in the bottom of the microphone itself. It is very important that this transformer is very well shielded from magnetic fields, such as from AC lines and equipment. This transformer will prove a fertile source of bad AC hum if it is not properly shielded and a ground connection

placed on the shield. Sometimes a separate ground, used for no other purpose, leading direct to a ground rod or plate, may prove desirable to remove all trace of hum from this unit. The input of the pre-amplifier should also be well shielded, but generally this can cause this brings it rather close to the speaker. Mountings should be rigid and sturdy, and at the same time arranged so that vibration and shock are not transmitted through them. Padding with felt or soft rubber shock-proof pads or mounts will prove beneficial.

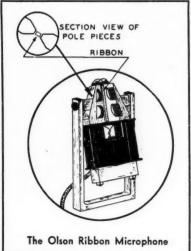

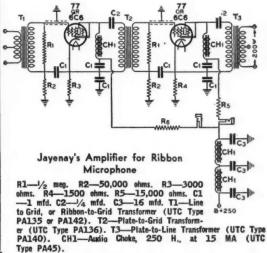

C1—1/2 mfd. C2—1/4 mfd. R1—50,000 ohms. R2—500,000 ahms. R3—5000 ohms. R4—30,000 ohms. R5—15,000 ahms. T1—Mike-to-Line Transformer (UTC Type PA143). T2—Line-to-Grid Transformer (UTC Type PA135). T3—Interstage Transformer (UTC Type PA133). T4—Plate-to-Line Transformer (UTC Type PA140).

FIG. 6. Ribbon Microphone Amplifier

be mounted in, and as a part of the pre-amplifier, and grounded to the common chassis.

77 type tubes were selected for the pre-amplifier. The shields and screens of these tubes were connected to the plate. This methods od of connection results in the use of the 77 as a triode. It gave very satisfactory results and the tube is non-microphonic. The pre-amplifier case should be built of sheet steel or aluminum. It is better to make it rather generous in size, so that the parts can be reasonably well spaced. There is a distinct reduction in the probable hum content if the chassis is kept at least an inch away from all

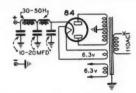


FIG. 7-Power Supply for Pre-Amplifier

parts. Ventilation may be desirable in the case of long continued use, and holes can be drilled or punched at suitable places in the chassis.

The mounting of the microphone and the amplifier is left to the individual builder. It amplifier is left to the individual builder. It is difficult to offer suggestions that will be of help, because individual problems differ so greatly. The microphone can be mounted either with the ribbon at the top or at the bottom, the first corresponding to a desk or floor stand type mounting, and the other to a suspension hanger. The microphone may also be hung from a counter-balanced cord and weight system. Owing to the rather great weight, it is inadvisable to try to hold the microphone in the hand while using it, be-

VP5PZ Honored


IT IS a pleasure to present a photograph of our old friend, John Grinan, VP5PZ, and two of his associates. This is not an ordinary photograph of a social ham gathering, but something a great deal more serious and dignified. Mr. Grinan has been honored with an appointment on the new Wireless Board of Jamaica. The duties of this board are to formulate new laws and regulations and to give examinations to ascertain the qualifications of candidates applying for Wireless Operators' certificates. General approval of the selection of the board has been expressed by prominent members of the wireless world in Jamacia and elsewhere, on account of the long and varied experience of the members; a better selection could hardly have been made.

Congratulations, John! Again, an amateur is appointed to a position of dignity and responsibility in the Governmental field!



NEW WIRELESS BOARD

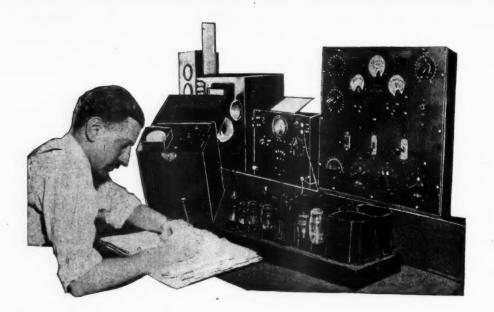(Center): Mr. T. J. Guilfoyle, chairman, Government Wireless Telegraph Inspector;; (left): Mr. J. F. Grinan, member Institute of Radio Engineers, (right): Mr. Edward Mockett, Chief Wireless Engineer, Direct West India Cable Co. in Jamaica.



A 38 Watt PA Amplifier Using '45 Tubes

By I. A. MITCHELL

Chief Engineer, United Transformer Corp.

THE WRITER'S article in the April issue of "RADIO" showed that 15 watts power could be obtained from low power tubes like the 42. A number of requests were received by the writer to indicate what could be done with other tubes in the same line. The information given below was obtained after considerable research on the characteristics of the 45 tube under various conditions of operation.

Due to its excellent fidelity and low harmonic content, the 45 tube has been very popular in both the radio and PA fields for many years, where low power was required. However, few people realize that properly used in push pull connection, a pair of these tubes can deliver from 12 to 19 watts with only 5% distortion and operating with only 275 volts on the plate. While some attempts were made in the past to increase the power output from 45 tubes, the tubes were invariably operated above the manufacturers maximum plate voltage rating (275 volts), so that the tube life was appreciably shortened

For public address work, an all-around amplifier should have a power output over 25 watts. While many class B amplifiers are available with this rating, the high harmonic distortion inherent with class B tubes at high and low levels is often objectionable. The past year has shown a marked increase in PA competition, and a corresponding increase in the demand for quality by the ultimate user of PA systems. Many men who were accustomed to taking a large number of jobs at low prices are now beginning to realize that a few jobs with quality equipment will bring the same amount of income.

ment will bring the same amount of income.

The word "quality" in audio amplifiers can be covered by four major points insofar as the ear is concerned. These are low frequency discrimination, low harmonic distortion, ample power-handling ability, and low hum level. The first of these qualities is controlled almost entirely by the transformers used in the amplifier. Good transformers are available; one grade on the market today having a response from 30 to 15,000 cycles. The second factor, harmonic distortion, is in-

herent in the amplifier construction, and also in the transformers used. Proper bias should be maintained on all the tubes, and transformers with negligible saturation are required.

T IS FOOLISH to make a general statement such that an amplifier has 20 watts power output. In many cases the less reputable amplifier manufacturer rates his power output in watts at the maximum saturated output. An amplifier rated at 20 watts in this way would probably be throttled down to 10 watts in use, so that the harmonics would not be objectionable.

Everything considered, anyone who has worked with vacuum tubes realizes that there is nothing superior to class A tube operation for low harmonic content. Class A prime has this same characteristic of low harmonic content plus high power output. The 45 tube lends itself very well to A prime operation. Using 275 volts on the plates and 56 volts self bias, a pair of tubes in push pull will deliver 13 watts with 5% harmonic content. Using the same plate voltage and 70 volts

fixed bias, 19 watts can be obtained with 5% distortion. This should be bright news to those of you who want to revamp your old 45 jobs. It should be noted, however, that some power is required to drive the 45 tubes and that the input and output transformers must be special. 56 tubes in pushpull make a perfect driver. The input transformer is the same whether fixed or self bias is used, and has a slight stepdown ratio. The United Transformer Corp. has made available a type UA233 transformer for this purpose. If self bias is used, the plate to plate load should be 6000 ohms (the same as that for class B 46's). If fixed bias is used, the plate to plate load should be 3500 ohms. A special output type PA245 has also been released for these tubes. Figs. 1 and 2 show self and fixed bias circuits for a pair of 45's used in this manner.

consider

bilize

double up. grids pull. ample again input

be cu is als exact

ances

dle !

the o

recti

first

supp

effici

capa

first

qual

of t

spor

T

term

also

imp

mus

arti

azoi

WOL


arti

pub

cath

tub

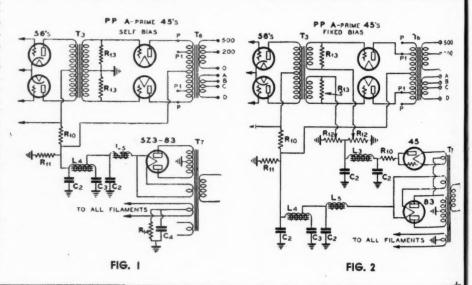Inasmuch as the 45 tube is quite inexpensive, the use of four tubes in push pull parallel becomes quite logical. Examining the above data we find that four tubes will



give us with fixed bias 38 watts, and with self bias 26 watts. These power outputs considering the non-objectionable harmonic content of 5 to 7 per cent are ideal for the medium and large PA job.

IG 3 ILLUSTRATES the schematic circuit diagram of a three-stage triple pushpull amplifier using self bias and having apower output of 26 watts. The unusual sim-plicity of construction and wiring is apparthe entire circuit. Resistors R3 and R4 stabilize the four 45's excellently. The input transformer has primary terminations to match 50, 200, or 500 ohm lines, single or double button mike, or low impedance pickup. This transformer is coupled to the two grids of the 57 tube triode connected in push grids of the 57 tube triode connected in push pull. The 57 tubes have the unusually good amplification factor of 20. These tubes are again transformer coupled to the 56's. The input transformer from the 56's to the four 43's is of a special type designed specifically for the purpose. If a transformer of standard nature is used, the normal power output may be cut 80 per cent. The output transformer is also somewhat critical and should be the exact impedance to match the tubes. The transformer shown has two primary imped-ances, so that it can be used with four 45's having either fixed or self bias. If fixed bias is available the lower primary impedance should be used. This transformer will handle 50-watt peaks. If fixed bias is desired, the output circuit is Fig. 4 should be used. Here the filament center tap is grounded and the bias obtained through a secretar 45 tube. the bias obtained through a separate 45 tube rectifier, as described in April "RADIO."

es

with 5% news to

your old ver, that

the 45

ut trans-

in push-

ut trans-

or self

down ra-

has made for this

plate to

same as

is used,

00 ohms.

Iso been 2 show

r of 45's

te inex

ush pull

amining

bes will

A A

UST

THE HUM LEVEL is maintained negligible through good filtering. The output tubes obtain their voltage after the first choke and condenser, so that the plate supply regulation is good. Following this a tuned filter is used having extremely high efficiency. This is augmented by a resistancecapacitance filter in the plate circuit of the first stage. Push pull tube operation has two great advantages in producing high audio quality. The direct current is balanced out of the transformers, allowing good low response, and both filament and plate hums are neutralized.

The output trnsformer from the 45's has terminations for a 200 or 500 ohm line and also for up to 20 voice coils. The voice coil impedances are 1.5, 3, 5, 8, 16 ohms. The

R4 FIG. 3 CONSTANTS R1—15,000 ohm, 5 watt; R2—1350 ohm, 5 watt; R3—100,000 ohm, 1 watt; R4—2500 ohm, 1 watt; R5—30,000 ohm, 5 watt; R6—400 ohm, 25 watt; R7—2000 ohm, 10 watt; R8—100,000 ohm variable, 10 watt; R10—10,000 ohm, 5 watt; R11—40,000 ohm, 5 watt; R12—20,000 ohm variable, 10 watt; R13—250,000 ohm, 1 watt; R14—775 ohm, 20 watt.

1—1 mfd. 200 v.; C2—8 mfd. 500 v. electrolytic; -1 mfd. 500 v. electrolytic; C4—25 mfd. 100 v. elec-

C3—1 mfd. 500 v. electrolytic; C4—29 mfd. 100 v. electrolytic.

T1—UTC Type 135 Transformer. T2—UTC Type 133

Transformer. T3—UTC Type 233 Transformer. T4—UTC

Type 445 Transformer. T5—UTC Type 425 Transformer.

T6—UTC Type PA-245. T7—UTC Type PA-22.

L1—UTC Type 102. L2—UTC Type 103. L3—UTC

Type 45. L4—UTC Type PA-100. L5—UTC Type PA-101.

plate to plate load impedance for push pull parallel 45's A prime self bias is 3000 ohms; for fixed bias 1750 ohms.

If we summarize the actual important fac-tors in this amplifier, they may be noted as

High gain—90 db. suitable for all PA applications.


Low distortion-less than 5 per cent at ALL levels below 26 watts self bias or 38 watts fixed bias.

True class A prime operation

High power output.
Plate supply having good regulation. Low hum level.

Unusual simplicity of construction. Inexpensive tubes, and economical op-eration, low cost of components.

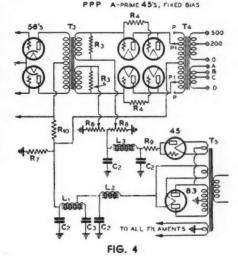All in all, it is apparent that the 45 tubes in A prime lend themselves very well to the construction of a high quality PA amplifier. With proper precautions in the amplifier construction and the choice of good trans-



formers, together with quiet resistors and non-leaky condensers, an amplifier of this type will be found foolproof for any PA

Special output transformers are also available now for use with two or four 45's in A prime for modulation purposes. These tre types PA201 and PA401, respectively.

Cathode Ray Tube Theory

article in which we hope to describe our sawtooth sweep oscillator. For the many who must certainly be confused by some of the articles on the interpretation of the trapazoidal figures obtained by connecting one set of plates to the modulating carrier and the other set to the modulating voltage, we would like to offer a suggestion. A good article, with appropriate illustrations, was published in "RADIO" for October, 1933. It is felt that since this article was so far in advance of the advent of popular priced cathode ray tubes, it may have well been overlooked. If so, the fifteen illustrations will interpret almost all of the possible troubles that may arise. It is regrettable that no back copies of this issue are available but if demand warrants we may re-print it at some future date.

To recapitulate, one of the most important considerations in designing a "Scope" is to avoid stray fields and pick-up. Be certain that the transformers are out of the field of the tube and mount them, preferably, in or on the rear of the housing. Use an iron or steel, non-magnetic shield around the cathode ray tube. By all means, keep the outfit away from the transmitter when measuring modulation. Determine carefully the correct value of bleeder and filter condenser to avoid disastrous ripple. Ground the metal case of the instrument with a good external ground. It is also good practice to provide some type of filter in the 110 input. This condenser can be a .01 mica from either side of the line to ground. Avoid allowing a bright spot to remain in one place on the face of the tube for any length of time, in order to prevent destruction of the fluorescent material on the

It is our hope that this paper will prove of some value to those who desire a more complete understanding of the theory and operation of cathode ray tubes. Those desiring additional information are referred to an excellent series on the subject by Arthur H. Halloran, a noted authority, whose articles appeared in several issues of "RADIO" last The application bulletins of RCA RADIOTRON are particularly fine and cover special phases in a thorough manner. The bulletins published by Allen B. Dumont Laboratories are also highly informative.

There can be no doubt that the introduction of the type 906 has opened an entirely new field for the amateur. "Thanks, Mr. RCA."

(Continued from page 9) CALLS HEARD AT WICNU STAMFORD, CONN.

June 17 to July 15—20 Meters

G2DI, G2DL, G2DV, G2GF, G2IM, G2KI, G2KT, G2KZ, G2MA, G2OD, G2PN, G2QH, G2XA, G2XU, G2ZJ, G5BD, G5CH, G5JU, G5LB, G5MQ, G5NF. G5NI, G5QA, G5QU, G5QY, G5SR, G5UF, G5VM, G5WY, G5YH. Heard on fone: G5CV. Heard on fone and CW: G5BJ, G6DL, G6HB, G6IB, G6JG, G6JU, G6KI, G6LI, G6LK, G6NJ, G6PY. G6QC, G6QX, G6UF, G6US, G6VP, G6WM, G15QX, F8GG, F8JJ, F8RJ, FM8BG, D4BCK, D4BGT, D4BHH, D4BIU, D4BKK, D4BTU, EA2AD, EA3EG, EA4AV, EA5BD, PA0AZ, PA0CE, PA0HM, PA0LL, PA0QL, PA0XF, PA0XG, PY1AW, PY5AD, HB9AQ, HB9Y, HC1FG (fone), IITKM, LY1J, LU1EP, OE1FH, OZ4LM, VOSZ, VP2GP, VP5JB, VP5PZ, VU2BQ, maybe this is a foney as he was R7 RAC at 6 p.m. EST on about 14375 KC. OA4Z, K5AA, K5AF, K5AZ, K6GUA. X1H. Heard on fone: X1G.

Conditions very poor here this month and the noise level higher than usual. I understand the boys from down under are coming through on 20 from about 11 p.m. EST on. Heard one Saturday night 7-14 at about 12 midnight about R2 VK3HM, not quite sure if the H was an H or an S. Will be on 14376 every Saturday night from 11 p.m. EST till 1 a.m. EST trying to hook VK and ZL.

3 Tube 15 to 200 Meter Receiver With R. F. Amplifier Stage

By E. M. SARGENT

A Discussion of Layout and Circuit Problems, and Helpful Hints for Builders of One of the Most Popular Circuits Used for Short Waves

ESPITE THE large number of short wave superheterodynes that are in use, a great many amateurs and fans still prefer the smaller receivers. The most popular combinations is undoubtedly the 3-tube circuit which employs one stage of tuned RF, regenerative detector and one stage of audio. This layout, properly built, is highly efficient, flexible, quiet, and last, but by no means least, it is inexpensive. Receivers of this type are remarkably efficient, and when adjusted correctly have a very high sensitivity level, especially for CW reception.

length to which the detector is tuned is the wavelength that will be received. The closer the RF stage can be brought into resonance with the detector the louder will be the signal and the more sensitive the set. Suppose, however, that in a receiver wired as in Fig. 1, with a 2-gang condenser to tune the RF stage and detector and an RF stage trimmer, some interaction is present. We will assume that it is desired to tune in a certain station, KDKA, for example, on 49 meters. The 2-gang tuning condenser is rotated until

"ground" and that it makes no difference where this connection is made. This is far from fact. The word "circuit" implies a complete ring, or circle. A DC circuit, as everyone knows, must be a complete, uninterrupted conductor of electricity, and if part of it runs through the ground, the ground is always taken into consideration as being a part of the circuit. A radio frequency circuit must therefore be considered as a complete circle through which the current oscillates, instead of flowing in a single direction.

poses all path. As

per cent quency. We th ground

denser i

riving a

lesser as

of the f

trace th

rent is

starting

current

via the

the rea

denser agonall

the cha

the coi

starting

tenden whether a piece. Therefore be four we are the dedetectoring rein a coolly of this of Enough seed of the tendent the ten

her in

Surpri

vious

ing at

of cit

canno

from

groun

detec

most

stage

the c


long

Abo

cated.



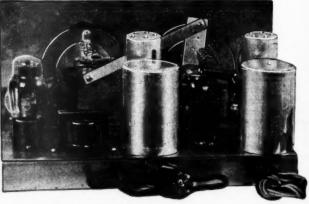Front panel view of Sargent 3 tube R.F. receiver with stage of R.F.
Amplification



Rear view, showing mechanical band-spreader and 3 inch coil shield cans

In reviewing this type of circuit, it is necessary for the sake of clarity to refer to a specific receiver and circuit. For this purpose the 3-tube "AMATEUR SPECIAL," designed by the writer, is here illustrated and the circuit wiring reproduced. However, the considerations apply to any receiver of this general style, and the intent of this article is to give practical hints to those who own, or those who contemplate building one.

NE OF THE most important considerations in the layout and wiring of a receiver of this kind is to make provision for complete isolation between the RF stage and the regenerative detector. Even a small amount of interaction is very undesirable. A regenerative detector, in itself is a none-too-satble proposition. Add to this an RF stage which affects both the regeneration and the tuning adjustment of the detector, and an electrical engineer will be needed to operate it. In addition to complicating the operation, interaction also makes is practically impossible to log the receiver. It is therefore highly important that interaction be reduced to a minimum.

action be reduced to a minimum.

Fortunately, with a little care, it is not difficult to do this. Interaction is caused by coupling between exposed parts of the detector and RF circuits. This coupling usually takes place between coils, variable condenser stators, and grid or plate leads. However, it can also occur in the heater wiring, power supply, or even in the shielding if it is not properly designed. The ideal receiver would have coupling only in the one-way action of the RF amplifier tube to the detector, and there would be no reverse coupling of any kind. In the normal operation of the receiver, the detector, because of its regeneration, is the controlling circuit, and the wave-

KDKA is heard. Then, to get maximum sensitivity and best signal, the RF trimmer must be adjusted. This trimmer adjustment, be-cause of the interaction, detunes the detector circuit. The detector controls the wavelength that is received, and when detuned in this way cuts out the signal. Then the main tuning condenser must be readjusted to bring the signal in again, the trimmer must be readjusted, and the whole process repeated a number of times until the loudest signal is obtained. With present-day knowledge of circuit design this complication is no longer necessary. If there is no interaction, the adjustment of the RF trimmer will have practically no effect on the detector adjustment. Thus, as the detector is the controlling circuit in the tuning, a single adjustment of the tuning condenser will suffice, after which the RF trimmer may be adjusted for maximum volume without changing the wavelength of the entire receiver.

The most troublesome medium of intercoupling is the power supply, particularly if it is of the rectified AC variety. This type of power supply, which is in general use, has a high impedance which has a tendency to couple all circuits that are fed from it. Perhaps the only way to prevent the power supply from coupling the receiver circuits is to use large isolation resistors in all screen and plate leads to the RF and detector tubes. They must then be bypassed by a fairly large condenser to a single-point ground for each set of circuits.

"Single-Point" Ground

ANY EXPERIMENTERS are careless when it comes to the grounding of circuits, the impression prevailing that any connection to the chassis is a

Before reading further, look at the illustration that shows the rear view of the receiver, and note the relative positions of the two coil shields, tube shields, and the 2-gang tuning condenser. The coil and tube to the extreme right are part of the RF stage, while those in the center are the detector circuit. Suppose that in hooking up the parts, the careless method of grounding is used. To do this we will put a grounding lug for the coils under the rear of each coil shield. We will also place a grounding lug under each tube socket for circuits that can be conveniently grounded at these points, and we will let the condenser take care of itself, with both sections going to ground through the rotor shaft to the front panel. Now look at the wiring diagram, and see the possibili-ties. Disregarding the antenna, which may be a doublet and therefore not grounded, the first circuit with which we are concerned is the input to the RF stage. This circuit con-sists of the secondary of the RF coil, the tuning condenser, the trimmer, and the grid and cathode of the 58. For simplicity, consider the current flow for half a cycle only, and follow the circuit as if it were DC. Start with the top of the secondary coil. Leaving this point the current flows into the stators of the tuning condenser, thence to ground, also to the grid of the tube. Continuing, it leaves the tube via the cathode and there it will divide into two branches, depending upon the iimpedance ratio of the two. Part it will go through the cathode resistor and the variable 10,000-ohm resistor to ground. The rest will flow to ground through the .01 mfd. by-pass condenser. If a good, noninductive by-pass is used, the impedance at 30 meters will be less than 2 ohms, as against 400 through the resistor,

18

we may assume that for practical pur-poses all of the current goes the condenser path. As a matter of fact, one-half of one per cent goes through the resistor at this fre-

We therefore have the current arriving at gound at the point at which the .01 condenser is grounded, which we will say is at the tube socket. We have more current arriving at ground through the tuning condenser rotor shaft to the front panel, and a lesser amount, depending on the ratio of the runing and trimmer capacities, at the center of the front panel where the trimmer is located. To complete the circuit, we must trace the radio frequency paths that this current is likely to follow in returning to the starting point at the top of the RF coil. The current from the .01 by-pass will go back via the chassis to the coil grounding lug at the rear. The current from the tuning condenser and trimmer will probably run diagonally down the panel, then flow across the chassis back to the grounding lug for the coil, then up through the coil to the starting point.

fference

is far

plies a

cuit, as

te, un-

id, the

tion as

quency

a com t oscil-

ection.

d can

illus-

of the

-gang o the while

rcuit.

the To

We

each

contself,

ough

look

ibili-

may the

d is

congrid

con-

only,

ving

tors

und,

g, it

ling

Part

stor

und

im-

If


OW COMES a very important point. Nadio frequency current does not take the most direct path. It has a tendency to spread, to follow the outside, whether it is flowing through a wire or over a piece of flat metal, such as a chassis. Therefore these currents will spread and will be found at all parts of the chassis. Suppose we are equally careless with the wiring of the detector circuit. We then have RF and detector circuit currents spread over the encetector circuit currents spread over the en-tire receiving set. There is a resistance drop in a chassis the same as in a piece of wire, only more so. The voltage built up across this resistance is a COUPLING voltage. Enough of that. If you get the point, the seed has been planted. Look over some of the sets you are using, make the changes her indicated, and get ready for some real surprises!

Reurning to the 3-tube set, it is now obvious that we should do all of our prounding at a single point, at least for a given set of circuits. In the case of the RF stage we cannot quite do this, because unless we go to unnecessary bother to insulate the trimmer from the panel we will have at least two grounding points at the panel. The rear section of the gang condenser is used for the detector and the front for the RF stage. The most practical arrangement is to run all RF stage grounds to a lug where the panel joins the chassis, right under the condenser shaft. The detector leads can go to a lug at the rear of the tuning condenser. Circuits belonging to the RF stage should also include the plate of the 58, and its return by-pass.

Above chassis layout, showing proper placing and spacing of essential parts.

N THIS PARTICULAR 3-tube receiver, the plug-in coils are furnished with in-dividual shields. They are large enough to reduce coil losses to a point where they are not serious, and they are well spaced so as to avoid intercoupling from the currents FIG. I

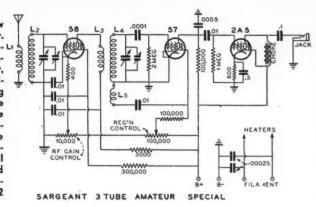tional copies of coil-winding charts can be secured free of charge by addressing the Technical Editor of "RA-DIO." The chart is of value to all builders of small shortwave sets because the coil constants are unusually good and can be used in designing many other types of 2 and 3 tube receivers.



induced in the coil shields from the coils. This is important. The mere fact that a coil is completely shielded means little. It still requires isolation, and should be treated almost as if it had no shield. True, the coil itself is shielded, but the shield is alive with current induced by the coil, and this can cause plenty of trouble in the right place.

Heater wiring often causes unsuspected interstage coupling, especially below 30 meters. The inductance of the heater wires, plus the capacity to ground through the tubes, forms a resonant circuit that is not affected by center-tapping to ground and which can cause a 60 or 120-cycle hum in the set. This hum can be eliminated by the use of a non-inductive by-pass to ground from each side of the heater at either the RF or detector tube. These by-passes can be of small values.

Coupling between exposed grid and plate leads can only be prevented by proper ar-rangement. In short wave sets of the tuned variety, like this receiver herein described, it is impossible to use shielded wire for grid and plate leads without loss of efficiency. Grid and plate wires should be kept as short as possible and located where they will not be near any live parts of other

The Band-Spread System

HE SYSTEM OF band-spreading used in this receiver is similar to that described in RADIO for July, 1933, in an article by this writer. It is a mechanically-operated band-spreader, different from any other known system. The rear photo of 3-tube set shows the main working parts of this band-spreader. The tuning condenser, instead of being rigidly mounted to the panel as is usually the case, is held securely in a swivel or cradle mounting. The cradle mounting is extended upward as shown. At the top a coupling arm fastens to it. The other end of the coupling arm connects to a small cam which is operated by the band-spread dial (left, in the photo). Obviously, rotating this dial will turn the cam and impart a small amount of back-and-forth motion to the coupling arm. This motion is transferred to the cradle mounting, and swivels the condenser STATOR over a small angle. The other dial turns the condenser ROTOR. The stator swivel angle is adjustable, and if the coupling arm is attached to the cradle at a lower point, the angle will be greater. Thus it may be adjusted to give any desired spread on any band. In these days of popularity for pre-selectors, etc., band spreading is becoming a real problem. It is just as easy to bandspread a 4-gang condenser as a single condenser when this method is used.

Regeneration

OR THOSE INTERESTED in an unusually stable regenerator, the writer recommends without qualification the circuit shown. By confining the feedback to the screen, the plate is left free of RF comof the proper size can be used. This improves the tone quality, also the stability, and each site of the stability. and makes it possible to go right into a stage of resistance coupled audio without any locking-up. Furthermore, this regeneration circuit is very good ahead of a superhet, for those who like such a combination. Operation of the regeneration control does not affect the adjustment of the IF transformer when used in that manner. The control is unusually smooth, there being almost complete freedom from squawking and spililng over.

The audio system for this 3-tube receiver consists of a single 2A5 with plate choke to protect the headphones or magnetic speaker from damage. The receiver is fully capable of operating a speaker on U. S. short wave broadcasting and on amateur phone and po-lice calls. For the benefit of those who like to build their own, all values of resistance and capacity are given. Number of turns on the coils, etc., depend on the size and type of coil form used. The coil shield should be at least twice the coil diameter and twice its length. Secondaries of the RF and detector coils should be identical. On the detec-tor coil the secondary should be in the middle, the primary on top, next to the grid end of the secondary, and the tickler below. Turns-ratio between secondary and tickler, although best determined by experiment, should be about 6 to 1 for 40 meters and up, about 4 to 1 for 25 to 40 meters, and about 1½ to 1 below 40 meters. On the waev-lengths around 20 meters and below, it may be necessary to interwind part of the tickler with the secondary in order to get oscilla-tion. The primary coil for coupling the RF stage to the detector should be two-thirds the size of the secondary, and spaced about

1/4 inch from the secondary,

For the CW man who is not interested in single-signal reception, there is perhaps no better set than one of this type. It is an old friend, well known in amateur circles, and also a most popular receiver for all-around

...

short wave reception.

A good way to check the linearity of a grid modulated stage is to plot different bias voltages against RF output. This can easily be done by varying the C bias either side of the working value (modulator disconnected) and checking against antenna current. If the C bias is varied in 221/2 volt steps, the different values of antenna current should be essentially linear when plotted on graph paper. If they are not, the transmitter certainly cannot be expected to have good quality on the air.



Impedance Coupling Vs. Resistance Coupling

MANY regenerative receivers use either resist-MANI regenerative receivers use either resistance or impedance coupling between the detector and the audio amplifier. For CW use there is little to choose between the two methods. Impedance coupling allows slightly more gain to be realized because there is less DC drop across the impedance than across a resistance load. However, resistance coupling gives less trouble from fringe howl.

If really good quality phase sentiments.

weer, resistance coupling gives less trouble from fringe howl.

If really good quality phone reception is desired, impedance coupling is taboo when working out of a screen grid detector. Practically no audio frequencies below 200 cycles or above about 3000 cycles are passed on to the next stage when an impedance is used as the plate load for a 24A, 32, 35, 57, 58, 77, 78, 6C6 or 6D6 tube. Thus resistance coupling becomes necessary.

However, if a triode is used as the detector, the use of the impedance is highly recommended. While impedance coupling, strictly speaking, is not capable of as good fidelity as resistance coupling; when used with triode tubes, the difference in fidelity is only noticeable below 20 cycles per second or above 25,000 cycles, both of which are out of the audible range. In general, impedance coupling gives better fidelity than transformer coupling, although certain manufacturers make audio transformers that give flat fidelity from 30 to well above 10,000 cycles. However, these transformers cost real money and it is often cheaper to add another stage, using impedance coupling, than to get equivalent gain through transformer coupling step-up.

Whence Came the Ten-Volt Filament In Common Transmitting Tubes?

THE ten-volt filament, as used in the 03A, 211, THE ten-volt filament, as used in the 03A, 211, 852 and others, came from the days of Tungsten filaments. A Tungsten filament, for best efficiency, must preserve a definite ratio of length to diameter. Thus in the old 203 tube the dimensions of the tube and its filament made ten volts the ideal voltage. When the Tungsten filament was replaced by the thoriated type the ten-volt rating was maintained, so that the 203 could be directly replaced with the 203A with as little inconvenience as possible. However, the ten-volt filament for tubes in the 100 dissipation class is not particularly satisfactory when thoriated wire is used as the filament material. A study of all the compromises involved calls for either 5 or 6 volts as more nearly the ideal. The lower voltage has two important operating advantages. First, the hum level is reduced 75%, when the voltage is reduced from ten volts to five volts. Second, it is possible to realize a much higher mutual conductance with the lower voltage because the ideal of a uni-potential cathode is more nearly realized.

Crystal Oscillator Tubes

AFTER many months of experience with practically every type of pentode tube, I have come to the conclusion that indirectly heated cathodes must be improved before they are genuinely satisfactory in transmitting circuits. The 59 and the 2A5 are particularly bad actors in that a good deal of the active oxide material from the cathode leaves the cathode and travels over to the control grid where it starts primary emitting. This makes for very unstable operation and is one big cause of the parasitics which characterize the 59 when used as a doubler. This brings us back to the old reliable 47 as the crystal oscillator. We have used it successfully as a tritet oscillator with the filament grounded and the screen above ground (to RF) but while it seems to give somewhat better results than a 59 I still cannot recommend it because the oscillator portion of the tube is still nothing but a triode, which I don't like for best tability and long crystal life. The old and proven pentode oscillator circuit still does the best job. By the way, I might mention that of all the tubes with indirectly heated cathods the 53 has about the huskiest structure. It gives much longer life than the 59s and 2A5s, although it is not as good as the 47, according to my experience with oscillators.

Sylvania Announces 12A7 Tube


THE Sylvania 12A7 type—a combination power pentode and rectifier tube designed especially for use in small AC-DC receivers where space is at a premium—is announced by the Hygrade Sylvania Corporation of Emporium, Pa. There is a 6.3 volt heater for each unit, the heaters being connected in series internally, thus making the rated heater 12.6 volts. Separate connections are brought out for the pentode-cathode, screen grid, and plate. The suppressor grid of the pentode section is connected internally to the pentode cathode. The rated power output from the pentode is 0.55 watt, and the maximum DC load current of the rectifier section is 30 milliamperes.

lam Hínts

- - By JAYENAY -


The Current-Fed End-Fed Antenna

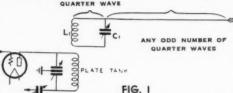THE end-fed Hertz antenna has long been recognized as about the simple has long been recognized as about the simplest arrangement available for ham use. However, 99% of all end-fed antennas use voltage feed to the antenna proper, which means that the hottest portion of the antenna must be brought into the shack, with consequent losses. Fig. 1 shows the current-fed



edition which has materially lower losses than the voltage-fed type, although this type is prac-tically unknown among amateurs. The antenna proper consists of any odd number of quarter waves proper consists of any odd number of quarter waves and the coupling tank, which consists of a coil and a condenser shunted across it, also has a quarter wave across it. If the antenna is rather long, it is important to check the tuning of the coupling tank. The best test is made with a neon bulb to determine that there is very little RF voltage at the point where the coil and the antenna connect, although the other end of the tank should be quite hot.

Push-Push Doubling With a Single Tube
THE OPERATION of a Push-Push doubler is
quite similar to the action of a Wunderlich
detector tube. However, until such time as some
tube manufacturer makes available a Wunderlich
tube with a plate dissipation around fifteen or
twenty watts, we will either have to use two
tubes in the conventional push-push circuit or else
use a single double-grid tube in the unbalanced
circuit shown in Fig. 2. The circuit is, in effect, a split-stator input circuit with the common
condenser lead grounded. However, an ordinary
split stator condenser is not suitable because the
two capacities are not equal. Thus we use two

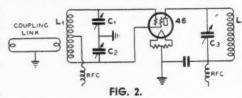

separate condensers, C1 and C2. This capacity unbalance allows us to compensate for the difference in the amplification factors of the two grids in the 46. Grid No. 1 being closest to the filament has the highest mu, so it receives less voltage than grid No. 2, which has a lower mu, and therefore requires more driving voltage to have an equivalent effect on the plate current of the tube. Thus we must adjust C1 and C2 so that the RF ground is closer to the end that feeds grid No. 1 so that the excitation voltage divides in accordance with the relative mus of the two grids. This adjustment is not critical and is made by increasing one condenser and decreasing the other condenser, until the plate current dips to the lowest possible value, meanwhile restoring resonance after each adjustment. While the same value of grid bias gives good results, the operation of the doubler can be improved slightly by using shunt-feed for the bias supply and then using separate and adjustable grid leaks for the two grids. In this case, grid No. 2 requires the greater amount of bias. If seriesfeed is used, the RF choke shown is quite important.

Correct way to make a QSL card for a Y.L.



C. C. Anderson, W6FFP, says this is the right way to do it. See page 23 for data on W6JFY. (P.S.—W6FFP is the artist.)

Improving Impedance-Coupled Circuits

PENTODE TUBES have a tendency to peak at approximately the center of the audio spectrum, i.e.,2500 cycles. Because impedance coupling is widely used in circuits employing pentode tubes, widely used in circuits employing pentode tubes, the peak effect can be further exaggerated by the resonant effect of the impedance itself. This objectionable effect can be largely overcome by shunting a fixed resistance of about 250,000 ohms across the terminals of the impedance, and in this way broadening its resonant characteristics. This method will also effectively eliminate fringe how, thus making for greater sensitivity by permitting the detector to oscillate at the threshold of oscillation, where greatest gain is secured. The objectionable hiss is also reduced.

Filter Fundamentals

No PORTION of the average Ham transmitter is subject to more of the hazards of guess work than the power supply filter network which supposed to by-pass the ripple voltage to

ligib many Th tions

to co

chan Wee not boas qual

ousl equa mod

scril may one

with

cast tion

out

Th

is supposed to by-pass the ripple voltage to ground, so that all that reaches the plates of the amplifiers is "adequately filtered DC."

Dellenbaugh and others have presented some fine material on how to forecast filter performance, but the complexity of the whole subject has made it difficult for the average Ham to practice what is preached, especially when so few manufacturers observe any standard basis for filter choke ratings.

However, it is possible in few words to show a rule-of-thumb that allows the operator to make a fairly-usable guess as to whether or not a given filter set-up will do the job.

The first thing to keep in mind is that the filtering EFFECTIVENESS of a condenser increases directly with the capacity but, what is more important, it also increases as the SQUARE of the applied DC voltage. Likewise, a filter choke's filtering EFFECTIVENESS increases directly as the inductance is increased and as the SQUARE of the DC current through it. Expressing it another way, we reach the interesting conclusion that the POWER being filtered has more to do with determining filter costs than the amplitude of the voltage.

For 60 cycle, full wave rectification (120 cycle

that the POWER being filtered has more to do with determining filter costs than the amplitude of the voltage.

For 60 cycle, full wave rectification (120 cycle ripple) the product of the inductance in henries and the capacity in microfarads should equal 20, if 10 per cent ripple is allowable. This amount of ripple is currently being found on some final amplifiers for CW use, although the Federal Radio Commission has not defined just what it meant by "adequately filtered DC." However this amount of ripple is definitely noticeable and should not be used on the oscillator or buffer stages as it is amplified in all following stages. It is unsuitable for phone use. The maximum permissible ripple is 1 per cent for phone use and broadcast practice requires that the ripple be kept below .1 per cent. To obtain 1 per cent ripple the product of the inductance and capacity in the filter should exceed 200. Thus 20 henries of inductance and 10 microfarads of capacity will do the job. By the same token the operator could use 50 henries and 4 mikes to get the same result. The inductance and capacity can be divided in any convenient way, such as 5 mikes, 20 henries and 5 mikes or possibly 2 mikes, 25 henries, 1 mike, 25 henries and 1 mike. Add all the capacities, then all the inductances separately, then multiply the total capacity by the total inductance. This method is not exact but will give fairly close accuracy and is quite simple. Be very suspicious of your choke ratings because many 30 henry chokes actually measure less than fifteen

close accuracy and is quite simple. Be very suspicious of your choke ratings because many 30 henry chokes actually measure less than fifteen henries at their rated current. Compare the size and weight of your choke with an equivalent known value choke and then revise the rating of your choke to suit your purpose. There is no substitute for iron and copper and, if possible, actually measure the inductance, WITH RATED DC FLOW-ING.

Sylvania Technical Manual

THE wide array of radio tube types now available is reduced to a logical ready-reference able is reduced to a logical ready-reference connections and other data in the Sylvania Technical Manual just issued by the Hygrade Sylvania Corporation of Emporium, Pa. The manual contains 104 pages. It is of convenient pocket size, bound in durable black cartridge paper. Aside from the data on all types of receiving tubes in current use, the manual presents sections on fundamental properties of vacuum tubes, amplifier classifications, definitions, general tube and circuit information, shielding, filtering, heater voltage supplies, volume control considerations, tube and base diagram symbols, and typical receiver circuits in current use. The manual is available to anyone sending 10 cents, in stamps or coin.

The RK-20 In a Broadcast Quality Phone

By McMURDO SILVER

WO things are outstanding in amateur radio telephony-the small number of phones in operation as compared to telegraph transmitters, and the all but unintelligible hash called modulation put out by many of these amateur phones.

ircuits peak at

pectrum, oling is

ated by
This obome by
00 ohms
in this
cs. This
ce howl,
mitting
of oscilThe ob-

smitter

which

age to of the

d some erform-subject o prac-so few sis for

show make given

the fil-

creases ore im-of the choke's ctly as UARE it an-clusion

to do

0 cycle henries 1al 20, mount e final Radio

meant

mount ld not

as it is unermise and ole be cent pacity denries y will could result.

result.
led in
enries
ies, 1
apacithen

tance.

suspi-ny 30 fifteen e size valent ing of o sub-

rence

base Tech-vania con-size, Aside es in unda-

lifier

The primary reason for both these conditions is cost . . . many amateurs would prefer to communicate by voice rather than by code.

This whole picture is now completely changed, thanks to the genius of Dr. Paul T. Weeks of the Raytheon Company, and it is not only possible to build an amateur phone boasting good broadcast station modulation quality, but such a transmitter can be built at a cost equal to or lower than that previously possible for a telegraph transmitter of equal power.

This is made possible by suppressor grid modulation in the new RK20 Raytheon Screen Grid RF Pentode. Previous articles have described this tube and its functions, which may be summarized by stating that less than one watt of audio power is required to modulate 100% its 100 to 120 watts plate input with quality equal to that of the best broadcast stations. This is made possible by variation of suppressor grid voltage, variation of which gives a linear control of RF power

The transmitter illustrated in Figures 1 and 2, and the diagram, Fig. 3, employs one RK20 in a crystal controlled Tritet electron-coupled oscillator circuit and deliveries 100 to 120 watts RF power on any amateur band, for C.W. telegraphy or 25 watts carrier with 100% modulation capability, which gives a peak power output of 100 watts. Modulation is effected through a simple two-tube threestage audio modulator and microphone.

The transmitter consists of three units mounted on three standard 19-in. Crystaline black %-in. thick aluminum relay rack panels, having a combined height of only 171/2-in. The lower unit is the RF power supply, the next is the 100 watt crystal oscillator, amplifier and antenna tuner, and the top unit is

Starting with the RF unit, one of the new RK20's is used as an electron coupled (Tritet) crystal oscillator and amplifier. The crystal is connected between grid and filament, and the oscillator "Plate" tank circuit between filament and grounded screen, thus making up the triode oscillator circuit. Despite the power developed, the crystal is subject to less strain than in the ordinary low powered crystal oscillator due to the high mutual conductance of the RK20-so high that as an RF amplifier, it requires less than a watt of RF driv-

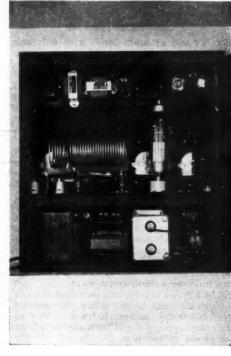


FIG. 2.


ing power. The "plate" circuit of the oscillator consists of two coils effectively in parallel, tuned by a 365 mmf. Cardwell Midway condenser. Since the RK20 is a filament tube and since the filament of an E.C. oscillator must be above ground, these two coils are inmust be above ground, these two coils are included one in each side of the filament circuit, and serve both as RF chokes and as oscillator "plate" inductances. They are wound on a plug-in form to permit interchanging for quick shift to operation on 10, 20, 40, 80 or 160 meter amateur bands.

Oscillator operation is checked by a "plate current" jack in the screen circuit, which is by-passed to ground for RF currents. Because of the effective screening and isola-

tion of the oscillator grid and plate circuits from the plate circuit of the RK20, it is possible to operate the oscillator and output circuits on the same frequency, or where opera-(Continued on page 22)

FIG. I.

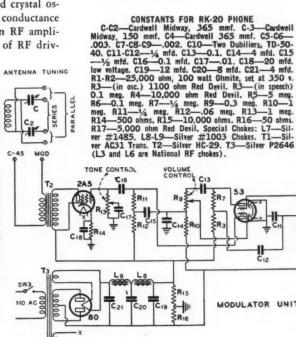ANTENNA TUNING 0000000 20 RF POWER SUPPLY



MODULATOR UNIT

FIG. 3.

RADIO FOR AUGUST

(Continued from page 21)

tion on two or more bands with only one crystal is desired, to double frequency in the

plate circuit.

The output plate circuit is the standard low C of RF amplifier practice, using a 150 mmf. tuning condenser with plug-in inductance wound with 1/4-in, copper tubing. A jack is provided in the RF unit negative plate return lead for plate current check. To keep this jack at ground potential a meter plugged into this jack reads both plate and screen current, so to determine plate current alone it is merely necessary to subtract the previously measured screen current from the total plate current reading to determine the actual plate current of the RK20.

Antenna coupling is by means of a copper tubing antenna coil with variable coupling to the plate inductance. Two 365 mmfd. condensers are provided for series antenna tuning, while both may be connected across the feeders for parallel tuning by simply shifting

two links on standoff insulators.

The RF unit is complete, including antenna tuning circuits, unlike other transmitters available today, and includes a switch to shift the suppressor grid from the modulator for phone operation to 45 volts positive for C.W. telegraph operation.

Frequency stability is what is to be ex-pected—crystal controlled-modulation causing no appreciable frequency shift. Operation and tuning up is childishly simply with the aid of a single 0-150 MA milliammeter. Power output with one RK20 is safely, 100 watts on crystal fundamental, but can be pushed up to 120 watts. It is about 60 to 70 watts on crystal second harmonic, on all bands. One pair of plug-in coils allows operation on the 80 and 160 meter amateur bands, and a second pair of coils permits operation on the 20 and 40 meter bands.

The RF power supply is simplicity itselfone large power transformer providing all filament and plate voltage, on RK19 high vacuum, low voltage drop rectifier tube, a high inductance, lo wresistance filter choke, and 8 mfd. of 1500 volt Pyranol oil capacity. The filter is choke input for good voltage regulation and long rectifier tube life. The power unit is provided with an on-off switch and jack for telegraph key, which must be short-circuited for plug pulled out) for telegraph operation. This power supply develops 1400 volts at 150 MA which, while slightly above the maker's rating for the RK20, is quite safe, and allows 100 to 120 watts of C.W. power output to be had from a single tube, or 25 watts of phone carrier power, running up to 100 watts or more on 100% modulation peaks.

The Modulator

HE modulator is nothing more than a simple three-stage audio amplifier having its power supply mounted in the same unit. It employs one 53 (dual high-mu triode) in two stages of resistance coupled amplification, developing a voltage gain of over 700 times. This two stage amplifier operates out of one of the new Astatic Crystal

Microphones (or out of a carbon or other microphone by addition of a mike-to-grid transformer). The resistance-coupled ampli-fier then feeds a 2A5 pentode developing 3 watts undistorted output, which is applied to the suppressor grid through a suitable coupling transformer incorporated in the ampli-The modulator has input and output terminals, a volume or gain control, an on-off switch, and a tone control. The latter is sup-plied in order to attenuate the modulator's excellent high frequency response in the event that the proposed regulation limiting amateur phones to 3000 cycle modulation bands goes into effect.

We a

effect o

strength

those in

of cours

that the

makes 1

we can' Take

feet) w

directio

sire to

situate

west (a

Now if

the east

naturall

tional 1

one mu

does no

right ar

does a l

in the

angle of

the ante

the ante

ily app

signals

the poin

grees to

other le

enter in the ante is on a

directio

nals fro the tilt

the pat plane,

of 15 o

is permi In ou

Fre

953 for

QS and at

YL bet arr

ma cou Ba

tar

RAI

The gain and power output of the modulator is more than sufficient to modulate the RK20—in fact, the gain control must be turned down to the point of no plate circuit kick during modulation to prevent overmodulation. The frequency response is flat to 4 db. from 40 to 8000 cycles-response which is better quality than the average high-power

broadcast station.

Such, then, is a crystal controlled amateur phone and C. W. Transmitter for operation in, or quick change to, the 10, 20, 40, 80 and 160 meter bands, capable of 100 to 120 watts peak power output, with modulation quality equal to the best American broadcast stations. Yet all this is available, including everything but antenna and 110 voltage power source, at a cost of less than \$160—less than \$1.60 per watt of useful antenna power!

In a future issue will be described a linear

amplifier to boost the power to the maximum

one kilowatt input allowed.

New McMurdo-Silver Band-Spreader

A NEW band-spread system is provided in the A new McMurdo-Silver receivers by the new "Watch" dial—a single airplane dial having four 180 degree scales accurately calibrated in megacycles (thousands of kilocycles) which is read with the large "minute hand" pointer, and two more the large "minute hand" pointer, and two mor 0-100 degree scales read by the "second hand

In operation, the tuning knob is pushed in and the "minute hand" pointer used for broadcast



The improved Silver 5-B single signal super het, the 5C (available Sept. 1, 1934) is the same as the 5B except for a new and simpler band spread tuning method and dial, higher RF gain, less inherent noise, and includes optional A.V.C.

band tuning, then, turning to short waves, this pointer is set to the top edge of any one of the short wave bands clearly marked by heavy black segments on the dial, and the tuning knob pulled out. This brings the separate low capacity threeout. This brings the separate low capacity three-gang band spread condenser shunting the main tuning condenser into use, and if the tuning knob is now turned, the "second hand" pointer will travel over the inside 0-100 degree dial scales. The entire 180-degree movement of this pointer and ovr four revolutions of the tuning knob will now tune the set only over a range of a few hundred kilocycles—the width of the short wave broadcast bands. On this secondary dial short wave stations will be found, not "half a hair wide" as on ordinary dials, but spread out over several degrees of the dial, easier to tune by far, than broadcast band stations, and even easier to read apart.

Mechanically, the system is simplicity itself. On one side of the three-gang tuning condenser, and integral with it, is built a second three-gang condenser of very low capacity, and small size, as is needed for band spread tuning. The shaft of this condenser is linked by an automatic take-up belt to the "second hand" pointer floating freely on the main "minute hand" pointer. Below the dial is

COIL WINDING TABLE FOR SARGENT 3-TUBE RF RECEIVER

R.F. COILS	"A" (Primary)	"B" Spacing between coils		1	(Secondary)	
15-32 METERS	2¾ turns, wound, No DSC.	close S ₁	pacing 1/8-inch etween "A" nd "C".	1	No. 24 DSC, aund, 1/8-inch	
26-53 METERS	43/4 turns, wound, No DSC.	. 32 b	pacing 1/8-inch etween "A" nd "C".	91/4 turns, space we between to		
49-106 METERS	73/4 turns, wound, No DSC.	. 32 b	pacing 1/8-inch etween "A" nd "C".	181/4 turns No. 24 DS	, close wound, C.	
100-208 METERS	10¾ turns, wound, No DSC.	. 32 b	pacing 3-inch etween "A" nd "C".	411/4 turns No. 28 DS	, close wound, C.	
DETECTOR COILS 5-PRONG FORMS	"A" (Primary)	"B" Spacing be tween A&	e. (Secondary)	'D" Spacing be- tween C & E		
15-32 METERS	3¾ turns, close wound, No. 32 DSC.	1/8-inch	41/4 turns, No 24 DSC space wound, 1/8-in spacing be- tween turns.	are inter-	wound with	
26-53 METERS	5¾ turns, close wound, No. 32 DSC.		91/4 turns, No 24 DSC space wound, To-in spacing be- tween turns	18-inch	4% turns, close wound No. 32 DSC	
49-106 METERS	13¾ turns, close wound, No. 32 DSC.	1/8-inch	181/4 turns, close wound No. 24 DSC		3 3/3 turns, close wound No. 32 DSC	
100-208 METERS	35¾ turns, close wound, No. 32 DSC.		411/4 turns, close wound No. 28 DSC		5% turns, close wound No. 32 DSC	

located the tuning knob shaft, carrying two idling pulleys, each belt-linked to either condenser shaft. On this tuning shaft and the idling pulleys are two reversed cone clutches—push in the knob and it engages the main tuning condenser pulley—pull it out and it frees this pulley and positively enit out and it frees this pulley and positively enit out and it frees this pulley and positively enit out and it frees this pulley. This system is known as a "cone clutch", and is

found in the most expensive American precision lathes. Its principles and application have been known for years, and it is so simple as to be entirely trouble-free as well as beautifully sweet and smooth to operate.

The tuning dial with its two pointers is shown in the illustration. Condensers and new McMurdo-Silver dial, \$6.60 net.

22

Antennas for City Dwellers

(Continued from page 7)

We are told that the decided directional effect of certain antennas tends to reduce the strength of signals in directions other than those in which the antenna is directed. This, of course, is true, but again we are reminded that the prohibitive length of such antennas makes them unavailable to us. Let's see if we can't arrive at a more simple substitute.

to

ff

p-

ch

ur


d,


d


n 0-

Take the case of a full wave antenna (65 feet), working on 14 MC. Let us say that the direction from which we wish especially desire to receive is north-north east. Let us so situate this antenna that it points east and west (approximately, as we will see later). Now if the high end of the antenna is toward the east and the low end toward the west, we naturally would consider the antenna direc-tional to the west, which it is. However, one must remember that a full wave antenna does not have its maximum directivity at right angles to the direction of the wire, as does a half wave, but instead it has two loops in the form of an "X", these being at an angle of 54 degrees to the direction in which the antenna points. If the angle of slope of the antenna is not too acute, it will be readily apparent that we may get very definite signals from directions 54 degrees north of the point, and also the same number of degrees to the south. We are disregarding the other lobes to the west, since they do not enter into the discussion. If the direction of the antenna is fixed so that one of the lobes is on a great circle bearing with the desired direction, we are certain to get strong signals from that locality. Rather obviously, if the tilt of the antenna is made too great the pattern will be in an almost vertical plane, consequently useless. Angles of tilt of 15 or 20 degrees are generally as great as is permissable. Back to our original example. In our case, the antenna is pointing ap-

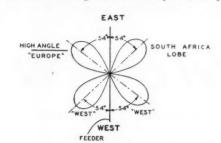proximately due east and slopes to the west with an 18-degree tilt. All east-coast U. S. signals are discriminated against, while at the same time signals from Europe are excep-



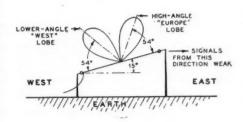

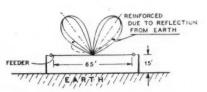

tionally fine. In this way, QRM from the U.S. eastern and southern stations is greatly reduced. We have been able to hear European stations with this antenna which were absolutely inaudible on our regular east an-

Since the antenna is tilted to the west, signals in this direction are also excellent, so we have in reality almost the uni-directional antenna. By using a little judgment as to the directions most desired, and obtaining great circle bearings on these directions, a compromise can be affected so that really strong signals can be obtained from at least one direction and very creditable signals from two of the others. Of course, such performance is only possible with a full wave antenna. A half wave antenna can be tilted to obtain directivity in one of the directions that would ordinarily be dead, but in this case the direction opposite the tilt will be a complete blank. In the case of longer an-tennas the loops make a smaller angle to the direction of the antenna as the length is increased, so that even with a tilt, signals will still be strong in either direction. Of course, signals at right angles to such an antenna will be correspondingly weaker as the length is increased for a given frequency.

One very obvious fault of the system outlined is the fact that it comes close to being a one-band antenna, since on 7 MC, for ex-ample, our fine full wave 14 MC antenna becomes a half wave affair and "blotto" goes the east direction. Conversely the full wave, 7 MC antenna becomes two full waves, with attendant drawbacks, as previously stated. Such an antenna might well be the ideal compromise, since it would seem probable that a balance could be found where the antenna would radiate in at least two desirable direc-tions on both bands, with the tilt adding still a third direction. Yes, the more we think of it the more we are convinced that this is the ideal antenna for the city dweller-but darn it all-our lot isn't big enough!

Fresno Hamdom's Sweetheart, W6JFY

そうこうこうこうこう

A YEAR ago while other YLs were studying for a different kind of license, Miss Opal Larson, 953 Roosevelt avenue, Fresno, Calif., was studying for her ham license, and passed. The call of W6JFY was assigned to her and soon she was on the air with about three watts, limited to local QSOs. She soon yearned for out-of-town contacts, and the low power expert, W6FFP, was hired at \$50 per hour with the result that she soon had a special "FFP" 16-watt '45 transmitter on the Her first out-of-state QSO was with another YL, W7NH, who honestly (?) gave her a much better report than FFP got while standing by to arrange the QSO. Then she gained confidence and many good QSOs followed. Yet she was not satisfied, for everyone gave her better reports than she could give them.

A new receiver was needed and old "Gainer Bane", W6WB, was prevailed upon to build her a custom "Gainer." Opal is a very active YL. She is secretary of the Valley Radio Club, and secretary of the 1934 Pacific Division Convention Committee.

mittee.

She has captured the hearts of all the hams who know her; in fact when she is visited by other hams all they can seem to do is operate her set. Imagine the embarrassment of some of her contacts, she was probably siting by, bored to death, being too much of a lady to suggest that the visiting ham take her to a dance, a show, or at least let her run her own rig.

We predict many shattered hearts at the coming convention for after all, there is only one Opal.

She is a good operator, has a very precise "fist", both for the key and for those who get too chummy. Ask FFP1




No foto is available of her transmitter. Who cares about that? She has a nice QSL card, likes to receive QQSL's, and is always the first to

QSL you.

All in all, W6JFY is a real ham. At her ham set her interest is all radio.

While sitting under a full moon, with a soft spring breeze blowing . . . well, what does a YL ham think about, anyhow?

Conducted by W6WB

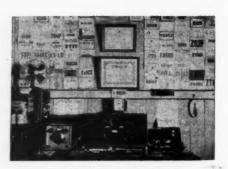

W6CXW

Henry and Sam Sasaki Long Beach, California



Headqu Kenneti Ave., I Meloan field, C

Secon

FOR field its high

who are ed to come and with the rea

than p

merged sponsik "the li Man; at thei operate men a routine

> Secre Int. Dear He S

Porto passi 1,00 dolla Store was

ston torn

of S
day,
to p
out.
only
steam

out, of t

quatent 22, Cro

Star Me ban Bul Sug day

W6CXW IS LOCATED approximately nine miles north of the city of Long Beach, California, at least a half mile from the main boulevard and no high-power lines or BCL's to disrupt the peace of mind of the operators. Not a bad location, any way one looks at it!

rators. Not a bad location, any way one looks at it!

The station is jointly owned and operated by two brothers, Henry (HY) and Sam Sasaki. They ask me to mention that the name is not Russian, they are Japanese. Hi! We have the pleasure of knowing both personally and, confidentially, they are as fine a pair of chaps as you would ever care to meet and both are real operators!

The first station license was acquired in May, 1929, and shortly after another rock-crushing RAC hit the air. A 210 was responsible—however, their stay on the air was brought to a sudden and rather disastrous close... the complete transmitter was stolen! With this and one other exception (when the station was moved to the present QRA), W6CXW has been on the air constantly. After their initial venture, an 852 was installed with 100 watts input (No, we didn't forget to add that other zero)! This same 52 is still in use and is getting better with age. Hi!

The operators were among the early users of crystal control, and as "Hy" says, ". . days when the more back wave one had, the more certain he was to receive that highly-valued report of 'xtal-control'." The old QRA did not live up to expectations as it was impossible to raise Europe for a WAC, although some 39 DX countries were worked, so that the station was moved to the present QRA in '32. In less than a month, the WAC was established. In seems funny for the boys to recall those early-day struggles because since that time WAC has been worked over 150 times!

For some time, the transmitter consisted of a total the control that the States.

times!
For some time, the transmitter consisted of a 47-46-852-852. On 14 MC one of the 52's was used as a doubler-amplifier. Hy and Sam say that disgusting results during the 1934 DX tests prompted the present installation consisting of 47 oscillator, 800 doubler, HK354 buffer and 2-852's in the final. For 14 MC the only change is the use of the 354 as a doubler. They say that

only lack of finances is keeping them from putting a pair of 354's in the final, since the use of this tube has really revolutionized the transmitter. The final 52's usually run at about 4000 volts and the input is all the law allows!

The receiver is at present a Hammarlund Comet Pro with which excellent results have been had. In one year the DX heard has mountd to over 100 countries. Previous receivers included a Schnell, Super Wasp and SW3, these receivers having become obsolete as conditions in the amateur bands changed.

The antenna used is a helf-wayer 10.

Super Wasp and SW3, these receivers having become obsolete as conditions in the amateur bands changed.

The antenna used is a half-wave 40-meter Hertz and is 65 feet 4 inches long, with a single wire feeder 9 feet 5 inches off center. The antenna is suspended between two 70-foot poles, a distance of 200 feet apart; the antenna is so situated that the feeder drops straight down to the shack. The antenna runs North and South, has been in use for the last three years and has gathered in R9 reports from every continent. Another antenna of the same length and height, but running Northeast by Southwest, works out better for Europe, but has been very disappointing in other directions, notably East Coast, U. C., and VK-ZL. It is planned to do some experimental work with directional antennas "as per RADIO" but we can tell you that from the way we hear CXW knocking over the Europeans this "experimental" work is going to be postponed. Hi! Incidentally, there is space aavilable on the east and south sides of the shack up to 1700 feet. Oh!

Activities include membership in A.R.R.L., J.A.R.L., R.S.G.B., IRF, WAC, WBE, and WCA. Most of these organizations are familiar to everyone but the last mentioned, namely WCA, is perhaps not so well known. The initials (WCA) stand for World Contact Association, the membership of which is made up of a small but select group of local amateurs of the world. The membership includes W6ADP, W6BIF, W6CVZ, W6EXQ, W6ENV, W6FAL, W6FKC, W6FZY and both ops at W6CXW. All are WAC, WBE and have worked at least 60 countries. The combined European QSO's of the club this year totals well over 5001

ment at CXW but those who have listened to the W5ATF-W6CXW chats for over a year and a half know that a good rag chew is always welcomed. In addition, a sked has been kept with W2CC for over four years!

DX includes 82 countries (78 not counting Chatham Island, Aelutian Islands, Cocos Island and Galapagos Island) in all continents. We regret that space does not permit a listing of all the wonderful DX worked by this station, but a list of some of the DX follows:

North America—Alaska, Canada, U.S.A., Maxico, Salvador, Spanish Honduras, British Honduras, Panama, Canal Zone, Trinidad, Antigua, Martinique, Costa Rica, Haiti, Dominican Republic, Cuba, Jamaica, Virgin Islands, Porto Rico, Newfoundland, Nicaragua. Oceanica—Australia, Tasmania, New Zealand, Fiji Islands, Ellica Island, Ocean Islands, Hawaii, Philippines, Java, Dutch Borneo, Sumatra, Sarawak, Guam, Tahiti. Europe—Scotland, England, Spain, Germany, Italy, Russia, Netherlands, Poland, Norway, Finland, Hungary, Austria, Belgium, France, Lithuania. Africa—Mozambique, South Africa, South Rhodesia, Nigeria, Egypt, Canary Islands, Algeria, South America—Venezuela, Brazil, Argentina, Peru, Chile, Colombia, Ecuador, British Gulana, Bolivia, Uruguay. Asia—Japan, Korea, Manchuria, China, Hong Kong, Straits Settlements, Federated Malay States, Unfederated Malay States, India, Siberia. Cocos Islands, Chatham Islands, Galapagos Islands, Aleutian Islands. We asked who does most of the operating and the answer was that the fellow who was lucky enough to get at the key first. They modestly state that the possible reason for their DX record is the fact that there are two operators at the key.

Both men have been to Japan and can certainly tell some great tales about their "J"

Both men have been to Japan and can certainly tell some great tales about their "J" brothers. They have visited J1, 2, 3, 4, 5 and J6 districts. They mention, in passing, that it is a pity that more U. S. amateurs do not get the opportunity to visit Japan because those chaps are spdendid hosts and the visitor is always assured of a wonderful time.

Well, you have heard the story of the brothers Sasaki: drop in some time and meet two real amateurs.

THIS 'N THAT-By W6WB

AT last, that much-discussed individual, O. M. Reid, ZS2A, comes to the fore and answers many of the questions which have been so widely discussed. We take the liberty of quoting part of his fine letter: "... I would like to settle that ill' argument with regard to the final stage used here. During the contest I was using a single type 210 with about 1250 volts at 40 to 50 mills, which gives me about 45 watts, average input. Total contacts were 244, with all W districts and two VE. Was able to exchange numbers with all stations both ways, making 8052 points if all the chappies send in their results ... about old ZS2F. .. He (so he says), was only using 10 watts maximum all the time he was on and raised 600 points. Not bad, eh? ZS6B, ZS1C, ZS1H and. I think, ZT5R were using 50 watts. ZU1E had more power, I presume, although I am not certain. ZS1H parked himself on 14 MC and the rest were all on 7 MC... You cannot guess what one day's mail was 'ere, I'll bet. .. 65 letter and cards to be precise! Yes, and have been rather a long time answering them, and had to QSL via the Bureau ... WID best 73s to all the mob over there, Thine, Bureau . . . there, Thine,

'PYE', Radio ZS2A."

DON'T FORGET THE MELBOURNE CENTENARY DX CONTEST TO BE HELD IN OCTOBER THIS YEAR! See back issues of "RADIO" for full details of the contest. Now is the time to get those great circle bearings on VK and get the antenna functioning so that you can raise plenty of the gang from "Down Under." East-coast and middle-west stations will have the opportunity of a lifetime to snaffle off a bunch of those clusive Australian stations.

AND now for a dip into the pages of that very excellent journal, "The T & R Bulletin", for DX news from the British Empire.

Mr. R. E. Erle advises that amateurs in the Strait Settlements will operate under the call VS8 instead of VS1. As far as he knows, this change does not extend to amateurs located in the Federated and Unfederated Malay States.

Malta stations are now officially licensed and up to May 19 the following have been registered: VP3C becomes VP3A, VP3H is VP3B, ex G2AZ is now VP3C.

The months of June and the early part of July saw a great increase of European DX on 14 MC. On the west ceast, G, F, ON, and D were com-

monplace. Such extremely rare DX as PAO, LY, OE, HAF, I, OH, SP, HB and SUI were heard and worked by many of the W6-W7 gang. Bearing out the theory of the effect of the moon on DX, we were able to predict the exact night on which European DX would be heard. Really worthwhile!


W7BB says he cracked W6CUH's record of 2! VK and ZLs in one morning! Well, here's the answer from W6QD himself: "... we think nothing of working 2! ... upon checking our log we find that during our best night we worked 2! VK and ZLs with 7 Js, 4 KAs, 3 VSs and 2 ACs, also 2 PKs thrown in for good measure." Well, well, what can you say in answer to that, Ed'I ft his column does nothing else, it certainly brings the boys out of the old hole to refute statements that others make. Hi!

ATTENTION, WEST COAST AMATEURS! The Federation of Radio Clubs will have its biggest session of the year at Santa Barbara on September 1, 2 and 3. This gathering will assume the aspects of a regular convention and no one within a reasonable distance should fail to attend. Maybe see you there.

24

I. R. F. NEWS (Formerly I.T.K.)

The Amateur's Legion of Honor

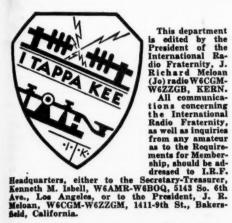

Second Honor Degree Awarded

Second Honor Degree Awarded
FOR distinguished or heroic radio service in the
field of communication this fraternity awards
its highest degree, the Honor Degree, to members
who are deserving of it. Only one has been awarded to date, although several brothers are eligible
and will receive the award in due time. Usually
only through friends of the deserving person do
the real facts become known, such is their modesty.
Too frequently is the radio operator belittled rather
than praised. Too often have the heroic efforts
of radio operators been doomed to oblivion or submerged in the praise of others not directly responsible for the beneficial action, even though
"the lightning jerker" may have made the supreme
sacrifice.

Many amateurs have become so sufficiently skilled

Many amateurs have become so sufficiently skilled at their hobby that they are also professional radio operators or engineers. The fact that professional men are paid for routine duties does not discount their service when their actions are no longer

hat-and gret the list

Ion-gua, pub-lico, alia, llice

ava, hiti.

thu-outh Al-

S!

Los Angeles, Calif., June 13, 1934.

Secretary, Int. Radio Fraternity, Los Angeles, Calif.

Here is a report of my services in connection with

Dear Sir:

Here is a report of my services in connection with the San Felipe hurricane:


San Felipe Hurricane Sept. 1928, commonly called Porto Rico Hurricane, started in British West Indies, passing over Porto Rico, Haiti, Cuba and Florida. 1,000 lives lost in Porto Rico. Damage 100 million dollars. Wind velocity over 150 m.p.h. for 2 days. Storm broke Thursday a.m. Vessel to which I was assigned was off north coast Haiti, relaying storm warnings. That a.m. no communication to be had with Island. Bull S.S. Co. vessel 'Edith' torn from anchor in secluded harbor of San Juan, dashed aground at entrance to harbor. Next day my vessel made port. Quoting P. R. "Progress' of Sept. 25, 1928: "Every man for himself—Friday, Saturday and Sunday". RCA short wave point to point station out. NAU, Navy station out, WPR out. No amateurs on. No power for 5 days, then only emergency power for hospitals and police from steam engines. Saturday messengers afoot and on horseback sent into interior to get news; all phones and telegraphs down. Whole cities of 10,000 wiped out, never again rebuilt. Humacao, P. R., is one of these. One week after storm struck people were digging in mud for food, milk selling for 75c a quart. Gov. Towner, of P. R., did not know extent of damage and did not act for 72 hours. Sept. 22, 1928, first vessel arrived from States with Red Cross supplies.

As a radio operator I handled all traffic for 4 days in and out of San Juan. Messages received from

22, 1928, first vessel arrived from States with Red Cross supplies.

As a radio operator I handled all traffic for 4 days in and out of San Juan. Messages received from States given to local Cable companies and Navy. Messages handled were U. S. Weather Bureau and bank code (10 letter groups—no rpits), War Dept., Bull Steamship Line, N. Y. Porto Rico Line, S. P. R. Sugar Co., British Government at St. Kitts. For 5 days only two or three hours sleep nightly. I had cooperation of Local Harbor Master and all agencies named above, except U. S. Navy. Receipts on hand for messages to Dept. of Interior of P. R., Bureau of Insular Telegraph and French Cable Co. Refer to N. T. "Daily News"—Sept. 1928; N. Y. American and P. R. "Progress" Sept. 1928 issues. It had not relayed this traffic, even though I violated Radio Laws by Port operation, that hundreds of deaths would have resulted from neglect. Red Cross would have sent an insufficient amount of food, blankets and medicine. Receipts, and official communications on hand for inspection of anyone.

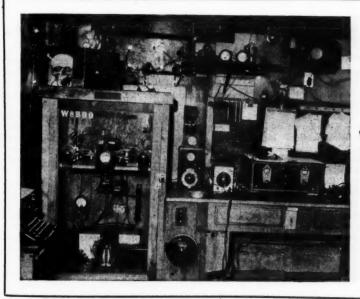Respectfully,
(Signed) JOSEPH DOCKENDORF,
W6JTC.



W6BOQ

Station of Kenneth M. Isbell, Secretary-Treasurer of I. R. F.

West Coast Division Chief Elected

RONNIE MARTIN, W6ZF-KUP, popular amateur leader, is chosen to head the important West Coast Division in which IRF has almost 200 West Coast Division in which IRF has almost 200 crack operators and engineers, truly the "cream of the crop". This Division includes Arizona, California, Nevada, Hawaii and the Philippines. W6BPO, Jack Smyser of Las Vegas, is State Chief of Nevada at present with an election in progress for State Chief of California with W6LN, W6SM and W6GHD as nominees. SC's for Arizona, Hawaii and P. I. are yet to be chosen with several excellent men under consideration.

Mr. Martin will represent IRF in this Division and supervise the operation of the State organizations in his charge. Through his State Chiefs he will supervise the organization and functioning of all Chapters and he will direct traffic and communications in conjunction with the IRF western network.

or all Chapters and ne will direct traine and communications in conjunction with the IRF western network.

W9HVN, Gene Poteet of St. Louis, government radio operator in the U. S. Engineers service on the Mississippl, has been appointed State Chief of Missouri. Members should henceforth make their monthly reports through him and lend their coperation to his efforts. Other State Chiefs for this Central Division are about to be appointed for Nebraska, North and South Dakotas. Inasmuch as few IRF members in these states have the necessary time available because of occupational pursuits, these several openings present excellent opportunity for prominent amateur leaders resident therein who are qualified for IRF membership. Such amateurs who have not yet received formal invitation to IRF brotherhood should communicate with headquarters at once.

IRF Silver Cup Contest

To choose the "Best Amateur Station in To choose the "Best Amateur Station in North America" each annum, open to all amateurs, is the purpose of this contest. Robert S. Kruse, prominent radio engineer and short wave pioneer, is tentative chairman of the Judges Committee. Other noted engineers from IRF ranks will be chosen from various sectors of North America to complete the board of judges. The contest will be unique and it will present an entirely new angle on amateur achievement. Every amateur will have an equal opportunity to compete. Application of modern short wave knowledge to amateur equipment, versatility of operation, facilities for emergency operation, past record, individual ingenuity, coupled with new ideas in action, will all be featured in this contest, together with other phases yet to be outlined.

The first cup winner will be chosen for this year, 1934. Watch for complete details and photo of the handsome silver IRF trophy.

Ten Meter Contest

FOR the purpose of the advancement of radio communication on the 28 mgc. band and the encouragement of portable activity during the vacation season, the Ten Meter Contest began July 15th and continues to September 15th. All

members entered in this contest should submit detailed reports on their accomplishments immediately at the conclusion of the contest. The prize will be awarded with respect to the general purpose of the contest and your general activities on 28 mgc. Frank C. Jones, IRF brother and noted authority on the ultra-high frequencies, has been asked to judge the contest.

W6DTJ, Russell Bennett of Stockton, Calif., won the low power contest, using a single 230 tube. His score was over 7000 points. The prize kas been awarded.

W6LN, Thorius LaCroix, took honors in the QSO contests and won the prize, a Munzig brass ribbon-wound adjustable antenna coil.

Attention, All Amateurs!

So desirable has it become to be an IRF brother, and so enthusiastic are the amateurs about the ITK-IRF plan, that headquarters has been besieged with countless letters requesting that we create a junior membership so that every worthwhile man can have an opportunity to cooperate in IRF's sound program of a great unselfish fraternity sponsoring a New Deal for the amateur with fair and honest administra-tion. Taking cognizance of this demand, the large Southern California Chapter submitted a tion. Taking cognisance of this demand, the large Southern California Chapter submitted a resolution to headquarters for vote of the general membership to wit: (1) That every worthy licensed amateur be permitted to join IRF, independent of the present requirements, and by merely making application. (2) That all of the present IRF members become brothers by reason of careful choice, formal invitation and the meeting of rigid requirements and that this membership shall be known as the ITK section (Order of ITK) of the International Radio Fraternity. (3) That the requirements remain unchanged for this ITK classification, with the possible addition of a 21-year age limit. (4) That ITK men shall retain their former degrees, exclusive of those admitted to "Junior Membership". All members of IRF, including the degree section of ITK, shall have direct voice on all IRF affairs, included in this resolution would probably be that radio clubs could as a whole become IRF clubs with their present officers, set-up remaining undisturbed. Such clubs are to be independent of ITK Chapters. While qualified amateurs could gain brotherhood in the Order of ITK (Degree Men) directly as formerly, amateurs not so qualified can join IRF and look forward to the day when their merits are such that they can become ITK candidates. The whole organization structure therefore would be known as The International Radio Fraternity, having an upper classification of Degree Men, known as ITK (not I Tappa Kee).

The above-mentioned plan effecting all licensed amateurs has been untilined publicly IRF Headquarters wishes an expression from all amateurs as to their reaction.

D-X NEWS

Proposed New D-X Country-Classification

T is with great pleasure that we here reproduce a letter received from Mr. O. M. Carter, W9ADN, together with his proposed list of DX Country Classification. "The Carter System", as we rightfully call it, was complied after much intelligent study of the matter of country classification. In Mr. Carter's letter you will find many interesting views of this rather-complicated situation. His proposed list has been sent to members of the Official Country Committee so that they may use it as a basis for their considerations. In the event that the Committee decides to adopt this new classification, the DX amateurs are indebted to Mr. Carter for his valuable and timely contribution to the art.

1010 Madison St., Lockport, Illinois. June 28, 1934.

"RADIO" Pacific Building, San Francisco, California. Gentlemen:

A note in a recent issue of "RADIO" states that you are undertaking a study similar to one I started about three years ago, the establishment of a list of countries of the world to be used as a standard or "yardstick" by all of us in computing the number of "countries heard", or "countries worked". I started to prepare such a list because I found that in comparing DX coverage with others there was so much disagreement in what was a "country" and what was not. I had, in fact, become irked at having someone say that he had worked so many countries (invariably more than I had, of course), and then discover that he had counted Yukon Territory, or Scotland, or some

other such place as a separate country.

When I started my "study" I had no idea that I was to spend the equivalent of weeks of work on it. I had expected to find a list of work on it. I had expected to find a list already prepared for me, but such was not my good fortune. But perhaps it was really fortunate that I did not find a list ready made for I was forced, before I got through, to look up many places, or countries, about which I had previously had a very imperfect idea as to their location, climate, people, etc. Which brings to mind again the suggestion which someone once made: . . . that we would all learn much more, find our hobby much more interesting, and instructive, too, if we would suggested the state of the suggestion of th familiarize ourselves with the land, people, and so on, of the DX stations to which we so glibby say, "Geom, R8, 2RU, 73, Gb."

In establishing our "yardstick", we should endeavor to have it confirm to our needs and also agree with modern ideas of these accura-

also agree with modern ideas of those accustomed to world geography, commerce and communication. An example of what we should not use is the suggestion once made that all minor subdivisions of all the countries should be counted, as well as 48 states, all provinces of Canada, Australia, South Africa, Brazil, Mexico, all islands, etc. There are a number of objections to such a system. (1) The prepara-tion of a standard list of such divisions would tion of a standard list of such divisions would be no mean undertaking and would correspond to multiplying this list I am submitting by, perhaps, 20 times. (2) It would be necessary for each amateur to have quite a good set of maps to check the locality of such small subdivisions. (3) Such a system would be preposterous to use in telling our DX accomplish-

ments to our friends, our bosses, etc., acquainted with international geography. Our yardstick should be so arranged that a person in one locality has no unreasonable advantage over a person in another locality, as would be the case if each island in the world were to be counted as a separate country. Think what an advantage a person in Japan would have if he got a friend to take a portable transmitter in a boat and land at each of the 1000 and more

islands in the Japanese group!

After one has studied the problem for a short time and made a start on a list he finds that there are apparently only two logical reasons for classifying localities as "countries", and that neither of these, alone, is quite satis-factory, either. The two ways are on the basis of geography, and on the basis of government. The geographical basis is ruled out, however, because of the immense number of islands, and similar considerations. At the start, a division on the basis of government looks to be comparatively satisfactory. If we were to use this rigidly, however, we would have to delete from our list such island groups as the Cape Verde Islands, Madeira Islands, and the Canary Islands, as they are governed just as though they were a part of the mainland countries of Europe to whom they belong, and so would reduce the total possible number of DX countries for us to communicate with, when such a reduction does not seem necessary considering the great geographical separation. The same thing is true of certain of the countries of northern Africa, which unquestionably we have every justification to consider as separate countries.

In view of these difficulties I was at a loss as to how to prepare a list of countries that would satisfy the requirements previously mentioned. I consulted several professors of history, and political science and they were able to suggest no simple formula for our use. The suggestion was made, however, and the more one studies the situation the more one realizes that something of the sort must be done, to combine the two methods of division on the

basis of government and geography. The method used was to prepare a list of all geographical localities listed in the U.S. Postal Guide. Then each locality was looked up in the Encyclopedia Brittanica to determine its political status. The division was then first made on the basis of government and then special cases made to agree with great geog-raphical separation. An arbitrary decision was made to list as a separate country all islands more than 300 miles distant from the governing country. Independent units such as the United States, Great Britain, Dominions and Crown Colonies of the British Empire, colonies of other countries than those of Great Britain not called Crown Colonies but administered in about the same way, are listed as "countries" in all cases. Groups of islands, such as the Bahamas. Dutch West Indies, Dutch East Indies, Gilbert and Ellice Islands colony are listed as one country and each island in the group is not listed as a separate country. the case of islands that are governed as independent units, such as Trinidad and Martinique, each independent unit is listed as a sepa-rate country. The Virgin Islands of the British Empire and of the United States are counted as two countries, and so on. In other words, whenever a colony is administered direct by the mother country, or protecting country as the case may be, the island is listed as a separate country. If an island has a Resident Officer who in turn reports to a Resident-General for a group of islands, then only the group is listed.

RADIO

100 P Design & Pane flers, & Receive Office

ment, Tubes, Unbeat Send

He

rh

ag

su

ch tic

H

6

AN

Due to the smallness of some islands and the fact that they are practically uninhibited at the present time, and also to the fact that some of the maps available, particularly those of the western Pacific, were not suitable to measure distances as small as 300 miles, they have been included with the governing coun-If these places later have stations, and subsequent investigation warrants it, they can be separated and listed as a country.

As a whole, the listing and classification of localities has been done slowly and carefully. However, it is my suggestion that each country that has island possessions, protectorates, etc., be given an opportunity to study the list before a final OK is put on it. It is possible that an occasional error has been made, or that some omission has been made in the condensed final list. Considering the immense number of localities looked up over such a long interval of time and the absence of anyone to check over my work, it would be a bit of luck if the list were perfect as it stands. However, before any appreciable changes are made, the person or persons recommending them should study the problem in its entirety so that the list will be consistent throughout and so that they will not be misled by any unintentional feelings of nationalism.

Yours very truly, (Signed) O. M. CARTER, W9ADN.

- I Aden
- Afghanistan
- Alaska, including Aleutian Islands, Pribilof Islands, St. Lawrence Islands
- Albania
- 5 Algeria
- 6 Andora
- Anglo-Egyptian Sudan
- Ascension Island
- Australia, including Norfolk Island, New Britain Archipelago, Admiralty Islands, New Ireland, New Britain, Solomon Islands, Santa Cruz Islands, Australia mandated territory of New Guinea
- 10 Austria
- II Azores
- 12 Bahamas, including Little and Great Abaco, Great Bahama, Eleuthera, Cat, Wattling, Rum Cay, New Providence, the Exuma chain, Long Island, Andros, Crooked Islands, Mayaguana, Inagua
- 13 Barbados
- 14 Basutoland
- 15 Bechuanaland Protectorate
- 16 Belgian Congo
- 17 Belgium
- 18 Bermudas
- 19 Bismarck Archipelago
- 20 British Honduras
- **British Somaliland**
- British Guiana
- 23 Canal Zone (Panama Canal Zone) 24 Cape Verde Islands
- 25 Ceylon
- 26 Costa Rica
- 27 Cuba
- 28 Cyprus 29 Danzig
- 30 Denmark
- 31 Dominican Republic 32 Dutch (Netherlands) East Indies, including

A.C. CURRENT-ANYWHERE! WITH Kato LIGHT PLANTS



o is

ind ted

nd

in.

list

ed

A Little Gas & a Kato AC plant enables you to operate transmitters, AC radios, amplifiers, refrigerators and all other standard household appliances. Sizes 300 watts and up. Write for interesting the modescriptive literature.

KATO ENGINEERING CO., Mankato, Minn., U. S. A. Mig's of AC Generators and Converters for operating AC Radios on 32 and 110 volts DC.

RADIO'S GREATEST VALUES

100 Pages: Filled with latest Design Portable, Mobile and Rack & Panel, Public Address Ampli-ders, Short-Wave and All-Wave Receivers and Convertees Receivers and Converters, Inter-Office Call Systems, Test Equip-ment, Replacement Parts, Kits, Tubes, and Accessories—all at Unbeatable Rock Bottom Prices! Send for Your Copy Today!



COAST TO COAST RADIO CORP

'HAMS' Here is the OHMITE Amateur

N D B



Here is the Handbook you have always wanted . . . sixteen pages of resistor and rheostat data needed by every amateur . . . how to select bleeder resistors, voltage dividers, filament rheostats, plate supply systems, etc. Ingenious tables and charts eliminate formulas and calculations and save 90% of the work. The Handbook also contains data on a new AC-DC Frequency · Meter · Monitor, a Class-B Modulator, wattage and resistance charts, Ohm's Law Charts, new MULTIVOLT tapped resistors, power rheostats, etc.

Price 10c

Use the coupon below or see your parts dealer for the higgest dime's worth you ever received.

OHMITE--

MANUFACTURING COMPANY 629 N. Albany Ave., Chicago, Ill.

Enclosed find 10c for my copy of the OHMITE AMATEUR HANDBOOK.

NAME ADDRESS CITY

for the 5 meter band particularly STANCOR TRANSFORMERS

This group of transformers, designed and made expressly for amateur transmitting . . . sound amplification, assure the builder of the 5 meter set the utmost in effective, satisfactory efficient performance. The experience of STANCOR in the making of the widest variety and number of EXACT-DUPLI-**CATE Replacement Transformers** for all makes and models of radio receiving sets has given STAN-COR engineers a keen appreciation of the necessity for special design

for special purpose . . . an unusual sensitiveness to differing requirements that is reflected in this specially developed group of transformers for your use.

Each unit is identified by the STANCOR trade mark placed in a prominent position as our pledge to you that it is not an adaptation of a transformer originally designed for other services . . . that you have bought, not just a transformer, but a STANCOR transformer for 5 meter work.

STANCOR transformers for the 5 meter band are distributed by authorized STANCOR distributors all over the United States, Canada and our Island possessions. You will want the STANCOR

> catalog of these units. Drop a card to this office so we may get it in the mail for you at once and tell you where your nearest STANCOR distributor is located.



STANDARD TRANSFORMER CORP.

Amateur Transmitting & Sound Amplification Division 850 Blackhawk Street, Chicago, Ill.

WIRES and CABLES FOR EVERY RADIO NEED

Whether you are building a "Super" or servicing a customer's set, you can always depend on Consolidated Radio products to fulfill your every requirement perfectly. CONSOLIDATED products are distributed by America's leading Jobbers and Dealers everywhere. Send for our latest catalog.



Peoria & Harrison Sts., Chicago, III.

Airplanes, Blimps, Broadcasting Stations, Commercial Operators, Hard of Hearing, or wherever exacting performance under all




conditions is required. you will find TRIMM FEA-THERWEIGHT headphones. Mechanically rugged, electrically accurate, they excel by test. We invite your beadphone problems.

Ask your favorite Jobber, or write us for information TRIMM RADIO MANUFACTURING COMPANY

The Pacemakers in Headphone Development 1528 ARMITAGE AVE. CHICAGO, U. S. A

10 WATTS

of Resistor Perfection

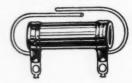

LOW - PRICED, efficient, moisture proof ten watter that will be welcomed wherever quality with economy is a factor.

Compact, wirewound, vitreousenameled, positive, low resistance contacts through non-oxidizing Monel metal bands and lugs-plus pigtails for convenience. Will withstand high temperature, give long usage and permanent resistance value.

Same type made in three sizes, three ratings and 67 resistance values.

FREE Vest-Pocket Volume Control Guide





SMITH-PRECISION **CRYSTALS**

Full-sized, specially ground X cut crystals; powerful, accurately calibrated, single-frequency escillators. Unconditionally guaranteed.

3500-4000 kc /s—Close to Frequency, \$2.35
7000-7500 kc /s—To Exact Frequency, \$2.90
465-525 kc /s—S.S. Filters X Cut...\$2.60
Postpaid by airmail.
Commercial Frequencies at Attractive Prices.

W. W. SMITH W6BCX

Pioneer Manufacturer of

Fine-Quality Piezo Plates 215 West Cook Santa Maria, Calif.



Brings You the Next 4 Issues of "RADIO"-Subscribe Now

New D-X Country Classification

(Continued from page 26) Bali, Banka, Billiton, Dutch Borneo, Celebes, Java, Dutch New Guinea, Sumatra, etc.

33 Dutch Guiana

34 Dutch (Netherlands) West Indies, including Aruba, Bonaire, St. Eustatius, Saba, Dutch part of St. Martin

35 Egypt 36 Eritrea

Esthonia

38 Ethiopia

Falkland Islands

40 Faroe Islands

Fernando Po and Spanish Guinea

42 France (including Corsica)

43 French Cameroons

44 French Equatorial Africa

45 French Guiana 46 French Indo-China, including Annam, Cam-bodia, Cochin-China, Laos, Tonkin

47 French India—Chendernagore, Karikal, Ma-he, Pondichery, Yanaon, Calicut

48 French Settlements in Oceania-Archipelago, Marquesas Islands, Tuamotu, Leeward Islands (French) Society Islands (including Tahiti), Tubuai French Somaliland

50 French West Africa, including Senegal, French Guinea, the Ivory Coast, Dahomey, the French Sudan, Haute-Volta, Mauretania, Niger, French Togoland

Gambia

52 Gibraltar

Gilbert and Ellice Islands—Indl. Line Islands, Palmyra, Washington, Fanning, Christmas Islands

54 Gold Coast Colony, including Ashanti and Northern Territories

55 Great Britain and Northern Ireland, including England, Scotland, Wales, and Northern Ireland

56 Greece, including Crete 57 Greenland

58 Guadeloupe, including La Desirade, Les Saintes, Marie Galute, Basse-Terre, Grande-Terre, St. Bartholomew, French part of St. Martins

59 Guam

60 Guatemala

Haiti

Hejaz, Nejd and Dependencies

Hongkong, including Kowloon

65 Hungary Iceland

India, including Burma, Bhutan, N.W. Frontier Prov., Brit. Baluchistan, Andaman, Nicobar, Laccadive, and Maldive Islands

68 Nepal

69 Iraq

Irish Free State

Italian Somaliland

73 Jamaica, including Cayman Islands, Turks, Caicos Islands

74 Japan

76 Latvia

77 Leeward Islands, including Anguilla, Antigue, Barbuda, Dominica, Montserrat, Nevis, Redonda, St. Ketts, Virgin Island (British part) 79 Liberia

80 Liechtenstein

81 Lithuania

Luxembourg

84 Madagascar and Dependencies (Ste. Mariede-Madagascar, Nossi-Be, Comoro Islands) 85 Madeira Islands

86 Malay States

87 Malta

88 Marianes or Ledrones, Marshall and Caroline Islands

Martinique

90 Mauritius

91 Mexico (Continued on following page)

HOLD-E-ZEE SCREW DRIVER

Instantly holds, starts and sets up those bothersome screws back of instrument boards on all autos; electrical and radio equipment. Gripper slides up out of way. It's easier . . quicker. Saves time, trouble and cost on first job. Used as regular screwdriver everywhere. Finest materials used throughout. Each blade of espe-cially tempered hexagon tool steel with special spring steel fingers.

Ala

Combir

1 Built

2 Swit

3 Built for 5

4 Built for 3

5 Amp phas as in

6 Pow

7 Leve

Alan 6 Ne

You

Send trial

Produ

N

608

CON

Mon

tice

stea

G.

RA

EN

RCA bined embra cal tr

specia new '

R-2 TYPE

Transparent amber unbreakable handle. Fully insulated. Blade 2"; overall 378". On display below.

List Price, 35 cents



6-ON 4 COLOR VARNISHED DISPLAY

Made in Popular Sizes S-7 shown below—Hardwood Handle, Blade 7". Overall 111/2". List Price 60c.



If Your Jobber Cannot Supply You, Order Direct from Factory

UPSON BROTHERS, INC. 84 EXCHANGE STREET, ROCHESTER, N. Y., U.S.A.

COMRADECO

QUARTZ CRYSTALS

for the

Commercial and Amateur Station

Whether you are the chief engineer or owner of a Broadcast, Experimental, Police, Amateur or any other class of radio transmitting station you can place implicit faith in COMRADECO Crystals to maintain your frequency within the limits prescribed by the Federal Communications Commission.

We have prepared a special Bulletin fully describing our commercial precision crystals and giving the new low prices. It is yours for the asking.

FOR THE AMATEUR

1715-2000 or 3500-4000 Kc. Crystals... All amateur crystals are supplied close to your spe-

cified frequency and the calibration at room temperature is accurate to .05 % .

HOLDERS, Dustproof, plug-in type... NOT a flimsy, molded affair, but a scientifically de-signed holder with good heat attenuation, thus mini-mizing frequency "creep."

COMMERCIAL RADIO EQUIPMENT CO.

KANSAS CITY, MISSOURI

Agents for Remler Broadcast and Public Address equipment in Missouri, Kansas, Oklahoma, Arkansas, Nebraska and Iowa.

Just Out Alan 60-A 16 Watt P. A. UNIT

Combining all the following features in ONE crackle finish metal case:

- 1 Built in input transformers and current sup-
- 2 Switch for change over from radio to mike to phone to line.
- 3 Built in input Transformers with provision for 500 and 4000 ohm lines.
- 4 Built in output Transformers with provision for 3-7-15 and 500 ohms.
- 5 Amplifier unit consisting of 53 1st stage and phase inverter, 53 pushpull stage and 2-2B6 as in the output stage.
- 6 Power supply utilizing one 5Z3 rectifier.
- 7 Level and tone control.

AND MANY OTHERS

Alan 60-A.P.A. unit list price less tubes \$75.00 Net to Dealers and Servicemen \$42.50

> ALAN RADIO CORP. 83 L Cortlandt St., New York City

MR. SERVICEMAN!

You Can Make Every Service Call SHOW A PROFIT

Send us your name, address, and 50 cents for trial samples and particulars about our Proven Product and Sales Plan.

Do It Now

NEAL POLISHES, INC.

608 Broadway


Cincinnati, Ohio

CONNECT phones and key into the Mixer Monitor, and you have a first-rate code-practice oscillator. Strong,

steady tone, volume control.

It's an excellent listening monitor.

For CW, or phone-It's always useful-

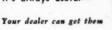

G. F. Lampkin Laboratories Cincinnati, Ohio

146 West McMillan St.

RADIO ENGINEERING (RCF

RCA Institutes offers a combined course of high standard embracing all phases of Radio. Practical training with modern equipment at New York and Chicago schools. Also specialized courses and Home Study Courses under new "No obligation" plan. Illustrated catalog on request.

RCA INSTITUTES, INC., Dept. RA-34 Varick St., New York 1154 Merchandise Mart, Chicago Recognized Standard in Radio Instruction Since 1909

- Morocco (French)
- Morocco (Spanish) Morocco (British)
- 95 Netherlands
- New Caledonia
- Newfoundland, including Labrador
- New Hebrides, including Banks and Torres Islands
- New Zealand, including Nauru
- Nicaragua 100
- Nigeria, including British Cameroons, Lagos Norway, including Spitzbergen Arch. 101
- 103 Nyasaland Protectorate
- 104 Palestine
- 105 Panama
- 106 Paraguay
- 107 Persia
- Peru 108
- 109 Philippine Islands
- 110 Pitcairn Island
- 111 Poland
- Porto Rico 112
- Portugal 113
- Portuguese East Africa (Mozambique)
- 115 Portuguese India (Goa, Daman, Diu)
- 116 Portuguese Timor
- 117
- Portuguese Guinea Portuguese West Africa (Angola)
- Reunion (Bourbon) Island
- Rhodesia, Northern
- 121 Rhodesia, Southern
- 122 Rumania
- 123 St. Helena
- 124 St. Pierre and Miquelon
- 125 St. Tome and Principe, including Sarame
- 126 Saar Territory
- 127 Salvador
- 128 San Marino
- Serbs, Croats and Slovenes, Kingdom of (Czechoslovakia)
- 130 Seychelles, including Admirantes, Cosmoledo, Aldabra
- 131 Siam
- 132 Sierra Leone
- 133 Spain
- Swaziland
- 135 Sweden 136
- Switzerland
- 137 Syria, including Lebanon, Alaouites
- Tanginyika Territory 138
- Tonga (Friendly) Islands
- Trans-Jordan
- 141 Trinidad, including Tobago
- 142 Tunisia
- Turkey (Asian and European) 143
- Uganda
- U.S.S.R., including Moldavia, Bashkir, Tartar, Kirghiz, Dagestan, Crimea, Vakutsk, Karilian, German Volga Settlements, Buriat (Caucasus) Mts., Georgia, Azerbaiken, Armenia
- 146 Union of South Africa, including Cape Province, Natal, Zululand, Amatongaland, Orange Free State, Transvaal, British Bechuana-land, Tristan Da Cuba, South West Africa
- Uruguay
- Venezuela
- Windward Islands, St. Lucian, St. Vincent, Grenada, Grenadines 150 Zanzibar and Pemba

Latest In"B"Power




Smallest unit on the market. 2%" wide, 4" wide, 4" high by 5" leng. This complete Genemotor furnishes up to 200 volts D.C. Operates from 6 volt storage battery. Ideal for Auto, Airplane or Battery Radios, and Portable Amplifiers.

Write for details and prices on this and

CARTER MOTOR CO.

365 W. Superior St.

Chicago, Ill.

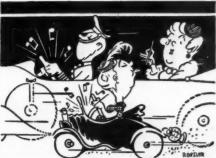

The Colonels and Judy O'Gra

may or may not be 'daughters under the skin"... but it's a sure bet that their auto radios function equally well . . . that is IF they are equipped with Centralab Suppressors.

For Centralab suppressors work mighty well against the asthmatic wheezings of a decrepit collegiate car of early vintage . . . and they do a real job filtering out the umpty umph horsepower impulses of a sixteen cylinder Rollsnice.



Milwaukee, Wis.

Centralab

Motor Radio Noise Suppressors



NEW AND BETTER

OF BAKELITE

SHIMPLE CONSTRUCTION

FITS PIN JACKSSHOCK PROOF
OF ORDER SIZE

WALL COTTLETS ETC

AD METAL PARTS

MAR & S

LONG

NO CHUCK TO INTERPERE

Servicemen, Technicians—Send for descriptive folder on the Ideal Test Prod, a real test prod that will fit into any socket or pin jack, outlet plug and will stay there! No chuck to interfere. Phonograph needle, easily replaced. Cord replaced without soldering. Furnished with either tinsel or stranded wire cords.

Maywood Radio-Electric Mfg. Co. 3533 E. Slauson Ave., Maywood, Calif.



Low Range FUSES voit ranges for broadcast equip-etc. \$100 Protection Guaran-4503 Ravenswood Ave. tee. There is a distributor near you.

Chicago, III. LITTELFUSE LABORATORIES

A Ham Receiver Lacking These Features is Antiquated!



The SKYRIDER The MODERN Ham Receiver

Pioneer W9RA Enthusiastic

George E. Joyce, President Chicago Radio Apparatus Co., a distinguished ham of pioneer days, W9RA established in 1909, says: "If a signal is on the air, the SKYRIDER gets it. Cuts through static—actually seems to thrive on this nuisance! I get a new thrill everyday from my SKYRIDER-more thrill than from any set I've ever owned, due to the extreme ease of locating stations and its extraordinary sensitivity. It's the best buy on the market. Con-gratulations!"

Actual Fractional Microvolt Sensitivity Built-In Monitor Calibrated Dial Co-Axial Coils with Non-Failing Switch Continuous Band Spread Built-In Power Pack and Speaker -vou get them all in the SKYRIDER

The old spark coil, the loose coupler and the "three piece" receiver with an arm load of plug-in coils have a warm spot in my heart. I used them—in the early days. But, like 2-cylinder cars and corsets they belong buried in the past! Yet, because the manufacturer long neglected the ham,

thousands of amateurs have had to lumber along with antiquated equipment. So, we built the SKYRIDER - a thoroughly MODERN Amateur Receiver, with everything to fit today's requirements, including a fair price.

SEND for BOOK: I can't cover half the features of the SKYRIDER here—ask your Jobber for the SKYRIDER Book or request it of me. It's free.

the hallicrafters,

W. J. Halligan, President

417 North State Street

Chicago, U.S. A.

whe

fact

sev

JOHNSON TYPE "D"

TRANSMITTING CONDENSERS

Single and Dual-Section (split-stator) Models JOHNSON Type "D" Transmitting Condensers achieve ca-pacity values and high voltage ratings in the most com-pact assemblies ever constructed. Though small in size and low in cost, they are equivalent in performance to many larger and more expensive condensers.



A few of the exclusive features: Sturdy, rigid, polished plates, .051" thick. Corners rounded and polished for high flash-over voltage. MYCALEX Low-Loss high-frequency insulation standard. Integral, laminated low-resistance photybor-bronze contacts. Bi-Metallic cone bearings front and rear; adjustabe. Large diameter %" spacars.

ers.
A full range of capacity values, in both Single and Dual-Section (split-stator) types. Voltage ratings, per section: 3500 RMS. (.080" spacing) and 7000 RMS.

m: 3500 Mms.

175" spacing).

no of the popular Dual-Section models:

3500 Volt Rating Per Section

No.

Cap. Per Section

List Price

\$12.50


18.50 List Price \$12.50 18.50 Ne. 100DD35 200DD35

For Full Details Get BULLETIN 200 From Any AUTHORIZED JOHNSON DISTRIBUTOR

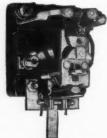E. F. JOHNSON COMPANY

Manufacturers of Radio Transmitting Equipment Waseca, Minnesota, U. S. A.





New Ward Leonard Relays

OVERLOAD RELAY

WARD LEONARD Midget Overload Relays are specially designed for use in transmitter circuits of amateur radio stations to provide protection to the tube against overload or currently the state of the

rent surges. These overloads may occur while tuning the transmitter or if resistance bias is used on the power amplifier, the tube may become overloaded should loss of excitation occur.

The normally closed relay contacts are connected in series with the primary of the plate rectifier transformer. The relay overload coil is connected in the negative return lead from the rectifier so as to operate at low potential.

When a current surge occurs the relay armature pulls in

When a current surge occurs the relay armature pulls in, opening the contacts in the rectifier circuit and protects the tube from damage. The contacts are held in the open position by a mechanical latch until the operator trips the latching device, thereby closing the contacts and reconnecting the tube in the

The relay is adjusted for operation in the vertical position.

Operating current 200 or 250 MA. List Price....\$8.50

UNDERLOAD RELAY

WARD LEONARD Midget Underload Relays are designed for use in transmitter circuits of amateur radio stations to provide protection to class "B" modulator tubes and possible breakdown of secondary of class "B" modulator transformers should the class "C" tubes fail to hold the load due to loss of

SHORT-WAVE MANUAL

120 page 6x9 book for newcomers in amateur and short-wave field. Profusely illustrated. \$1.00 per copy.

"RADIO," Pacific Bldg., San Francisco, Cal.

TRANSCEIVERS



6-VOLT MODELideal for plane, auto or wherever 6-volt source is available.

Price\$17.95

Tubes ... 1.68 2-VOLT MODEL for portable or field work. Employs smallest size batteries.

Price\$18.75 Tubes 2.04

Built

LE

chassis-class B circuit with five tubes including a stage of speech amplification-outputs of 3-10 watts, Price including tested tubes. \$29.50 Power supply for the above\$26.50 RK-20 POWER AMPLIFIER employing two of the new suppressor-grid tubes in push-pull, permitting 100 watts CW output on four bands and 30 watts output when modulated. Price including two tested tubes \$65.00.

Write for new bulletin describing the above apparatus in detail. It will be sent free upon re-

Harvey Radio Laboratories

12 Boylston Street

Brookline, Mass.

ty

ch

R

e"

rm ike

st! m,

ti-

or-

fit

our

Ā.

95

for rk. ize

04

es. 50

kle

50

ew tts

This midget size mica condenser is extremely popular where space limitation is a factor — Polymet fabricates seven different types of mica condensers from .000005 mfd to .03 mfd capacities.



Hí·Frequency Condensers

These condensers are designed to eliminate the common faults of ordinary condensers such as poor power factor and inductance. Because of their low loss characteristics Polymet's new Hi-frequency line is particularly recommended for use in short wave receivers.

Behind the POLYMET PRODUCT

Are recognized by many of the leading manufacturers in both the radio and electrical industries for that HIGH QUALITY so essential to dependability. THEIR ENGINEERS DO NOT GUESS—THEY KNOW. The successful service man, experimenter, or amateur does not guess, he knows that the use of POLYMET products in his work is his GUARANTEE OF SATISFACTION.

POLYMET STANDARD WET ELECTROLYTIC
This type wet electrolytic condenser type is most popularly used throughout the entire world because of its established reputation for quality and durabilities.

Polymet Condensers

ELECTROLYTIC—Wet and Dry Types PAPER-Tubular and all can types MICA—All Types, Midget Sides with lugs & leads TRANSMITTING OIL CONDENSERS CONDENSER for all PURPOSES



PETITE CONDENSER

A new POLYMET Tubular paper condenser in greatly increasing demand by radio manu-facturers. Its compactness and low cost effect many economies in radio.



POLYMET DRY ELECTROLYTIC CONDENSERS
Exceptionally popular in the leading AC-DC receiving sets. Furnished in many combination dual and triple units. Supplied in either cardboard or metal-envisioners.

We Also Manufacture TRANSFORMERS and WIRE WOUND RESISTORS

Polymet Manufacturing Corporation NEW YORK, N. Y., U. S. A.

831 E. 134th ST.

durability.

Write for New 1934 Catalog

=QUALITY=

at a Price You Can Afford to Pay!



FRANKLIN Transformers

Very conservative rat-ings on Transformers ings on Transformers and Chokes for every Amateur Station.

"MOST SOCK PER DOLLAR"

Write for Catalogs

FRANKLIN TRANSFORMER MFG. CO. 607-609 22 Ave. N.E., Minneapolis, Minn.

LEICHNER CAPACITORS

Built up to a Standard-Not Down to a Price

You will be money ahead by using LEICHNER CAPA-CITORS in any RF circuit of the transmitting. Both by their low initial cost, and greatly increased efficiency.

LEICHNER CAPACITORS embody the following out-

- Dielectric, finest quality Flint Glass.
 No change in capacity due to heating.
 High current carrying capacity.
 GUARANTEED FOR ONE YEAR.

Manufacturers' inquiries solicited Your dealer can supply you-or write us for prices

Leichner Electric Company FORT WAYNE, INDIANA

UNING CONTROLS

FOR RADIO SET MANUFACTURERS

New Airplane Type

in Ten Styles

More Than 50 Kinds Shown in Our Catalogs Also Escutcheons, Cabinets, Name Plates and Other Specialties

Write for Catalog

REMOTE CONTROLS FOR AUTO RADIOS

EXPORT ORDERS RECEIVE SPECIAL ATTENTION Cable Address-CROWNAME CHICAGO

Jobbers and Dealers Find Our Line Profitable



No. 120 style 2/5 actual size. Ratio 12 to 1 in 180°.

CROWE NAME PLATE & MFG. CO.

Established 35 Years 1755 GRACE STREET CHICAGO, ILL., U. S. A. Pacific Coast Representative, W. BERT KNIGHT, INC.

NOTICE! You can get the next 4 issues of "RADIO" for only \$1.00. Subscribe now.

W9USA—"At the Hall of Science Theatre—in Chicago"

(Continued from page 10)

to demonstrate the marvel of high-frequency transmission and reception. You'd be surprised to notice the favorable impression created.

Undoubtedly, the presentation could be more effective than it is, but before defaming W9USA at the Hall of Science too strenuously please attempt to appreciate the handicaps under which the station is operated.

Whether it is generally realized or not, it should be quite apparent that through this presentation amateurs are offered that once in a lifetime opportunity to demonstrate to a heretofore unappreciative audience the intriguing thrill of the art that is our hobby. The amateurs, through the medium of their transmitters, are putting the show across. Keep up the good work.

Getting More Out of the FBXA

(Continued from page 12)

before. Because the main bands used are the 7 and 14 MC, the work seemed well worth while. Nine-tenths of the images disappeared, and those that were left were quite weak.

A word should be said about the variable resistor that controls the screen grid voltage. This should be of a fairly high wattage rating; it is connected across the total voltage of the power pack. The .1 mfd. condenser which was removed from the original cathode resistor was placed on the arm of this potentiometer. The wire that originally went to this screen was cut out of the circuit, and the voltage was picked up at the resistor leading to the primary of the xtal IF stage. No condenser was found necessary across the variable cathode potentiometer. Also, these po-

tentiometers need be set but once for each

While it is true that the noise increased with the signal strength, it was well worth it, because the terrific volume of the BFO noise drowned it out. If someone will come forth with some dope on how to kill this terrible background noise which is always R5 to 6 when the BFO is turned on, I believe that the information will be welcomed by many.



SANGAMO Accurate Condensers

These condensers are ideal for shortwave equipment. Tested at 2500 and 5000 volts for use in small radio transmitters. For maximum efficiency use these low loss units.

Write for catalog sheet

SANGAMO ELECTRIC CO.

SPRINGFIELD, ILLINOIS

Twice as Big as Before

THE SECOND EDITION of

KRUSE'S RADIOPHONE GUIDE

- and is just as full of operating and constructional information that isn't found elsewhere.
 - And furthermore . . . there's a complete set of

Batcher's 'Radiografs'

Circuit-

erodyne.

tector-

58 tuned

oscillator

'59 outp

in mega

3362 N

High

comp

Range—five ama:
Tuning—ed vernie

the simplest problem-solvers we ever saw.

• At your dealers or Postpaid for 50c (Canada 75c)

ROBERT S. KRUSE, Guilford, Connecticut

Greater Power with GRAPHITE ANODES



The Cooler Operation of Amperex Power Tubes—because of the greater surface and black body radiation of the Graphite Anodes results in longer life and greater power output.

800	- \$	10.00	List	Price
203A	-	15.00	List	Price
211	_	12.50	List	Price
210	_	3.00	List	Price
830	_	8.75	List	Price
845	-	17.50	List	Price
852	_	22.50	List	Price
860	_	35.00	List	Price
866A	_	5.00	List	Price
872	_	15.00	List	Price
872A	_	17.50		
204A		95.00		
849	_	160.00		

Dealers write for complete catalog and discounts

AMPEREX ELECTRONIC PRODUCTS, INC.

79 Washington St., Brooklyn, N. Y.

AMPEREX
Power Tubes •

BIG NEWS FOR HAMS



Kit \$15.75 Wired \$19.75

Sargent 3-Tube "Amateur Special"

NEW -- BETTER

Receiver with Stage of Radio Frequency Amplification

Get REAL

- · Selectivity
- Sensitivity
- Tone, Volume
- DX, Band Spread

ORDER YOURS TODAY

E. M. SARGENT CO.

2085 Broadway

Oakland, Calif.




each

ased h it,

oise orth ible 0 6 the

5B CHOSEN IN PREFERENCE TO LL COMPETITION Selected as official

Communication Receiver at W9USA...

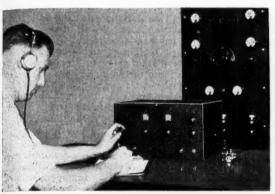

One of the 5B's at W9USA being operated by D. L. Warner, W9IBC

The 5B has won the enthusiastic approval of Col. Foster and hundreds of amateurs who know. The latest honor accorded it, namely selection by W9USA is but further proof of the 5B's perfectly obvious excellence and superiority.

S E N D 3 c
stamp for new complete catalog describing above items, E. C. Frequency
Meters, New Airplane Dials, Relay
Racks, RF Chokes, Audio, Power and
Filter Transformers, and a host of
new and interesting amateur and
commercial apparatus.

- SPECIFICATIONS -

Tuning-One main illuminated vernier tuning dial, smooth and easy, directly calibrated in megacycles. Band spread tuning anywhere in range— Sensitivity — Better than one amateur, broadcast, commer-microvolt absolute.

Tubes—'58 tuned RF, 2A7 1st detector—E.C. oscillator, two '58 tuned IFS, '58 audio beat oscillator, 56 second detector, '59 output, 5Z3 rectifier.

SO 000 KC—

SO

fve amateur bands on 1 dial. IF Amplifier—Dual air tuned, Litz wire . . . 465 KC.

Beat Oscillator—Electron coupled '58. Beat note pitch adjustable from front panel.

Circuit—Eight-tube superheterodyne.

20 and 40 meters—200 degree
built and adjusted for crystal
resonator, without crystal, resonator, without crystal, band width 21 KC 10,000 times down. With crystal, absolute single signal (50 cycles wide).

Power Output—3 watts undistorted. Supplied complete with Jensen dynamic speaker, and head phone jack on front


Shielding—100% perfect, all parts individually shielded. Overall cabinet shield easily removable with 6 thumb nuts.

WORLD'S FAIR RADIO AMATEUR COUNCIL COMMUNICATIONS COMMITTEE 59 East Van Buren Street CHICAGO, ILLINOIS June 14 1934, Attentions Mr. Mein

PRICE \$59.70 net to amateurs with eight guaranteed and tested Raytheon tubes. Each set complete with selectivity control, crystal switch, phasing condenser and crystal socket-ready for insertion of crystal. Add to above price \$9 net for Bliley crystal with holder, and complete crystal alignment—complete price, ready to go single signal with crystal, \$68.70.

McMURDO - SILVER, INC.

CHICAGO, U. S. A.

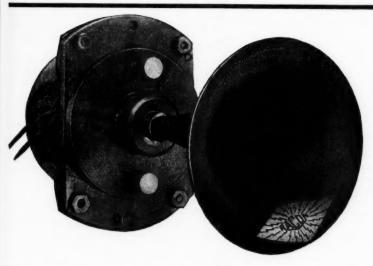

for WIDE-RANGE HIGH-FIDELITY REPRODUCTION

RACON can now supply a complete line of electrodynamic units for both low and high-frequency reproduction. The high-frequency loudspeaker illustrated operates in the band from 3000 cycles to 10,000 cycles. Special types for higher-frequency reproduction can be supplied.

High-quality low-frequency units are available for a wide range of power inputs. The complete line is described in a new catalog just issued. A copy will be sent upon request.

Racon electrodynamic borns and units are manufactured under 14 exclusive Racon patents



SALES OFFICES IN PRINCIPAL CITIES



QST Oscillating Crystals

"Superior by Comparison

All "Scientific Radio Service Crystals" are accurately ground to an accuracy better than .03% on equipment tested regularly by the U. S. Bureau of Standards standard frequncy

BROADCAST and COMMERCIAL BANDS Mounted in our Standard Holder and ground to our usual high degree of accuracy \$35.00 each. Mounted in our NEW Isolantite Monel Metal Crystal Holder \$45.00 (adjustable air gap). Prices for other Frequency Bands quoted upon

AMATEUR BAND

Ground to within FIVE Kilo-cycles of your specified frequency in either 80 or 160 meter bands \$15.00 each. Accurate calibration with each crystal.

Free! Send for New Illustrated Folder-Free!

Scientific Radio Servicé "The Crystal Specialists" Since 1925



124 Jackson Ave., University Park, Hyattsville, Maryland

RADIO CLUBS

Special Group Subscription Rates

are offered if 5 or more members subscribe at one time. Write for rates.

...

"RADIO," Pacific Bldg., San Francisco, Cal.

NEW CATALOG

JUST ISSUED ON

Lenz Radio Wires and Cables

Featuring Many New Items

Lenz Wires and Cables are used ex-tensively by a ma-jority of the set manufacturers to-day. This places us in a position to pass on to you advance on to you advance information con-cerning the proper types of wires and cables to be used for Auto installation and Home Set Service work.



LENZ ELECTRIC MFG. CO.

1753 N. Western Avenue, Chicago Send coupon below NOW for the Up-to-Date information in our Catalog No. 20,

Please	send	me	сору	of	your	Catalog	No.	20
Name								
	-							

State

Col. Foster's Comment

think that any business man with a vested interest permits that interest to be ignored then

you just don't know commercial people.

Since it is the only way the League directors may keep themselves informed of the wishes of all members the liaison officer learns the desires of the commercial members and carries them to the directors. In 1931 Liaison Officer Warner learned that the commercial members wanted the amateur members to ask for no more frequencies at Madrid. He wrote the directors putting this up to them and calling for a mail vote on the question. At that time the Canadian government itself was planning to demand more frequencies at Madrid for its amateurs. Warner indicated to the ARRL directors that they should vote to ask for no more frequencies. They so voted

The commercial members had long desired to stop the amateur members from transmitting third-party messages across the Pacific. There was no way of accomplishing this by law in the United States but there was a way of doing it at the Madrid convention—by getting the wording of the international regulations changed and then getting the United States Senate to ratify the new regulations. With the acquiescence of Liaison Officer Warner they got the wording changed. They got it changed without either knowledge or approval of the ARRL Board. The com-mercial members wanted the new amateur regulations ratified. Whether the directors would have voted to oppose ratification is a question; that Liaison Officer Warner failed to convey to them the new wording of the regulations is a fact. In this case the Liaison Officer took it upon himself to pass upon this question; he sided with the commercial mem-From then on he acted in accordance with their wishes and worked tooth and nail for ratification.

A record of the Circuit Court of Appeals of the District of Columbia says that up to February 23, 1927, the amateurs were entitled to all waves from 200 meters downward but that at various national confer-ences they had, "through their authorized ences they had, "through their authorized representatives offered to relinquish most of their frequencies for commercial develop-ment". The commercial members of the The commercial members of the ARRL wanted this territory of the amateur members and made their wishes known. Just who were the amateurs' "authorized representatives" I don't know. Liaison Officer Warner was one—if not the only—authorized representative of the ARRL. And I don't know if the relinquishment of nearly all of the amateur territory was authorized by the ARRL Board; but I do know that the com-mercial members of the League had their wishes well taken care of by the ARRL.

Besides these instances of the ARRL's looking after the interests of its commercial members there are numerous others; but these three will illustrate the point. So let no one hold the false notion that the ARRL may, or does, work for the interests of its amateur members and ignore those of its commercial members. The amateur members make a thousand and one demands upon the ARRL, and the directors and officers accede to a few of their wishes. The commercial members make few demands but of great consequence, and ALL of their demands are

The ARRL headquarters claim that the directors are elected mostly by the votes of the amateur members and that there is therefore no danger of the League's being influenced by the commercial members. From the fore-going illustrations you may see the shallowness of this claim.

It is a sorry contretemps, however one looks at it. But it is a mess that one is sure to

make when one tries to mix amateurism and commercialism in the same association. That has never succeeded and NEVER WILL. The man who was responsible in 1920 for infringing the property rights of the then owners of the ARRL-the licensed amateurs-by arbitrarily making co-owners of all QST subscribers did a horrible injury to amateur radio. He started an irritation that developed into a suppurating sore. In all these 14 years nothing has been done to heal it. Occasionally a layer of thin guaze has been laid over it to hide it from view but the sore has gone on eating into the flesh and bone of amateur radio until now it can no longer be hidden, and nothing but a major operation for extirpating the whole infected area will give

it a chance to heal from the bottom.

(Continued from page 6)

Vice Directors

T SEEMS from the minutes we are now to have a flock of "vice directors". President Maxim suggested, "without objection", that the General Counsel prepare the wording for a motion to bring this about. Just whose vices these 14 new officials are supposed to direct I don't know, but at any rate henceforth each division will be required to carry a spare. And each vice director will be nominated and voted for just as in the case of directors. That should make elections doubly interesting—and doubly irritating. And should keep the hams so busy with internal squabbling that they will have less time to keep a wary eye on headquarters. It seems that the sole official duty of a vice director is to go to an annual meeting and vote in the event that the director himself shall have notified the Secretary of his inability to be present. If the director dies, then-under the resolution—the vice director stays home. That is, unless the director shall have been thoughtful enough to notify the Secretary of his approaching demise and thus make it possible for the vice director to appear and vote. In case the director has not exercised this precaution then the vice director stays home. Or he, too, may die if he feels like it, for all the difference it would make to his division. And all this nonsensical over-organization-with its accompanying expense and its doubling the political campaigning and internal strife—is set up ostensibly for the sole purpose of providing that no division lose its vote at an annual meeting in the re-mote event that its director is unable to at-An alternate could have been authorized to vote by a slight change. It surely would not have mattered at this meeting if any one division had lost its vote. If its di-rector was in the Warner-Segal-Maxim bloc his vote would not have been needed for the Combine would still have had 13 of the 16 votes anyway. While if he had been of the opposition, composed solely of Directors Jabs and Culver, the division's vote would have counted as little as their votes did.

IRECTOR CULVER put squarely up to the Board the question of the right of a director to give out for publication any non-confidential information coming into his hands. The gang grudgingly admitted, "It is the individual director's privilege, at his discretion, and his responsibility." That "responsibility" was dropped in by way of indicating that if the "individual director" exercised his right he was assuming a heavy load of it. My prediction is that herefter load of it. My predicition is that hereafter many more of the communications from Warner to directors will be labelled, "Confidential". It is questionable whether any of this stuff is confidential.

The ARRL, Inc., is stated to be a "scientific and educational institution" from which no

(Continued on page 35)

Col. F

individu and as s of incor tion tha secret it formatic property reason held fro tion are their or forced t This las of this United

> heavy showing 'swell" ing hov have d of the how m States a the per

> > An al ham. and s Your RADIO

date by

ALL IE ments consul livest tion. beatab

В

City .

Col. Foster's Comment

and

That

The

ring-

rs of

sub. adio. into

years

sionover

gone

teur

den. exgive

w to

dent

on".

ding

nose

d to

nce-

arry

mi-

ably

And

rnal

to ems

the

ave be

the

me. een of it and sed ays

his

or-

nse ing for ion reator-

elv diloc he 16 bs

to

of

on to

ed,

at at

of

m

nny

fic

ar-

(Continued from page 34)

individual ever secured any part of the profits, and as such to be exempt from the payment of income taxes so just why ANY information that affects members should be kept secret it is hard to see. Every item of information collected by headquarters is the property of the members and there is no reason why one scrap of it should be with-held from them. The owners of a corpora-tion are entitled by law to know all about their own business but they should not be forced to go to law to get their information.
This last year especially has brought the truth of this principle home to the people of the United States.

ARNER sums up his retort with,
"The percentage of active amateurs
who belong to ARRL is so extremely heavy that it constitutes a perfectly swell showing." We aren't interested in how showing." 'swell" it is but we are interested in knowing how "extremely heavy" it is. What we have demanded to know for several years, and what we shall find out, is: how MANY of the ARRL members are licensed amateurs, how many of such members are of the United States and how many are foreign. Of course the percentage changes slightly from day to day but it can be obtained as of any given date by checking the ARRL membership list

"WHO'S WHO IN AMATEUR RADIO"

An absolutely indispensable book for the active ham. Contains 170 pages of photos, personal and station writeups of over 3000 amateurs. Your shack is incomplete without a copy. Sent for one dollar, postpaid.

RADIO AMATEUR PUBLISHERS, 1107 Bway., New York

ALLIED will supply your 5 Meter equipment requirements at consistently lower prices. Before you buy—consult us. We are specialists in this newest and livest field of radio activity—5 Meter communication. Our complete stocks of 56 M.C. gear are unbeatable. • Be sure to see Allied's dramatic 5 Meter exhibit at W9USA when you visit "A Century of Progress."

Build your own effective 5 Meter Transceiver at an amazing low cost. Designed by Frank C. Jones of "RADIO." Sold exclusively by ALLIED. Kit of quality parts (No. R1300) sells at only \$5.441 Kit complete with accessories including hand microphone, type '19 tube, and batteries, is only \$11.19. (R1301). Simple to build. Equally successful as transmitter and receiver.



NATIONAL HARVEY



Transceivers
The 2 Volt National model sells at \$27.00 less tubes.
(Order No. F9960). The 2 volt Harvey model sells at \$18.75 less tubes. (Order No. R1140). We handle all types of 5 Meter Antennas—Johnson Q system—Pickard type, etc. For complete 5 Meter information and for our large FREE Catalog with Amateur Equipment listings write Dept. J.

Ilied ₹ Radio CORPORATION W. JACKSON BLVD., CHICAGO

with the latest amateur call-book and government records. Or it may be obtained very simply and cheaply by asking each member for his call if he has a license—by buying 20,000 double postcards and asking that those members who are licensed to sign their calls on the duplicates and mail them in. Then well all see just what this "perfectly swell

showing" is in an organization of 20,000 that proclaims itself to be wholly "amateur". We want to make of the ARRL what it was for several years before Warner came upon the scene, an organization of licensed amateurs; but first we want to find out how many com-mercials and other non-amateurs have been taken into it.



TRANSMITTERS

PEERLESS RADIOPHONE TRANSMITTER, complete with microphone, tubes, milliammeter, ready to plug into 110-rolt 60-cycle A.C. supply, special \$36.50
PEERLESS CRYSTAL CONTROLLED TRANSMIT-

\$10.95

CO

7

Q

0

A

H	ROUND THE WORLD RECEIVERS Latest Models—Made With First Quality Parts	
∢	Kit Form	Wired, tested and Assembled
-	PEERLESS 1-tube Blackhawk\$ 3.89	\$ 4.89
U	PEERLESS 2-tube Junior receiver	6.15 8.95
H	PEERLESS 3-tube PROFESSIONAL	10.95 24.50
4	WRITE IN FOR DETAILED DESCRIPTIONS OF ABOVE AS WELL AS OTHER TO FIT YOUR POCKETBOOK.	
	LET US ALSO QUOTE YOU ON THE LATEST NATIONAL AND HAMMARLUN	D RECEIVERS!

TUBE	SPEC	IALS
Lin	ht Duty	Heav

TUBE SPECI	ALS		
Light Duty 30-day Gtd. 210, 15-watt	Heavy Duty 90-day Gtd. \$1.35	Extra Heavy Duty 6-month Gtd. \$2,10	SLIGHTLY USED TELEPLEX WITH THREE TAPES
866	1.65 1.35 1.20	3.35 2.10 1.75	SPECIAL \$9.95
Naty 5-watters, CG-1162 tubes, WHILE THEY INSULINE SHORT WAVE COILS, PER SET OF CROCKER-WHEELER AEROPLANE GENERATOR	FOUR—only	275 volts at 60 mills	s, and 250 volts at 110
mills. Only a few leftXTAL BLANKS\$1.00 WE	STON MILLIAM	METERS, 0-5 up. Mo	del 301, SPECIAL 3.69

RED HOT SPECIALS

			65
hone filters, prevent t	humina analism outs d		
none tilters, prevent i			of Marin
	ourning, packing, cuts o	own miss, lengthens the nie	or your
			3.39
eys, fully encased, flam	perroof, silver contacts, e	ach	
ED CONDENCEDS "	monditionally guarantee	d for one year made up of	the best made
ER CUMPENSERS—"	ilconditionally guarantee	u for one year, made up or	'ment-Anna't
ins; crinkle finish, blac	ik enamel metal cans, po	rcelain high tension bushing	insulators:
1500 v	2000 v	3000 v.	3500 v.
			\$ 7.00
2.45	4.50	8.50	10.00
3.05	7 50	35.75	19.00
UNMOUNTED	TYPE-SEALED IN I	PARAFFIN	
	eys, fully encased, flam ER CONDENSERS—u ons; crinkle finish, blad 1500 v. \$1.75 2.45 3.95	teys, fully encased, flameproof, silver contacts, e ER CONDENSERS—unconditionally guarantee ons; crinkle finish, black ename! metal cans, po 1500 v. 2000 v. \$1.75 \$3.00 2.45 4.50 3.95 7.50	1 cys, fully encased, flameproof, silver contacts, each

	90-Day Guara		
Cap.	600 volt	800 volt	1000 volt
1 mfd.	\$.20	\$.30	\$.40
2 mfd.	.25	.40	.70
3.5 mfd.	.50	.50	.90
4 mfd.	.40	.60	1.00
	PEERLESS 100 WATT BL	EEDER RESISTORS	
Res. Ohms	Rati		Price
20 000	95 N	// A	40

30 MA .59 25,000

AUTOMOBILE RADIOS

Gypsy Automobile Radio Chassis, 6-tube, uses two 236's, two 237's two 238's. Set Only—Special (while they last) \$7.95

Franklin 6-tube Super-het. remote control feature, set only. 9.95
Set complete with RCA tubes and speaker. 15.50

EXTRA SPECIAL!

Have just landed the Wurlitzer Franchise. Write for your Wholesale Prices on WURLITZER REFRIGERATORS! Good Discounts, Guaranteed Merchandise. Write for Descriptive Literature if more information is needed.

Write in for Our New Ham Catalog-Just Off the Press!

UNCLE DAVE'S RADIO SHACK

356 BROADWAY

FOREIGN TRADE SOLICITED CABLE ADDRESS Uncle Dave"

ALBANY, N. Y.

RME-9D SINGLE SIGNAL SUPER



CONTINUOUS BAND SPREAD FROM 13 TO 540 METERS

No plug-in coils used. All controls located on

able feature and you will find it incorporated the front of panel. A precision instrument built with the idea in mind that the best is never too good for particular amateurs. Mention a desir-

RADIO MFG. ENGINEERS

313-315 BRADLEY AVENUE

PEORIA, ILLINOIS

CONTINENTAL Transmitting CONDENSERS



Get the latest CONTINENTAL Catalogs showing heavy-duty oil-filled condensers—and the high-voltage insulated CONTINENTAL Carborite Resistors.

Here is a complete line of high voltage paper transmitting condensers-designed to withstand the most severe operating conditions. Conservatively rated. Compact in size to save space in your layout. Stand-off porcelain terminals. Convenient base mounting plate.

	Working			Working	
Capacity	D.C.	Amateur's	Capacity	D.C.	Amateur's
Mfds.	Voltage	Net	Mfds.	Voltage	Net
1	1000	\$1.26	4	1500	5.49
2	1000	1.98	1	2000	2.25
4	1000	3.51	2	2000	3.99
1	1500	1.74	4	2000	7.50
2	1500	3.00			

New-Complete Catalog Ask your jobber or write

CONTINENTAL CARBON Inc.

Cleveland, Ohio

You can get the next 4 issues of "RADIO" for only \$1.

We make every effort not to see how cheaply QSLs can be made, but to make the finest available funds for the work permit. At your request, you will receive a few samples—ideas of others—and prices. See what improvements you can make upon them, and let us create your ideal!

CHAS. E. SPITZ

BOX 1804 (W6FZQ) PHOENIX, ARIZ.

For better and longer service, better filtration with no current leakage,

Use G-H PAPER WOUND **ELECTROLYTIC REPLACE-**MENT CONDENSERS

GIRARD-HOPKINS, Oakland, Calif.



To the editor of the

To the editor of the magazine section of "RADIO". Hon. Friend:

You have unquestionably read without doubt from previously sent letters of lack of radio engineering education which Scratchi fail to enjoy. Hon. neighbor friend inform me that such education can be advanced several stages with increased efficiency if new announced correspondence course in radio engineering be given look in consideration. From perusal of numerous and scandalously exaggerated phraisings of correspondence school advertising writers Scratchi find that best correspondence school to make enrollment in is such as are known as Minnieslopolis Institot of Technicalknowledgy. Request to such school for radio engineering catalogs bring notice from Hon. postal authority that school have make movement to Cincinnapolis for non-payment of one office rent in former city. It then become quite necessary to contact with other schools which are more stable in operation. Next letter go to The Great Inter-solar College of Technical Education For Up The Ladder Students who, upon reaching top of such education ladder, can forthwith walk into office of president of any radio concern, fire the boss and take seat in boss's chair without benefit of employment application. Such inducement sound interesting to Scratchi

without benefit of employment application. Such school also offer post-graduating course in beakeeping, stable management and Swiss bell ringing.

Such inducement sound interesting to Scratchi and upon sending enrollment fee of 25 yen in advance, there soon come to me through mails my first lesson in new school. First chapter of first lesson are entitled, "What Is A Watt and What Of It Anyway?" Further instructions say that if such subject are not of interest to student, he can skip first 400 pages of text and proceed to second lesson which are entitled, "Ohm's Laws And How To Violate Them".

Subject then become quite interesting because all calculations made from formulas given in textbook work out fine on paper but when applied to amateur transmitter in radio shack, each tube blow out one by one and it soon become apparent with Scratchi that correspondence school must be stockholder in tube manufacturing plants.

But before course are half finished I am asked to send final payment to schools and upon doing such I am mailed all of balance of lessons in one stack, together with neatly rolled Diploma which are large enough to cover roof of radio shack. President of school also attach personal letter which he forget to sign and inform me I am now ready to step out of the world of hardship and misery and enter the life of the aristocrooks of leisure, the radio engineering fraternity.

I go to print shop and have nice cards printed on which read—Hon. Igiolo Scratchi, Seasoned Radio Engineer & Employment Looker For. My quest for employment seeking begin following morning. I go from factory to factory and each manager tell me same, old sour story—" We have such many radio engineers in our plant that we ship one out free with each case of radio sets so that lazy dealers can make sure that such sets work when they and the engineer are unpacked from the box." One dealer become insulted when he open box and find half-starved engineer crawling out from under X-celsior and he promptly stuff engineer back in box again and s

when he know practically everything about noting."

Such heart busting experience soon get under Scratchi's skin like exzeema and I thus make trail for home with one pocket full of correspondence school diploma and other pocket full of emptiness, but which once hold gold plunder which Scratchi pay over to correspondence school for course in radio engineering.

Next morning I start anew my quest for position, with added determination, because diploma say I can step into chair of any radio factory president, big or small. I walk into big factory plant, thro out my chest and shake diploma at fat president who are fast asleep in soft chair. I pound fist on table, he wake up and ask me what-in-the-who-in-the something I want. I show (Continued on Page 37)

"R9 SIG paid 60c W6BY, CATHO

CRYST square, kimer S BACK (sues, ca Address 128th St

Prompt, Kahn, 1

Scrat

because in his for me of facto for ma most exposition plication of facto He a uncurl list of have be E.E., Mand B.S. He tallast on he tell I have and he

say are really the election is so look at He tell I see of sun friend



"R9 SIGS!" Book on transmitting antennas. Post-paid 60c net. Get louder reports and more DX! W6BY, Box 31, Redlands, Calif.

CATHODE RAY OSCILLOSCOPES completely built and tested to your order. Special designs. Send us your specifications. Prices on request. Prompt, reliable engineering service. Frederick Kahn, 1366 21st Ave., San Francisco, Calif.

CRYSTALS: 80 or 160 meter bands, Y cut, 1" square, accuracy .002%, \$1.50. W8CHJ, 9255 Herkimer St., Detroit, Mich.

BACK COPIES OF "RADIO", 25c each, some issues, can be secured from the New York office. Address your orders to Edw. J. Byrne, 253 West 128th St., New York City, New York.

Scratchi

ering eigh-n be ency radio

rom rated ising lence lown edgy. cata-that for

beetchi

sec-And

ause ext-d to olow with ock-

sked

one hich ack.

and of

med My ing ach We that

osi-ory ory at air.

(Continued from page 36)

(Continued from page 36)
him my diploma and tell him to get out of chair,
because Scratchi are ready to step in as president
in his place. He tell me it are not very polite
for me to oust him from his position as president
of factory, because he have been holding such job
for many long nineteen years and it would be
most exceedingly hard for him to give up such
position without struggle, with furthermore complications come into case because he is soul owner
of factory of which he are president.
He ask me to let take look-see my diploma. I
uncurl stiff parchment sheet and show him long
list of great titles which correspondence school
have bestown upon me. It read: "Igiolo Scratchi,
E.E., M.D., Ph.D., B.A., B double A, B triple A
and B.S.
He take long pencil and strike off all titles except

and B.S.

He take long pencil and strike off all titles except last one which he say approve of very much and he tell me to take it to bank and have it certified. I have friend who have friend who work in bank and he give me introduction to friend who he say are teller in bank. I quickly find out he are really a teller in bank . . . he tell people where the elevator is.

really a teller in bank. I discript him out he are really a teller in bank. I he tell people where the elevator is.

I soon find correct teller person and when he look at last title on diploma he laugh like higheena. He tell me to go to see a lawyer.

I see lawyer and tell him I wish to take legal action against school for improperly informing me of sun bright prospects for graduates but lawyer friend inform me such actions would cost more money than course cost and that court costs would also be more than course costs, so of course if court costs would be more than course costs it appears of course that no recourse can be had from courts. Such legal language when interpreted in any other kind of language simply mean that Scratchi have had again, as usual, been stung. A few more of such similar experiences and Scratchi will make request to be removed to bug house where, I hope, Hon. Editor, you and I will occupy different rooms together.

Your faithful reader, Scratchi.

RADIO CLUBS

Special Group Subscription Rates are offered if 5 or more members subscribe at one time. Write for rates. "RADIO," Pacific Bldg., San Francisco, Calif.

NEW MRL Lowest Loss Coils

Try a Celluloid Coil Form . . . and HEAR the difference! The ever-increasing popularity of the new M.R.L. Celluloid Forms is proof of their superiority. Set of coil forms for the 3-tube R.F. Sargent Receiver described in this issue, \$2.00.

Ultra-Efficient Transmitting Inductances. Wound on 2 inch Celluloid Forms, with 5-prong bases to plug-into standard sockets, 160, 80, 40 or 20 meter bands, \$1.50 list, each.

Dealers and Jobbers Are Invited to Write for Territory
Send 3c stamp for latest MRL Oscillator. Contains many timely circuits and much s.w. data.

Modern Radio Laboratories

151-F LIBERTY ST., SAN FRANCISCO, CALIF.

151-F LIBERTY ST., SAN FRANCISCO, CALIF.



Ask for INCA TRANSFORMERS



INCA is equipped to build transformers or coils for any application. Write for INCA'S new bulletin, L-4, listing a complete line of transformers, chokes and wire for every transmitting, receiving or replacement use. From your jobber or write direct to:

INCA MANUFACTURING DIVISION PHELPS DODGE COPPER PRODUCTS CORP.

2375 E. 27th St., Los Angeles, Calif.



"Best by Test"

All DUCO Condensers fully guaranteed for one year.

IN NO OTHER CONDENSERS DO YOU FIND THESE FEATURES:

- 1. Duco condensers are positively self-healing, even up to 3000 volts.
- Better and longer life than the wet electrilytic condensers.
- Smaller in size than any other make on the market.
- For economy in costs it has no equal.
- DUCO condensers in use over six years showing long shelf and use life.
- All condensers are rated very conservatively.
- Growing faster than any other make. Used by best service men in the world.
- Adopted by finest engineers of set manufac-
- Guaranteed for one year.

DUCO CONDENSERS are fully protected by patents and patent applications all over the world. The response since we intro-duced our new condenser has been remarkable.

You, too, will be surprised at its

Send for Free Catalog Sales and Jobber Territory Open

> Mfgd. by DUMONT

ELECTRIC CO.

453R Broome Street New York City, N. Y., U. S. A.



New Book-Iust Out! 5-METER RADIO-TELEPHONY" By FRANK C. JONES 25 cents per copy. Sold by "RADIO", Pacific Building, San Francisco.

Best and Most Complete 5-Meter Book Ever Published

Engraved Terminal Plates

WRITE for complete bulletins just printed showing several types of terminals and other useful items for every short wave transmitter. Select type of terminal and send us sketch of panel with dimensions. Show location of terminals with lettering and numbering. Quotation will be sent by return mail.

Our products have been used by manufacturers for over ten years

HOWARD B. JONES
ABANSIA AVE. CHICAGO, ILLINOIS 2300 WABANSIA AVE.

Radio Dealers and Jobbers who desire to advertise in these columns are invited to write for rates.

RADIO **BUYERS' GUIDE**

A Monthly Listing of Reliable Radio Dealers and Jobbers who solicit the patronage of our readers. Buy from your nearest Dealer or Distributor. He is dependable and reliable.

DENSER

SERIES

1 = C1

SISTANCE PARALL

CI

R

CHICAGO, ILLINOIS

Chicago Radio Apparatus Company, Inc. 415 South Dearborn Street

Harrison 2276

Dependable Radio Equipment Established 1921

Bulletins on request—we specialize in short wave transmitting and receiving apparatus. Catalog Ten cents.

CHICAGO, ILLINOIS

MID-WEST RADIO MART

520 South State Street CHICAGO

Write for Special Catalog-Free

CHICAGO, ILLINOIS

Newark Electric Company 226 W. Madison St.

Chicago All Kinds of Equipment for Service Men - Amateurs - Experimenters Write for free catalog

OAKLAND, CALIFORNIA RADIO SUPPLY CO.

2085 BROADWAY.

New 2-Tube Sargent DX-Ranger Kit, \$12.50 complete
New Sargent 9-33 Superheterodyne, \$69.50, net,
less tubes
Sargent Short-Wave Sets and Kits.

Write for Circulars.

ST. PAUL, MINNESOTA

LEW BONN COMPANY

2484 University Avenue

Rex L. Munger, W9LIP, Sales Engineer

Radio Wholesaler

ST. LOUIS, MO.

HAMS' TRADING POST

Want to buy? We have it to sell. Want to sell? We will buy for cash. Want to trade? We will trade. References—any midwest ham.

WALTER ASHE RADIO CO.

121 North Eleventh

CHICAGO, ILL.

Allied 🖟 Radio CORPORATION

833 W. Jackson Blvd.

5 meter Headquarters. Complete Stocks of all standard lines of Transmitting equipment, replacement parts, tubes, etc.

Write for our 100-page free catalog



Tube-Short & Leakage Tester

THE new Alden No. 9SC Tube Short and Leakage THE new Alden No. 9SC Tupe Short and Lerkage Tester accommodates all four, five, six, large seven and small seven prong tubes in two especially constructed composite sockets. An insulated control grid cap and lead are provided for connection to all tube caps.

A special nean tube in-

A special neon tube in-A special neon tube indicates leakages up to 1,000,000 ohms, as well as dead shorts. This tester is particularly useful in detecting cathode-to-heater shorts which cannot be tested in the average tube checker.

A special feature is the pair of jacks which general continuity testing when used with

permit general continuity testing when used with a pair of test leads. The circuit is so designed that either test lead may be grounded, even continuously, without causing a short circuit. A single screw through its center conveniently mounts the tester in any position. Five feet of cord is provided with a plug which may be plugged into any AC or DC outlet. The list price is \$3.50.

Tobe Condenser Analyzer

THIS instrument has been designed specifically

THIS instrument has been designed specincally as an aid to the solution of the many problems encountered in condenser testing.

Based on a well-designed and engineered circuit, the instrument operates with ample accuracy and surprising simplicity and speed of test.

dicator. Good condensers with ample accuracy and surprising simplicity and speed of test.

Paper, Mica, and Oil dielectric condensers are tested by the method of measuring the DC resistance under an applied voltage. The resultant leakage current is indicated by means of a special Neon Glow Tube Inhigh resistance, as well as open, shorted, intermittently open and closed, and poor leaky condensers are readily indicated by this instrument. Of interest is the complete analysis the instrument affords electrolytic condensers. Methods of procedure in testing this type of condenser accompanied by technical information constitute a basis for this test. The Glow Tube Indicator quickly gives a measurement of the DC leakage current at the rated voltage passed by the condenser under test. Satisfactory and defective electrolytic condensers are quickly identified.

The instrument contains a built-in power supply operating on a 110 volt AC 60 cycles. Voltages up to 700 volts DC are available for testing at the output terminals. The instrument is encased in a metal container finished in black Damaskene wrinkle. The size of the Analyzer case is 3%-in. by 4½-in. by 7½-in. Net price. \$11.40, east of the Rockies. \$11.70 on the west coast.

Get This New Catalog

Ohmite Manufacturing Company, 636 N. Albany Avenue, Chicago, announces a new Rheostat and Resistor Catalog No. 10. This catalog has eight pages of helpful information concerning the use of these items in both radio and electrical work. It lists many new types of resistors, power rheostats, and replacement units.

This catalog will be sent free to anyone writing for it.

CHICAGO, ILLINOIS

Chicago Radio Apparatus Company, Inc.

415 South Dearborn Street Harrison 2276 Dependable Radio Equipment

Established 1921 Bulletins on request—we specialize in short wave transmitting and receiving apparatus. Catalog Ten cents.

PITTSBURGH, PENNSYLVANIA

CAMERADIO COMPANY

603 Grant Street

Tri-State "Ham" Headquarters Standard Apparatus Standard Discounts

FRESNO, CALIFORNIA

PORTS MANUFACTURING

3265 E. Belmont Ave. Radio W6AVV
National FB7-SW3 and Parts; Hammarlund,
Cardwell, Bliley Crystals; Johnson Insulators.
Complete Stock "Wirts for the Dope
Established 1914 Leading Ham Supply Store

SAN FRANCISCO, CALIFORNIA



1452 Market Street.

"The House of a Million Radio Parts" Hammarlund and National sets and parts. RCA-DeForest Amateur Transmitting Tubes.

Collins Transmitters.
Arcturus Receiving Tubes.
Trimm Phones, all types.
Johnson Antenna Feeders, Insulators,
Transposition Blocks.

SEATTLE, WASHINGTON

SEATTLE RADIO SUPPLY

LARGEST PARTS SUPPLY DEPOT IN THE NORTHWEST

Four of Our Employees Are Licensed Amateurs

DISTRIBUTORS

DUBILIER-WARD LEONARD CARDWELL-RCA TRANSMITTING TUBES WESTINGHOUSE METERS

VANCOUVER, B. C.

Palmer Radio Supply Company 524 WEST PENDER STREET

B. C.'s Original "Ham" Supply House Everything for the Amateur and Service Man Write for Catalogue